

# Arithmetic Micro-operations

Definitions:-

A micro-operation is an elementary operation performed with the data stored in registers. Arithmetic Micro-operations perform arithmetic operation on numeric data stored in registers.

The basic arithmetic micro operations are:-

- Addition
- Subtraction
- Increment
- Decrement




# ADDITION

## MICRO-OPERATION

- The arithmetic add micro operation is given by the statement.
- **$R3 \leftarrow R1 + R2$**
- It states that the contents of register R1 are added with the contents of register R2 and the result will be transferred to register R3.



# 4 - bit Binary Adder

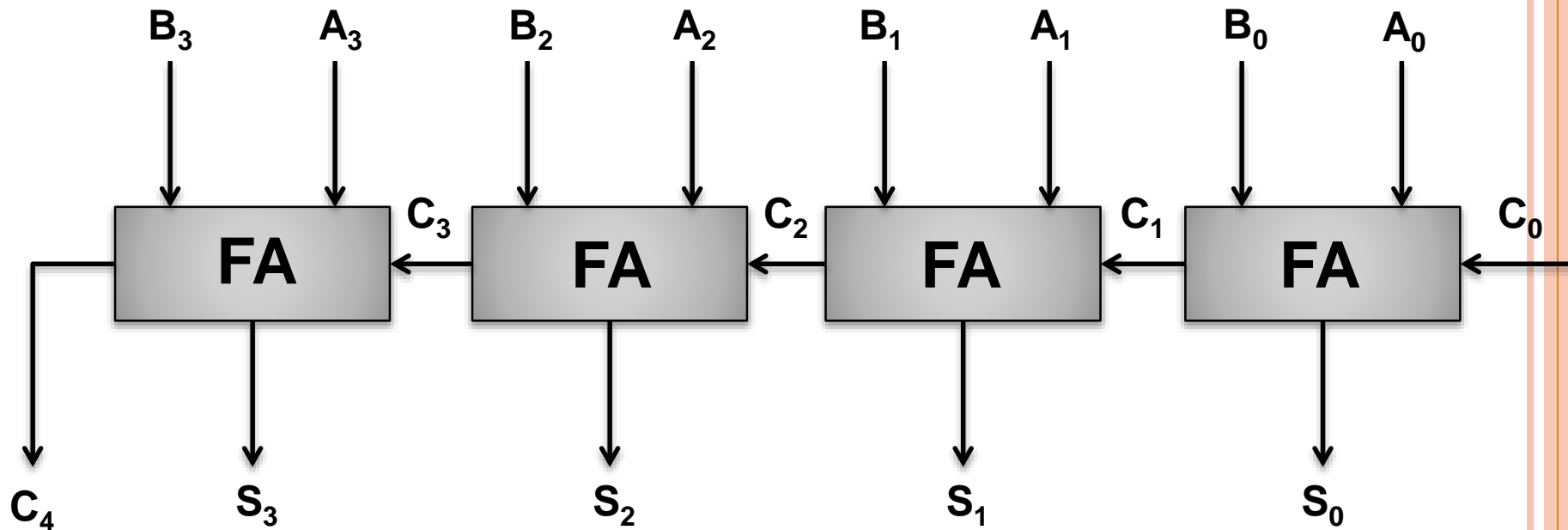

# Working

Add Micro operation can be implemented using Full adders. Each full adder takes 2 inputs from 2 numbers and a third input as a previous carry.

All the carries are connected in serial fashion to the next full adder.

Number of full adders depends upon number of bits of data.

When  $A_0$   $B_0$  are added and initially  $C_0$  is 0 then as a result  $S_0$  gives the sum of  $A_0$  and  $B_0$  and so on.




# ADDITION / SUBTRACTION MICRO-OPERATION

- The arithmetic addition / subtract micro operation is given by the statements,
- $R3 \leftarrow R1 + \overline{R2} + 1$
- $R3 \leftarrow R1 + R2$
- The addition and subtraction operations are performed in one common circuit by including an exclusive-OR gate with each full adder.



# 4 – bit Adder - Subtractor

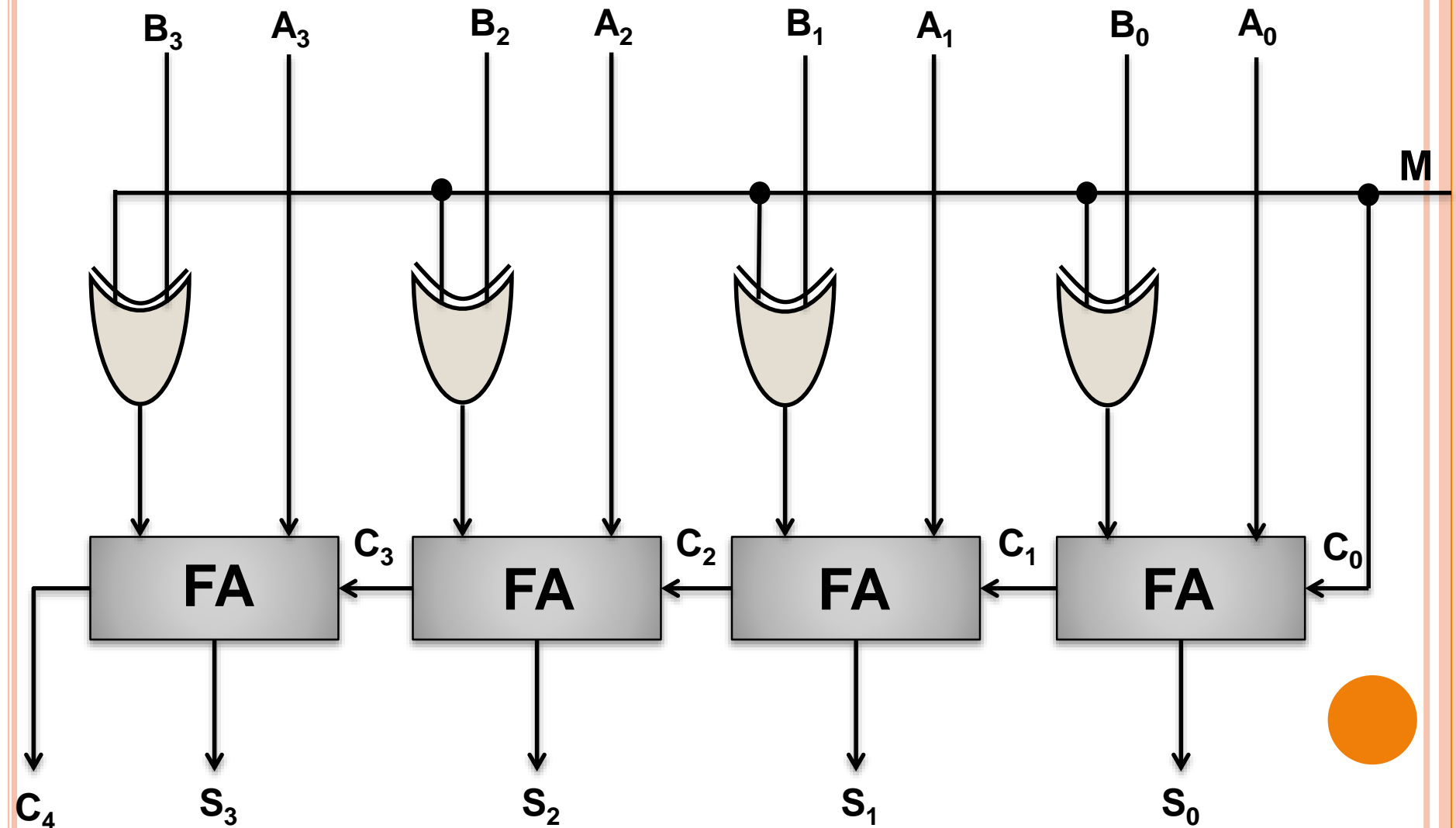

# Working

The addition and subtraction operations can be combined into one common circuit by including an XOR gate with each full-adder.

With the help of a mode bit we can add or subtract.

- **M = 0**

When M is 0 then  $C_{in}$  will be 0 and  $0 \oplus B_0$  gives  $B_0$  then  $S_0$  will be the sum of  $A_0$  and  $B_0$ . hence by M = 0 will perform addition.

- **M = 1**

When M is 1 then  $C_{in}$  will be 1 and  $1 \oplus B_0$  gives  $B_0$  then  $A_0 + B_0 + 1 = A_0 - B_0$  hence M = 1 will perform subtraction.




# INCREMENT MICRO-OPERATION

- The increment micro operation is given by the statement,
- $R1 \leftarrow R1 + 1$
- The contents of register R1 are incremented by one.





# 4 - bit Binary Incrementer

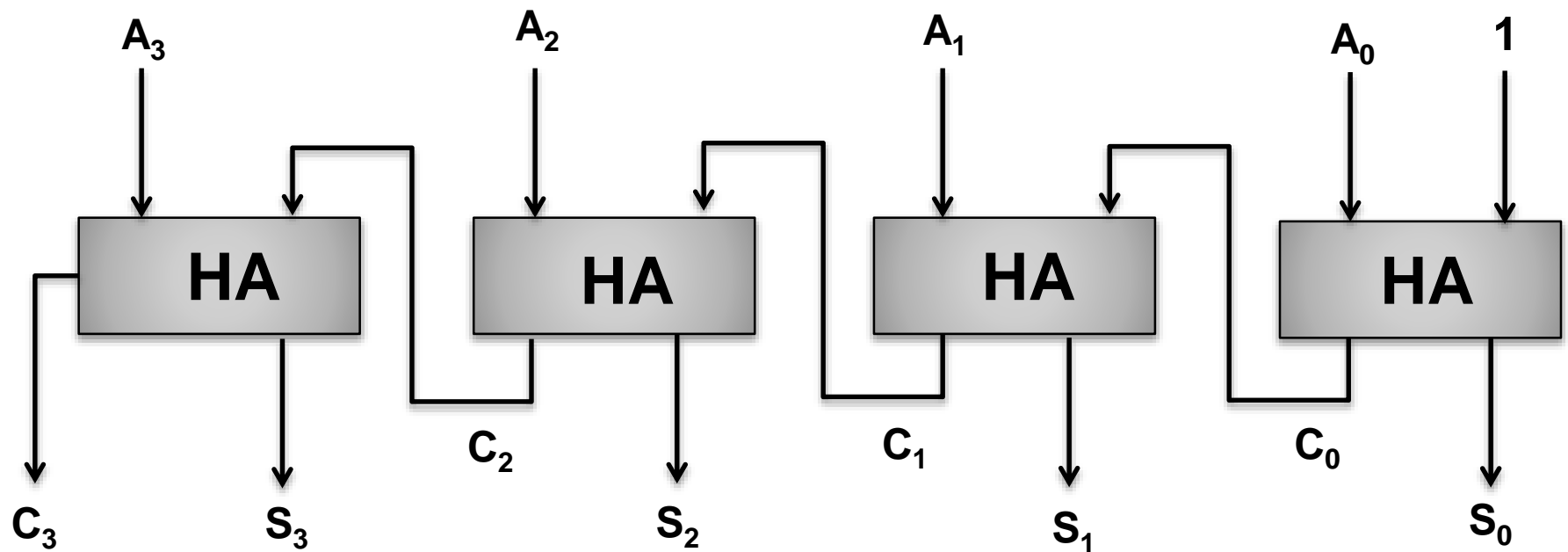

# Working

The increment Micro operation adds 1 to a number in a register.

This Micro operation easily carried out using half adders as described in previous slide.

Each half adder needs 1 input and 1 carry. In the very first half adder the carry is 1.

As this is the increment micro operation hence the carry is forward to the next half adder if generated and as a result sum bits  $S_3$ ,  $S_2$ ,  $S_1$ ,  $S_0$  are generated along with a possible carry out.




# ARITHMETIC CIRCUIT

The basic arithmetic micro operations (addition, subtraction, increment and decrement) can be performed in one composite arithmetic circuit.

Select			Input	Output	Micro operation
$S_1$	$S_0$	$C_{in}$	Y	$D = A + Y + C_{in}$	
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with Carry
0	1	0	$\bar{B}$	$D = A + \bar{B}$	Subtract with Borrow
0	1	1	$\bar{B}$	$D = A + \bar{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A



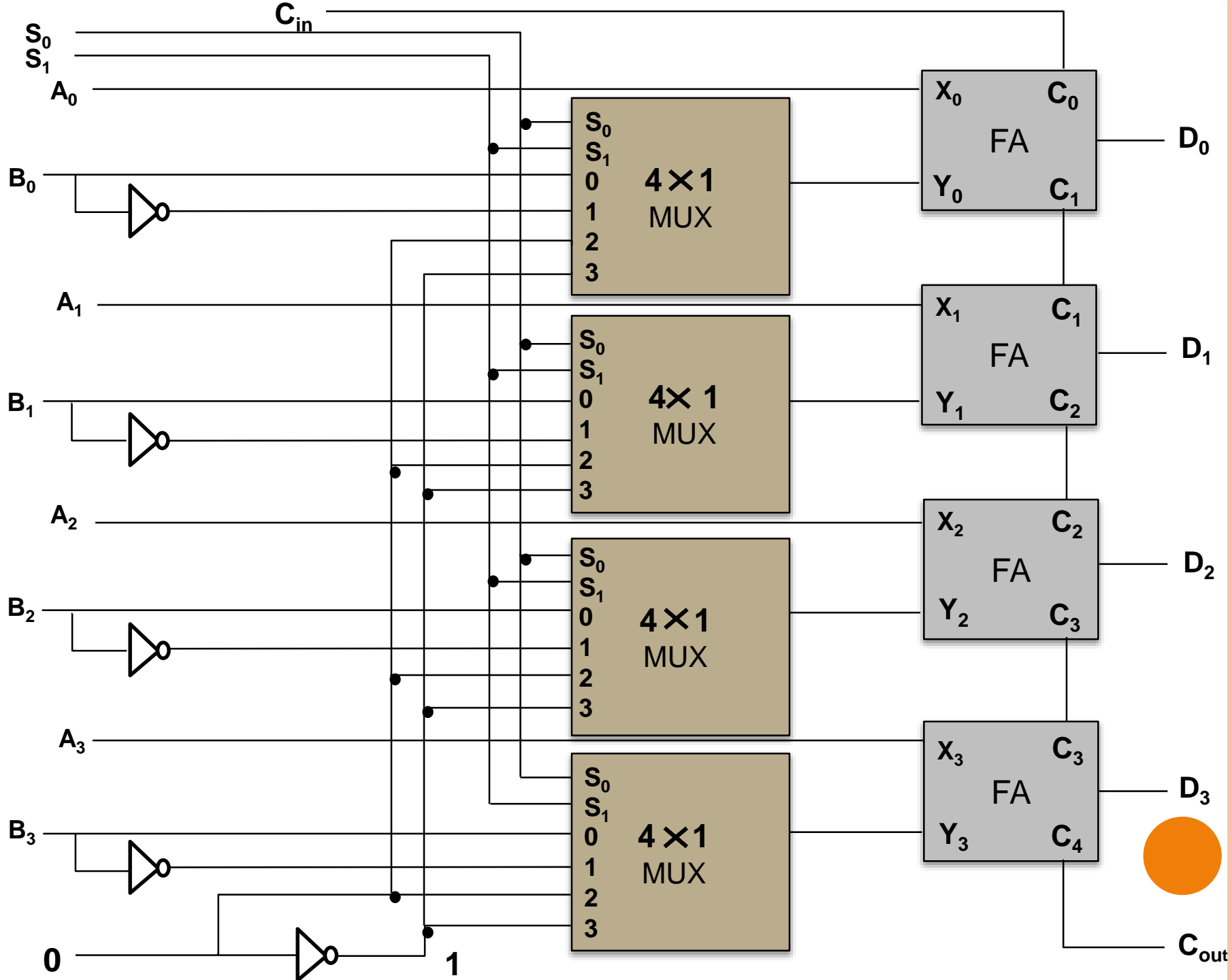

# Working

This arithmetic circuit can perform 8 operations among them some are :-

## **Addition:-**

When  $S_1 S_0 = 0 0$ , the value of B is applied to the Y inputs of the adder. If  $C_{in} = 0$ , the output  $D = A + B$ . if  $C_{in} = 1$ , output  $D = A + B + 1$ . Both cases perform the add microoperation with or without adding the input carry.



## Subtraction:-

When  $S_1 S_0 = 0 1$ , the value of  $B$  is applied to the  $Y$  inputs of the adder. If  $C_{in} = 1$ , then  $D = A + B + 1$ . this produces  $A$  plus the 2's complement of  $B$ , which is equivalent to a subtraction of  $A - B$ . when  $C_{in} = 0$ , then  $D = A + B$ . this is equivalent to a subtract with borrow, that is ,  $A - B - 1$ .



## Increment:-

When  $S_1 S_0 = 1 0$ , the inputs from B are neglected, and instead, all 0's are inserted into the y inputs. The output becomes  $D = A + 0 + C_{in}$ . This gives  $D = A$  when  $C_{in} = 0$  and  $D = A + 1$  when  $C_{in} = 1$ . In the first case we have a direct transfer from the input A to output D. In the second case, the value of A is incremented by 1.



## Decrement:-

When  $S_1 S_0 = 1 1$ , all 1's are inserted into the Y inputs of the adder to produce the decrement operation  $D = A - 1$  when  $C_{in} = 0$ . This is because a number with all 1's is equal to the 2's complement of 1 (the 2's complement of binary 0001 is 1111). Adding number A to the 2's complement of 1 produces  $F = A + 2's \text{ complement of } 1 = A - 1$  when  $C_{in} = 1$ , then  $D = A - 1 + 1 = A$ , which causes a direct transfer from input A to output D.

## NOTE :-

Microoperation  $D = A$  is generated twice, so there are only 7 distinct Microoperations in the arithmetic circuit.

