

Electricity is modern society's most convenient & useful form of energy. Without energy the present society would not at all work. The increasing of consumption of electricity throughout the world reflects a growing standard of living of the people.

The above diagram shows the typical parts of electrical power system in a single line diagram.

Generation of Ac: bulbs of 220 volt work

through maximum to 11 KV or 13.8 KV busbar.

By using hydro, thermal, nuclear, non-conventional Sources. we are generating 6.6 KV, 10.5 KV, 15.75 KV, 21 KV and 33 KV.

Tie line:
The interconnection of Generating stations con-

T/m lines:

200 KV, 400, 500, 750, 165, 800 KV are called as

T/m lines:

Sub-T/m lines:

33 V, 66 V, 110 V, 132 V.

Feeder:

The voltage can be step-down to 33/11 KV.

Distribution substation:

$\frac{415}{240}$ V, 433/250 V, 440/220 V.

Service line:

We are converting the voltages from distribution feeders to consumer lines.

Important Terms:

- * Demand: The average load at receiving terminal over a specified time.
- * Demand Interval: It is the time period over the which the load is average.
- * Connected Load: It is the sum of all load points to and outlets connected to the system.
- * Maximum demand: The maximum power at the ckt drawn at any time is called maximum demand.
- * Demand factor: It is the ratio of maximum demand to the connected load.

$$\text{Demand factor} = \frac{\text{Max. demand}}{\text{Connected load}}$$

- * The Demand factor lies b/w 0.5 to 0.8

Diversity factor: It is the ratio of sum of individual demand to coincident max. demand.

Diversity factor = sum of individual max. demand

or $\frac{\text{sum of coincident max. demand of all consumers}}{\text{sum of individual max. demand}}$

$$= \frac{\sum_{i=1}^n D_i}{\sum_{i=1}^n C_i}$$

coincidence factor: It is the ratio of coincident max. demand of all consumers to sum of individual maximum demand.

co-incidence factor: It is the ratio of co-incidence max. demand to sum of individual maximum demand.

$$= \frac{\sum_{i=1}^n C_i}{\sum_{i=1}^n D_i}$$

It is reciprocal of D.F.

Contribution factor: It is per unit of individual max. demand to max. demand.

Load factor: It is the ratio of Average load to max. demand at a specified demand.

$$\text{Load factor} = \frac{\text{Average load}}{\text{max. demand}}$$

Average load: It is the ratio of no. of units generated to no. of hours at a certain time.

$$\text{Average load} = \frac{\text{Number of units generated}}{\text{number of hrs} \times \text{max. demand}}$$

Loss factor: It is the ratio of average power loss to peak load power loss (or) max. power loss.

Utilization factor: It is the ratio of max. load to rated capacity.

$$\text{utilization factor} = \frac{\text{max. load}}{\text{rated capacity}}$$

Plant capacity factor (PCF): It is the ratio of average annual load to plant rated capacity.

$$\text{plant capacity factor} = \frac{\text{Avg. Annual load}}{\text{plant rated capacity}}$$

Plant use factor: It is the ratio of actual energy produced to multiplication to no. of hours at a certain time.

$$\text{plant use factor} = \frac{\text{Actual energy produced}}{\text{no. of hrs} \times \text{plant capacity}}$$

Problems:

Q. A residential consumer has a connected load of 10A & max. demand of 100W. Find demand factor, load factor & No. of units generated 100W.

Demand factors $\frac{\text{max. demand}}{\text{connected load}}$

$$\text{DF} = \frac{10}{10} = 10, \text{ demand factor}$$

$$\text{Load Factor} = \frac{\text{Avg. load}}{\text{max. demand}}$$

$$\text{load factor} = \frac{0.041}{100} = 0.041 \times 10^{-3} = 0.00041$$


$$\text{Average load} = \frac{100}{24 \times 365} = \frac{1}{8760} = 0.00041$$

Load curve: (load variation with time)

The curve obtained by plotting the time in hrs on x-axis & load on y-axis is known as "load curve".

From the load curve we can know the following information:

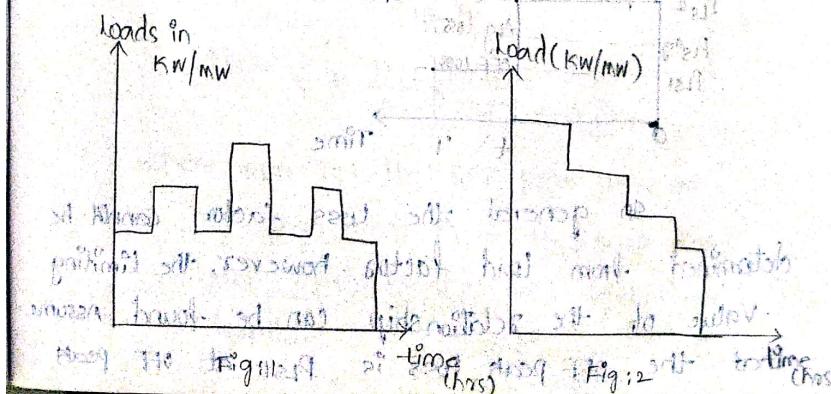1. The variation in load during different hrs is advantageous as load during night is less.
2. The area under load curve represents the total no. of units generated in a day.
3. The min. & max. loads in a day.
4. The area under load curve is divided by area of rectangle is gives load factor.
5. The area under load curve divided by no. of hrs. gives the average load on the power station.
6. And also, load variation after ration A.
7. The load curve for Sunday or holiday is different from the week days.
8. The load curve for summer & winter seasons will be different.
9. The load curve for rural & urban areas will be different.



Load duration Curve:

This curve also gives the variations of the load.


1. It is obtained from load curve.

2. This curve all the loads are arranged in descending order of magnitudes.


3. This is the greatest load on left side/least load on the right side.

Fig. 6.12 shows the load duration curve.

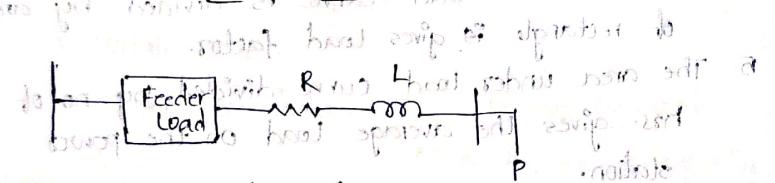* Relationship b/w load factor & loss factor:



A Feeder with variable load.

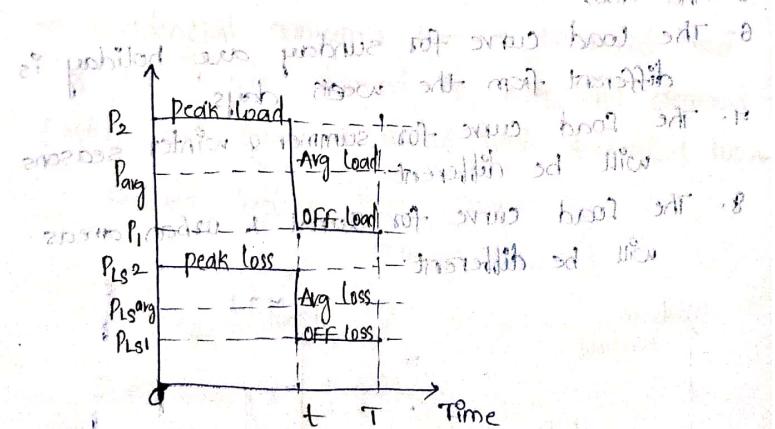

In general the loss factor cannot be determined from load factor. However, the limiting value of the relationship can be found. Assume that the OFF peak loss is P_{LS1} at OFF peak.

load, P_1 . The peak loss is, PLS_2 , at peak load, P_2 .

The load factor is

$$FLD = \frac{P_{avg}}{P_{max}} = \frac{P_{avg}}{P_2} \rightarrow ①$$

From load curve P_{avg} is

$$P_{avg} = \frac{P_2xt + P_1x(T-t)}{T} \rightarrow ②$$

Substitute eqn ② in eqn ①

$$FLD = \frac{P_2xt + P_1x(T-t)}{P_2xT}$$

$$FLD = \frac{t}{T} \times \frac{P_1x(T-t)}{P_2xT} \rightarrow ③$$

The loss factor is

$$FLS = \frac{PLS_{avg}}{PLS_{max}} = \frac{PLS_{avg}}{PLS_2} \rightarrow ④$$

From the load curve,

$$PLS_{avg} = \frac{PLS_2xt + PLS_1x(T-t)}{T} \rightarrow ⑤$$

Substitute eqn ⑤ in ④

$$FLS = \frac{PLS_2xt + PLS_1x(T-t)}{PLS_2xT}$$

$$FLS = \frac{t}{T} + \frac{PLS_1x(T-t)}{PLS_2xT} \rightarrow ⑥$$

where, PLS_1 is the OFF peak loss, at

OFF peak load, P_1 is the peak load

duration, $(T-t)$ is the half peak load duration.

∴ OFF peak load & peak loads can be expressed in

$$P_{LS1} = K \times P_1^2 \rightarrow (i)$$

$$P_{LS2} = K \times P_2^2 \rightarrow (ii)$$

Where, K is constant

Sub (i) & (ii) in eqn ⑥

$$F_{LS} = \frac{t}{T} + \frac{K \times P_1^2}{K \times P_2^2} \times \frac{T-t}{T} \quad \text{or} \quad F_{LS} = \frac{t}{T} + \left(\frac{P_1}{P_2} \right)^2 \times \left(\frac{T-t}{T} \right) \rightarrow ⑦$$

Case : 1 OFF peak load is 0

$$P_{LS1} = P_1 = 0$$

$$\Rightarrow F_{LP} \neq F_{LS} = \frac{t}{T}$$

The load factor is equal to loss factor if

$$\text{they are } = \frac{t}{T} \text{ (constant)}$$

Case : 2 Very short lasting peaks.

$$t = 0$$

$$\Rightarrow F_{LS} = (F_{LP})^2$$

The value of loss factor approaches the value of load factor squared. $\frac{t}{T} = 0$

Case : 3 Load steady

$$\text{for } t=T \text{ i.e. full load for } T \text{ hours}$$

$$\Rightarrow F_{LS} = F_{LP}$$

The value of loss factor is equal to the value of load factor.


In general,

$$F_{LD}^N < F_{LS} < F_{LD}$$

The loss factor cannot be determined directly from load factor.

Approximate formulae to relate the loss factor to load factor:

$$F_{LS} = 0.3 F_{LD} + 0.7 F_{LD}^N$$

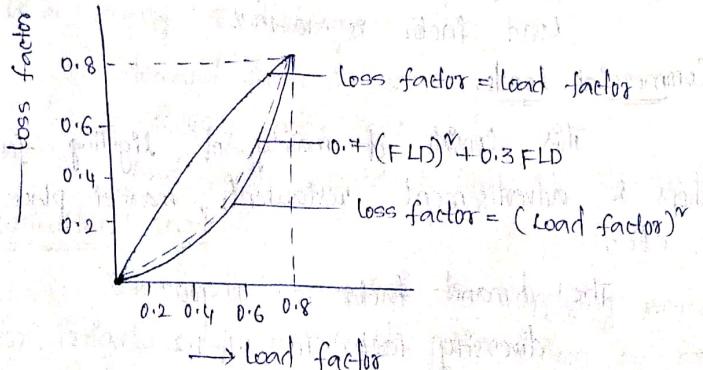

loss factor curves as a f_o of load factor.

Classification of Loads:

1. Domestic loads
2. Commercial loads
3. Industrial loads
4. Municipal loads
5. Agricultural loads
6. Other loads

Domestic loads:

This consists mainly of lights, fans, domestic application appliances such as heaters, refrigerators, air conditioners, mixers, ovens, heating ranges, small motors for pumping, various other small house holding appliances....etc;

Demand factor is 70-100%.

Diversity factor is 1.2-1.3

Load factor is 10-15%

Commercial loads:

This consists of mainly of lighting for shops & advertisement, restaurants, market places.... etc,

The demand factor is 90-100%.

Diversity factor is 1.1-1.2

Load factor is 25-30%

Industrial loads:

These loads may be following power ranges
Cottage industries < 5 kw

Small scale industries 5-25 kw

Medium scale industries 25-100 kw

Large scale industries 100-500 kw

Heavy industries above 500 kw

For large scale & heavy industries need power over large period & which remains uniform throughout day.

For large industries,
demand factor 70-80%
Load factor 60-65%
For heavy industries,
demand factor 35-90%
Load factor 70-80%

Municipal loads:

This load is for street lighting & remains practically constant throughout night.

The other type of municipal load is for water supply & drainage.
Demand factor is 100%.
Diversity factor is 15%.
Load factor for street light is 25-30%.

Agricultural loads:

This load is required for supplying water for irrigation by means of pump driven by motor.

Load factor is 20-25%.
Diversity factor is 1-1.5%.
Demand factor is 90-100%.


Other loads:

The other load such as bulk supplies, special industries such as paper, textile, etc,

Government loads have their own characteristics.

Characteristics of loads:


Domestic loads:

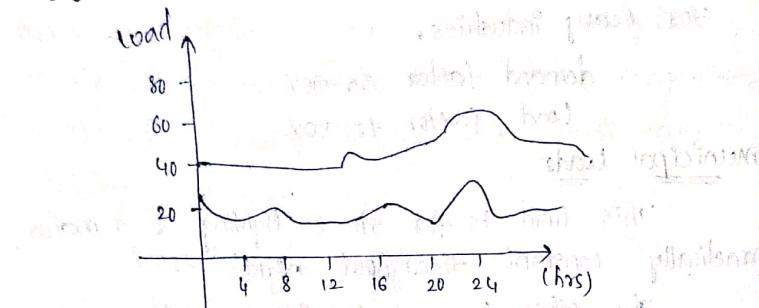

From figure during morning hrs, load requirement is very less.


During evening hours, load requirement is very high & max. during 6pm to 10pm.

Commercial loads:

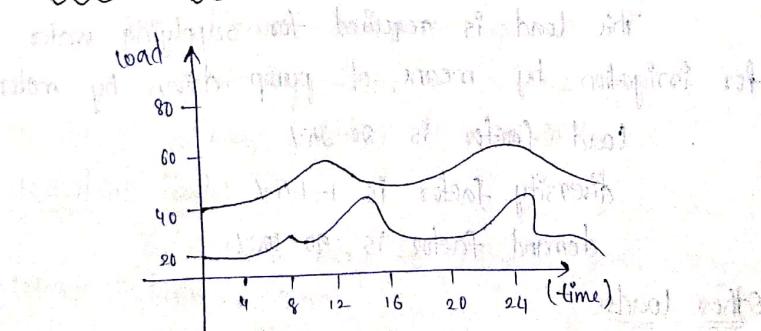

During morning hours load requirement is high and maximum during 8 to 10 pm.

During night, load requirement is less.

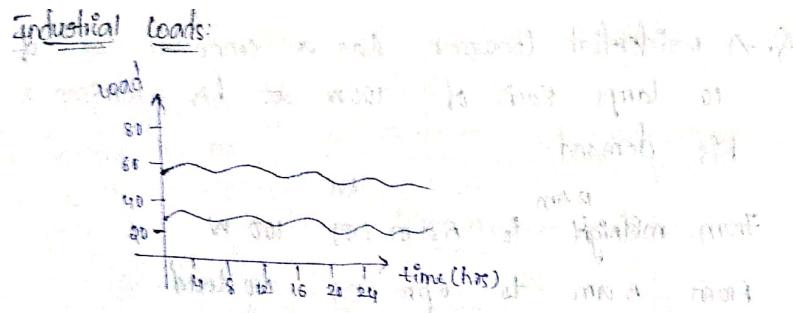

From graph, for industrial loads, the load requires throughout the day.


7/10/22 Problems

Q. A daily load on a station is given below:

Load, KW	1000	5000	500	3000	2000
Time, hrs	4	3	6	6	5

It is desired to draw a load duration curve & determine energy units consumed in a day.
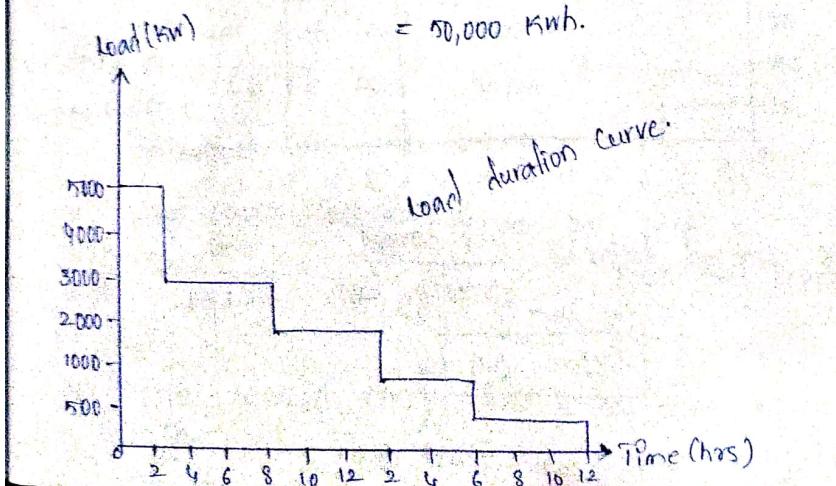
$$\begin{aligned}
 \text{Total energy consumed} &= 1000 \times 4 + 5000 \times 3 + 500 \times 6 + \\
 &\quad 3000 \times 6 + 2000 \times 5 \\
 &= 4000 + 15000 + 3000 + 18000 + 10000 \\
 &= 50,000 \text{ Kwh.}
 \end{aligned}$$




Q. A residential consumer has a connected load of 10 lamps each of 100W at his premises & his demand:

	100	0	800	900	600
12 Am	100	5	13	1	2
From midnight to 5 am (5)	100 W				
From 5 am to 6 pm (13)	no load				
From 6pm to 7pm (1)	800W				
From 7pm to 9pm (2)	900 W				
From 9pm to midnight (3)	400W				
12 pm	100	5	13	1	2

a) plot the load curve. & $C.L = 10 \times 100 = 1000W$

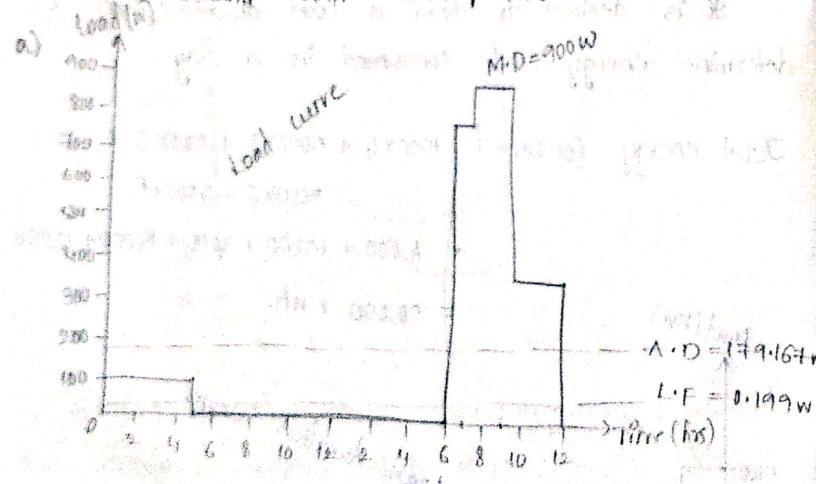b) Determine Demand Factor, Avg. demand, max. demand and load factor.



b) Demand factor = $\frac{\text{Max. demand}}{\text{Connected load.}} = \frac{900}{10 \times 100} = \frac{900}{1000}$

D.F = 0.9 /W

$$\begin{aligned}
 \text{Average demand} &= \frac{\text{No. of units generated}}{\text{No. of hrs}} \\
 &= \frac{100 \times 15 + 67.5 + 800 \times 1 + 900 \times 2 + 1000 \times 3}{24} \\
 &= \frac{1500 + 67.5 + 800 + 1800 + 3000}{24} \\
 &= \frac{6367.5}{24} \\
 &= 265.3125 \text{ kW} \\
 \text{Annual demand} &= 265.3125 \times 8760 \\
 &= 2270.16 \text{ MWh} \\
 A.D. &= \frac{2270.16}{24} \\
 &= 94.16 \text{ kW}
 \end{aligned}$$

- Q. Assume that annual peak load of 1^o feeder is 8000 kW, at which the power loss i.e., total copper loss (I²R loss) is 80 kW per 3-φ. Assume annual loss factor is 0.15. Determine
1. Avg. power loss
 2. The total annual energy loss due to copper loss of the feeder.

Given,

$$\text{Annual peak load} = 8000 \text{ kW}$$

$$\text{Copper loss} = 80 \text{ kW}$$

$$\text{Annual loss factor} = 0.15$$

$$\begin{aligned}
 \text{a) Avg. power loss} &= ? \quad \text{Annual loss factor} \times \\
 &\quad \text{peak load power loss} \\
 A.P.L. &= 0.15 \times 80 = \underline{12 \text{ kW}}
 \end{aligned}$$

$$\begin{aligned}
 \text{b) Total annual energy loss} &= \text{Avg. power loss} \times \\
 &\quad \text{no. of hours} \Rightarrow 12 \times 8760 = 105120 \text{ kWh.}
 \end{aligned}$$

Assignment - 1

1. Derive the relationship b/w load factor & loss factor?
2. Explain load curve & load duration curve?
3. Classification of loads with their characteristics?


Assignment - 2

1. Explain connection schemes of Distribution S/m's?
2. Derive V.D when d/lr connected at both ends with equal & un-equal voltages with C.L?
3. Derive V.D for d/lr fed at both ends with equal & un-equal voltages with U.L?

Assignment - 3

1. Explain Primary feeder voltage levels & its factors?
2. Factors affecting primary feeder loading?
3. Explain voltage drop calculations:
 - i) when the p.F loads refers to receiving end voltage?
 - ii) p.F loads referred to respective load voltages?
4. Define TAF?

UNIT-2
DC DISTRIBUTION SYSTEMS

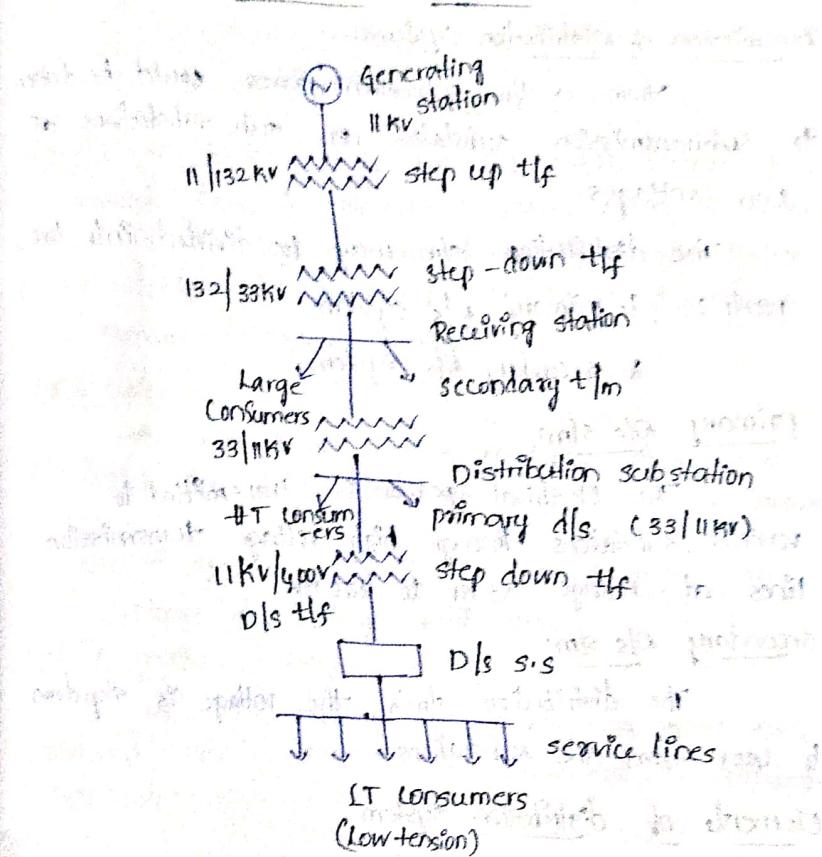

The electrical power s/m has 3 important components:

1. Generating s/m
2. Transmitting s/m
3. Distribution s/m

The electrical energy produced, at g.s is conveyed to consumers through the tlm & distribution s/m's.

It is difficult to draw the lines b/w tlm & d/s s/m's of large power system, so

We have used single line diagram for representing the O/S S/m.

Transmission & Distribution systems:

* From a H/m substation power could be taken to subtransmission substation or sub substations at low voltages.


The distribution s/m may be divided into two parts :
1. primary O/S system
2. secondary O/S system,

Primary O/S s/m:

The Electrical power is transmitted to various substations through high voltage transmission lines at voltage 33 KV to 820 KV.

Secondary O/S s/m:
The distribution s/m's, the voltage is stepped down to 400V from the substations.

Elements of distribution system

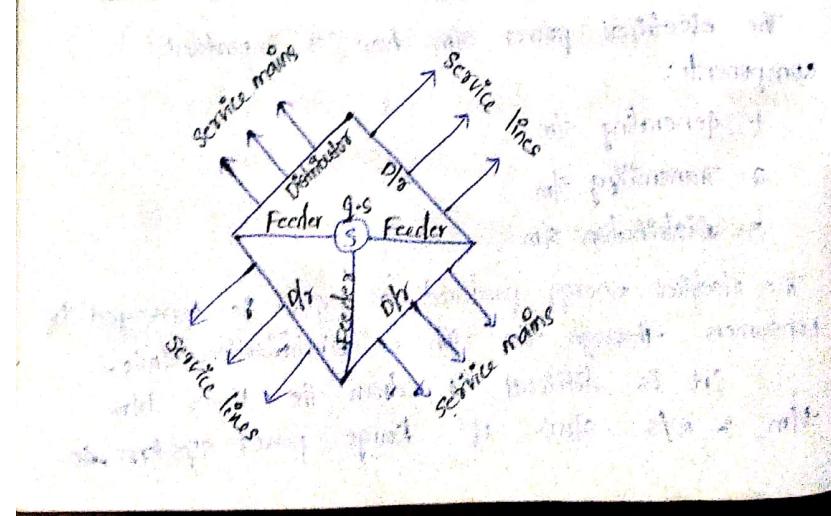

The distribution system can be subdivided into three parts:

1. Feeders

2. service mains.

3. Distributors

Feeder: A Feeder is a conductor which connects the substation (G.S) to the area where power is distributed.
* There is no tappings are taken from the feeder.
* The design of feeder is considered depends on current carrying capacity.

Distributor:

A Distributor, is a conductor from which tappings are taken from the supply to the consumers.
* The design of D.R is considered depends on voltage drop along with length.

service mains:

A service mains is generally a small cable/conductor which connects the distributor to consumer terminals.

Development of distribution plan:

The distribution plan for a particular area, the following main points should be considered:

1. Service conditions:

i) Load to be served

ii) density of customers

iii) Length of lines.

iv) Points of supply.

2. Electrical design:

- i) voltage of supply
- ii) then voltage regulation at the consumers
- iii) transformers and accessories

iv) protection of electrical systems and
v) operation of the system.

3. Mechanical design:

- i) poles and spans
- ii) hardware and guyings
- iii) wires and clearances and

4. Cost:

per kilometer of distribution lines and cost
per consumer.

Requirements of a distribution system:

The following are the requirements of a
good distribution system:

1. Proper voltage
2. Availability of power on demand
3. Reliability
4. Proper voltage

One of the primary requirements of a
dls system is that the voltage variations at
the consumers terminals should be as low [as possible].
while low voltage causes revenue loss, inefficient
lighting and possible burning out of motors] the
high voltage causes permanent burning out of

- the lamps and may also cause failure of other appliances.

2. Availability of power on demand:

A good DLS must make available the consumers the required amount of power efficiently. This necessitates that operating staff must continuously study load patterns.

3. Reliability:

Another important requirement of a good DLS is its reliability. Although cent percent reliability is not possible yet the reliability can be improved to a considerable extent by:

- i) Interconnected S/m
- ii) Reliable automatic e.s
- iii) providing additional reserve facilities.

Classification of DLS systems:

1. According to "nature of current":

- i) D.C. distribution S/m
- ii) A.C. distribution S/m

2. According to "type of construction":

- a) overhead S/m

- b) underground S/m

3. According to "scheme of connection":

- a) Radial S/m

- b) Ring main S/m

- c) Interconnected S/m

- d) piped in gas distribution system

According to "Number of wires":


- Two-wire s/m
- Three-wire s/m
- Four-wire s/m

Connection schemes of distribution s/m:

according to scheme of connections, the d/s s/m is classified into 3 parts:

1. Radial d/s s/m
2. Ring main d/s s/m
3. Interconnected d/s s/m

1. Radial distribution s/m:

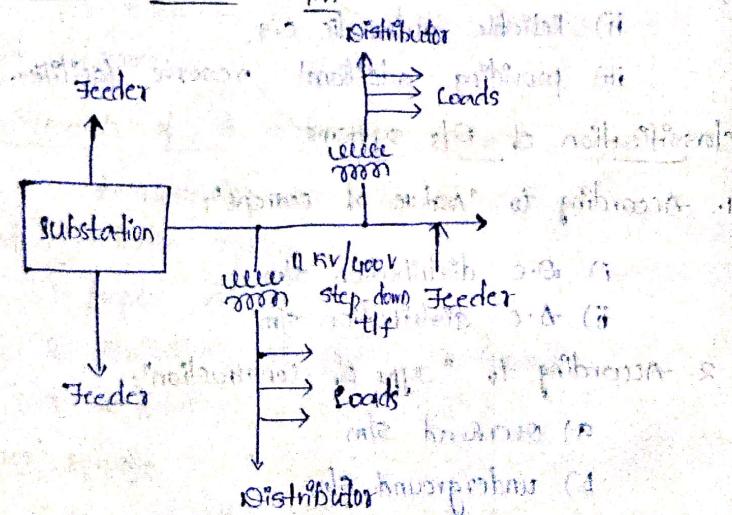


1. The end position of the distributor nearest to the feeding point will be heavily loaded.
2. The consumers are dependent on a single feeder and single distributor. Therefore, any fault on the feeder or distributor cuts off supply to the

consumers who are on the other side of fault away from the sub-station.


3. The consumers at the distant end of the distributor would be subjected to serious voltage fluctuations when the load on the distributor changes. Due to these limitations, this system is used for short distances only.

2. Ring main Distribution System:

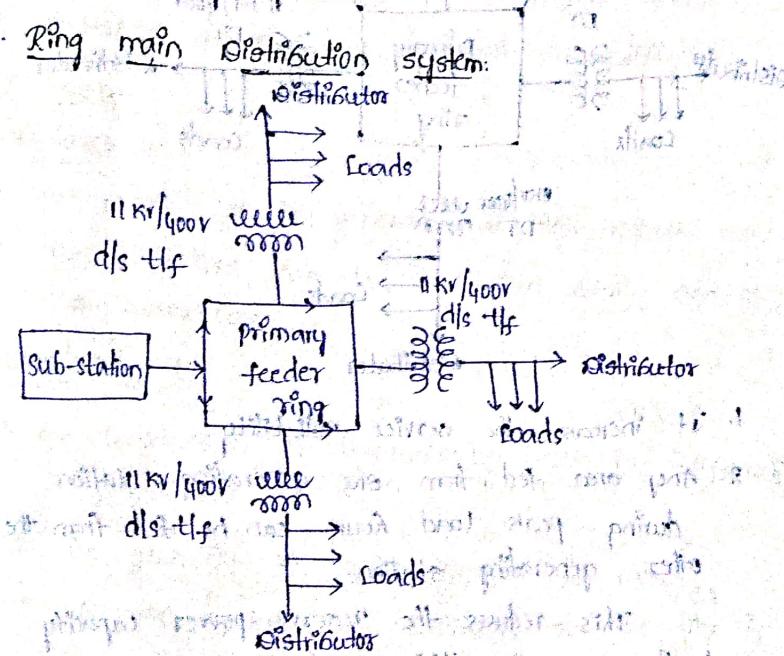

1. There are less voltage fluctuations at consumer's terminals.
2. The system is very reliable, as each distributor is fed via both the sides of the feeder.
3. Less copper is required for the conductors as each part of the ring carries less current than that in radial systems.

3. Interconnected Distribution system:

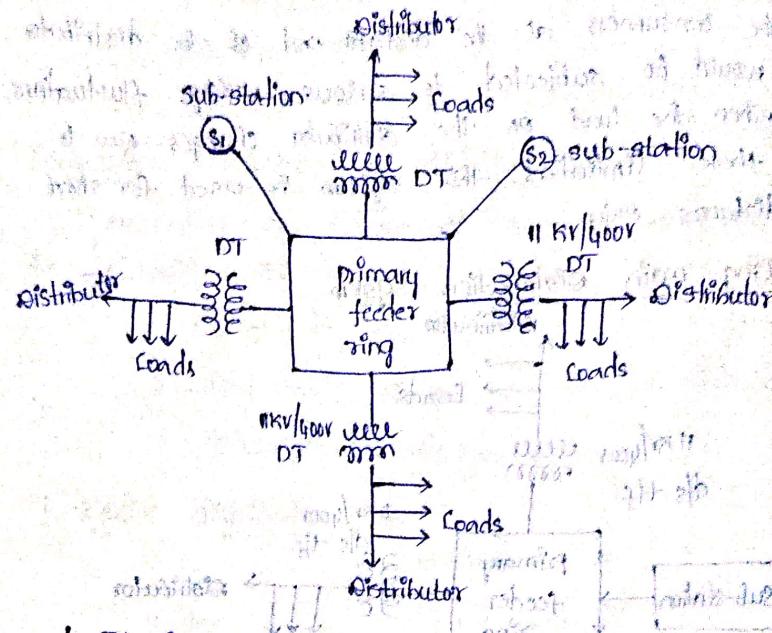

1. It increases the service reliability.
2. Any area fed from one generating station during peak load hours can be fed from the other generating station.

This reduces the reserve power capacity and increases the efficiency of the system.

Comparison b/w DC & AC systems of transmission

DC and AC distribution:

DC system:

Advantages:

1. There is greater power per conductor and simple line construction.
2. Ground return is possible.

- 3. No stability problems & synchronizing difficulties.
- 4. Since, the potential stress on the insulation in case of DC system is $4\sqrt{2}$ times that in AC.

Disadvantages:

- 1. Converters require considerable reactive power.
- 2. Harmonics are generated which require filters.
- 3. Converters do not have overload capability.

AC system:

Advantages

- 1. The power can be generated at high voltages.
- 2. The substations can be maintained easily and at a lesser cost.

Disadvantages:

- 1. The construction of transmission lines is comparatively difficult.
- 2. The quantity of copper required is more.
- 3. In AC system, the resistance of the line is increased due to skin effect.

Comparison between overhead lines and underground cables:

- 1. The large charging current on very high voltage cable limits the use of underground cable for long length t/m , where a long distance t/m is required, over t/m lines are used.

2. The insulation cost is more in case of cables than the overhead lines.
3. The erection cost of an overhead line is much less than the underground cable.

There are certain situations, They are:

1. For power stations and substation, Connection

(or) a link in overhead lines.

2. For submarine crossings.

Overhead lines

→ ^{over} _{high v} _{l/m}	→ ^{under} _{low v} _{l/m}
→ _{in X loss} ↓	→ _{regulation/lss} ↓
→ <u>Adv:</u> _{more insulation} → _{cost ↓}	→ _{cost ↑}
→ _{fault easy} → _{difficult}	→ _{fault diff} → _{more diff}

1. J/m & Φ/s by overhead lines is much cheaper than the underground cables.

2. The capacity of l/m-line can be increased easily by only replacing the conductor, by now one of larger cross-sectional area.

Dis-adv:

1. The overhead lines are subjected to supply interruptions due to lightning, short-circuits, the breakage of line conductors, bird-faults etc.

2. Maintenance cost is higher.

3. Interference with communication circuits.

→ _{radio wave} _{radio noise} _{interference} _{with} _{radio} _{noise}

under-ground cables:

Adv:


1. Elimination of accidents to public
2. Freedom from interruption of service and damage due to the thunderstorms, lightning and falling objects.
3. No disturbance to communication chls.

Dis-adv:

1. underground cable sl/m is more costly than the overhead system.
2. Faults cannot be easily detected by inspection
3. Repairs and extension is not as easy as in overhead sl/m.

Types of DC distributors:


1. Distributor fed at one end:

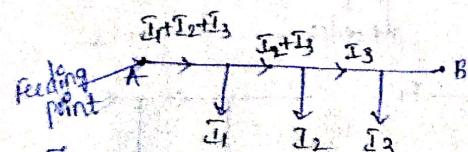

* The current at various sections of the d/lr away from the feeding point is I .

* The fault occurs in any section of the feeder the whole d/lr will have disconnected from the supply mains. Therefore, the continuity of supply is interrupted.



2. Distributor fed at Both ends:

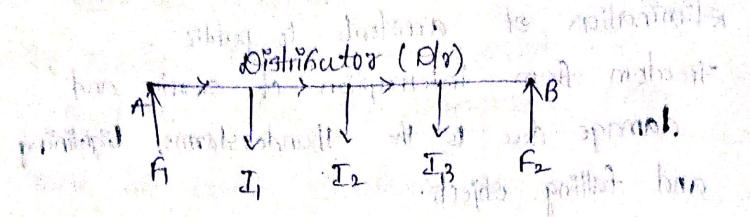

* The fault occurs on any feeder & point of the D/r, the continuity of supply maintained from other feeding point.


* The area of cross-section of conductor required for D/F Double fed D/r is less than single fed d/g.

3. Distributor fed at centre:

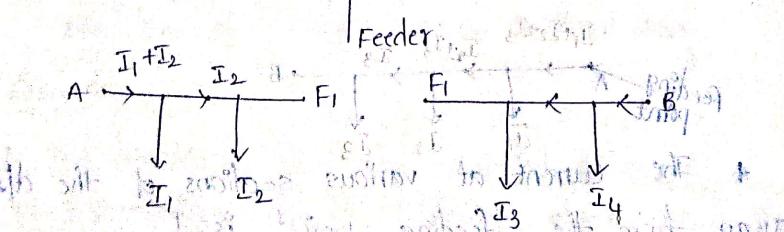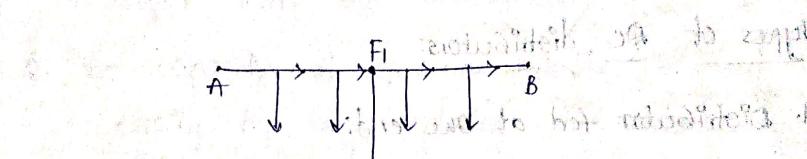

* The d/r is equivalent to two-single fed d/r's, each d/r having common feeding point and length equal to half-off-the total length.

4. Ring main Distributor:

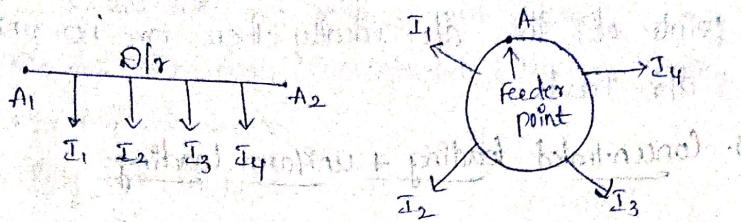


* It is equivalent to straight d/r fed at both ends with equal voltages, the two ends combined together to form a closed ring.

Types of loadings:


1. Concentrated loading
2. Uniform loading
3. Concentrated loading in addition with uniform loading.

* Concentrated loading:

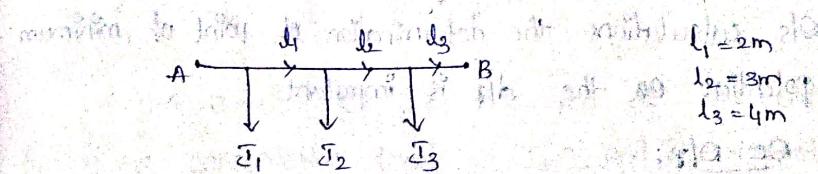


The concentrated loads act on a particular point of the d/r. The magnitude of loads & length of sections of d/r may be unequal.

* uniform loading:

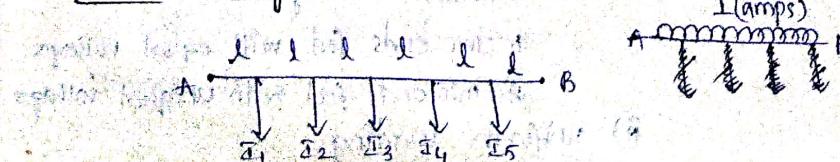

The d/lr loads are uniformly loaded on all points of the d/lr. Ideally there are no uniform d/lr loads.

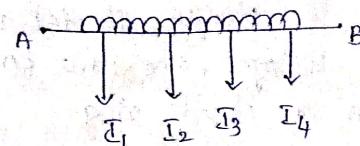3. Concentrated loading + uniform loading:



The above diagram shows the combination of concentrated loading & uniform loading.

calculation of voltage drops in the distributor:

The main requirement of d/lr is to supply power to consumers at the rated voltage within the permissible voltage variation. Hence, the Ols calculations the determination of point of minimum potential on the d/lr is important.

1. Oc D/lr:

- a) D/lr fed at one end
 - i) concentrated loading
 - ii) uniform loading
- b) D/lr fed at both ends
 - i) concentrated loading
 - 1. two ends fed with equal voltages
 - 2. two ends fed with unequal voltages
 - ii) uniform loading

1. Two ends fed with equal voltages

2. Two ends fed with unequal voltages.

c) D/c fed with both concentrated & uniform loading

d) D/c fed at centre.

e) Ring main D/c.

2. AC D/c:

a) concentrated loading


i) 1- ϕ AC supply using 2-wire s/m

ii) 3- ϕ AC supply using 3-wire s/m

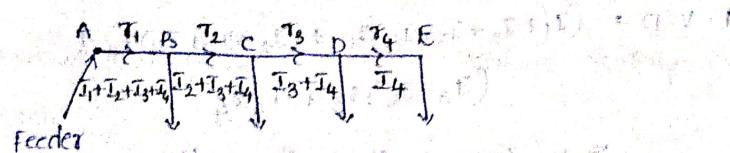iii) 3- ϕ & neutral using 4-wire s/m

Derivations:

DC Distributor fed at one end - concentrated loading:



A 2-wire DC D/c AE fed at one end having a concentrated loads J_1, J_2, J_3 , and J_4 flapped off at point B, C, D, E.
currents

current in section AB = $J_1 + J_2 + J_3 + J_4$

current in section BC = $J_2 + J_3 + J_4$

current in section CD = $J_3 + J_4$

current in section DE = J_4

Voltage of Resistances

Resistance in section AB = r_1

Resistance in section BC = r_2

Resistance in section CD = r_3

Resistance in section DE = r_4

Voltage drop

Voltage drop in section AB = $(I_1 + I_2 + I_3 + I_4)r_1$

Voltage drop in section BC = $(I_2 + I_3 + I_4)r_2$

Voltage drop in section CD = $(I_3 + I_4)r_3$

Voltage drop in section DE = $I_4 r_4$

$$\text{Total V.D} = (\text{V.D in AB}) + (\text{V.D in BC}) + \\ (\text{V.D in CD}) + (\text{V.D in DE})$$

$$T.V.D = (I_1 + I_2 + I_3 + I_4)r_1 + (I_2 + I_3 + I_4)r_2 + \\ (I_3 + I_4)r_3 + I_4 r_4$$

= Σ (current flowing in section + Resistance in section)

$$T.V.D = \Sigma (\text{V.D in individual section}).$$

In a 2-wire DC circuit system the 2 wires (go & return wire) are present.

Hence, the actual V.D will be equal to V.D in both wires. The min. potential will occur at point E which is far from the feeding point - A.


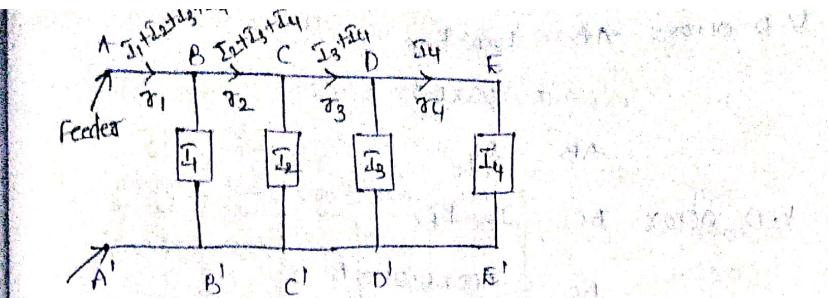



Fig: DC 10/r fed at one end with 2-wire.

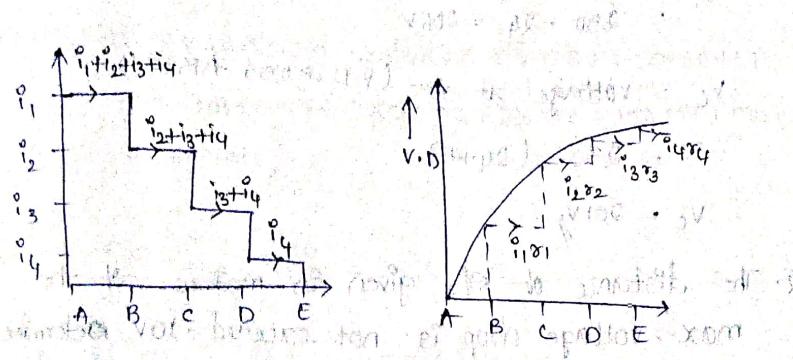

Various currents Various voltage drops.

Problem:

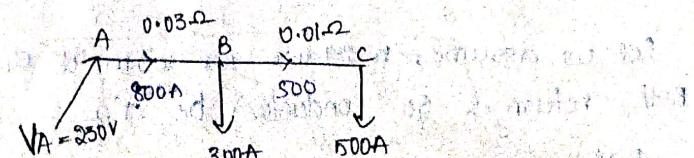1. A 2-wire DC 10/r shown in fig: If the voltage at feeding point A is 230V, calculate the voltage at point B & C?



Given, $V_A = 230V$

$$I_1 = 300A, I_2 = 500A$$

$$r_1 = 0.03\Omega, r_2 = 0.01\Omega$$

$$V.D \text{ across } AB = I_{AB} R_{AB}$$

$$\approx 800 \times 0.03$$

$$AB = 24$$

$$V.D \text{ across } BC = I_{BC} R_{BC}$$

$$BC = 500 \times 0.01 = 5$$

$$V_B = \text{voltage at } A - (\text{V.D across } AB)$$


$$\approx 230 - 24 = 206V$$

$$V_C = \text{voltage at } A - (\text{V.D across } AB + BC)$$

$$\approx 230 - (24 + 5)$$

$$V_C = 201V$$

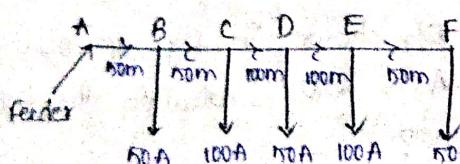2. The distance of Ø1/2 given in meters, if the max. voltage drop is not exceeded 10V. Determine the cross-sectional area of the Ø1/2. Take $\ell = 1.78 \times 10^{-8} \text{ ohm-m}$.



Let us assume, resistance for 100m of Ø1/2 length (Both return & go conductor), be 2Ω


$$\text{Resistance across Sec-AB} = \frac{50}{100} \times 2 = 0.5\Omega$$

$$BC = \frac{50}{100} \times 2 = 0.5\Omega$$

$$CD = \frac{100}{100} \times 2 = 1\Omega$$

$$DE = \frac{100}{100} \times 7 = 17\Omega$$
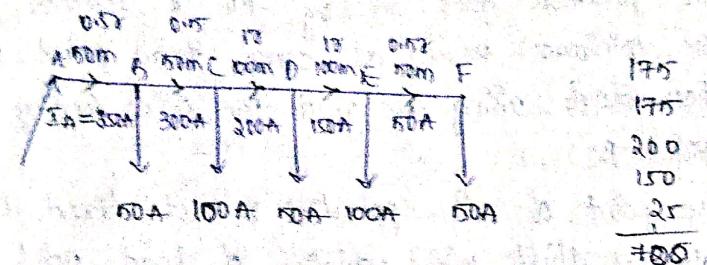
$$EF = \frac{150}{100} \times 7 = 0.57\Omega$$



$$I \cdot V \cdot D = V \cdot D \text{ across section AB} + V \cdot D \text{ BC} + CD \text{ DE} + EF$$

$$= 350 \times 0.57 + 300 \times 0.57 + 200 \times 13 + 150 \times 13 + 150 \times 0.57$$

$$V_1 = 700V$$


$$\tau = \frac{V}{700} - \frac{10}{700} = 0.01428 \Omega$$

$$R = \frac{\rho l}{A} = \alpha = \frac{\rho l}{K} = \frac{1.78 \times 10^{-8} \times (2 \times 100)}{0.01428} = 2.492 \times 10^{-4} \text{ m}^2$$

$$= 2.493 \text{ cm}^2$$

Distributor Feed at both ends - Concentrated Loading:

a) Equal Voltages:

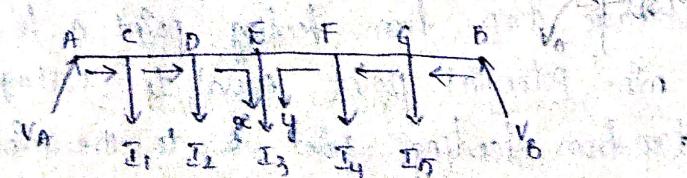

Consider, a dlr AB fed at both ends with equal voltages V (volt) and having concentrated loads I_1, I_2, I_3, I_4 and I_5 at points c, D, E, F, g

respectively.

- As we move away from the feeding point A the potential goes on falling till it reaches the minimum value at some load point, then starts rising we reach the other feeding point B.

The point of min. potential is not fixed it is always shift with variation of load point.


- All the currents tapped off b/w point A & E will be supplied from feeding point A. while tapped off b/w point E & B will be supplied from point B.

- The current tapped at min. point of potential is supplied by both point A & feeding point B.

- The sum of currents fed from feeding point A & B equal to the total load current tapped off from the sys.

$$I_A + I_B = I_1 + I_2 + I_3 + I_4 + I_5$$

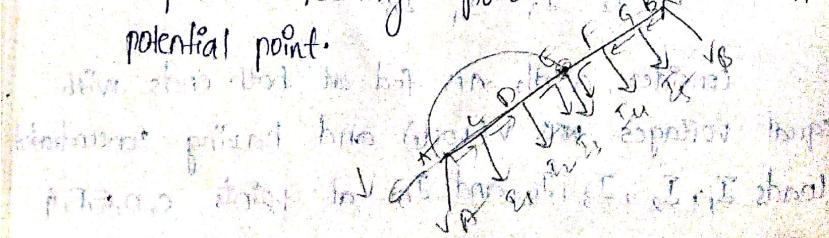- voltage drop from feeding point A to the min. potential point equal to voltage drop from feeding point B to the min. potential point.



<u>section</u>	<u>I in section (A)</u>	<u>R of section (Ω)</u>	<u>V.D in section (volts)</u>
AC	\bar{I}_A	R_{AC}	$\bar{I}_A \cdot R_{AC}$
CD	$\bar{I}_A - \bar{I}_1$	R_{CD}	$\bar{I}_A - \bar{I}_1 \cdot R_{CD}$
DE	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2)$	R_{DE}	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2) \cdot R_{DE}$
EF	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3)$	R_{EF}	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3) \cdot R_{EF}$
FG	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4)$	R_{FG}	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4) \cdot R_{FG}$
GB	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 + \bar{I}_5)$	R_{GB}	$\bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 + \bar{I}_5) \cdot R_{GB}$

Voltage drop from F.p A upto point B,

$$V_A - V_B = \bar{I}_A \cdot R_{AC} + (\bar{I}_A - \bar{I}_1) R_{CD} + \bar{I}_A - (\bar{I}_1 + \bar{I}_2) \cdot R_{DE} + \\ \bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3) \cdot R_{EF} + \bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4) \cdot R_{FG} + \\ \bar{I}_A - (\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 + \bar{I}_5) \cdot R_{GB} \rightarrow ①$$

As the 2 ends are fed with equal voltages

$$V_A = V_B \text{ i.e. } V_A - V_B = 0$$

From the above expression the value of unknown current \bar{I}_A can be determined when the other quantities being known values.


b) un-equal voltages:

The magnitude of voltages at 2 ends are subtracted in eqn ①


The value of unknown current \bar{I}_A can be determined the point of min. potential will be determined in the same manner as that for two ends fed with equal voltages.

$$V_{AB} \quad A_{AB} \quad A_{AB} \quad A_{AB} \quad A_{AB}$$

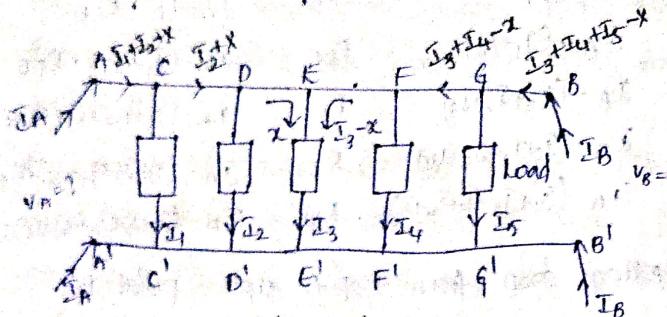- * voltage drop b/w feeding point A & B is equal to voltage drop over d/l/r AB (con)
- * $V_A - V_B = \text{voltage drop over d/l/r AB.}$




a) D/l/r fed at both end

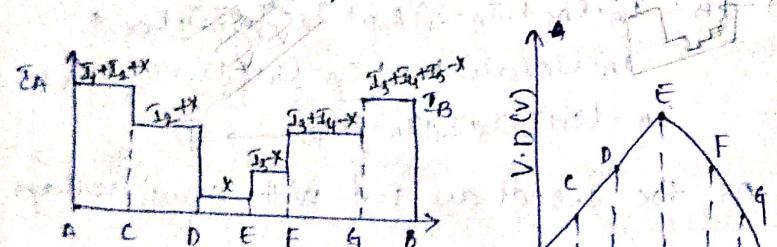

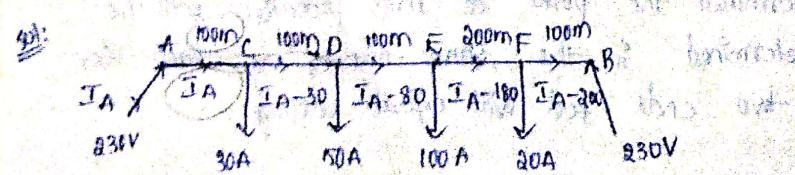b) Current d/l/r at various sections.



Q. A DC σ -wire Ω/l_r , 600m long tapped at distance of 100m , 200m , 300m & 500m from the end A respectively. If the area of cross-section of d/l/r conductor is 1.0 cm^2 . Find the min. consumer voltage take $\ell = 1.7 \times 10^{-6}\text{ cm}$.



Let the current supplied from feeding end (point) A
= I_A (A)

The resistance of 1m length of $\frac{1}{2}$ inch (Both go & return conductors): $\tau = \frac{\rho l}{a} = \frac{1.7 \times 10^{-6} \times 100}{1.0} \times 2$

$$\tau = \frac{\rho l}{a} = \frac{1.7 \times 10^{-6} \times 100}{1.0} \times 2$$

$$\tau = 3.4 \times 10^{-4} \quad \gamma = 0.2$$

Resistance at sec. A.C: R_{AC}

$$R_{AC} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$$

$$CD: R_{CD} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$$

$$DE: R_{DE} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$$

$$EF: R_{EF} = (3.4 \times 10^{-4}) \times 200 = 0.068 \Omega$$

$$FB: R_{FB} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$$


Voltage at A - Voltage at B = V.D over AB

$$V_A - V_B = I_A \times R_{AC} + (I_A - 30) R_{CD} + (I_A - 80) R_{DE} + (I_A - 180) R_{EF} + (I_A - 200) R_{FB}$$


$$230 - 230 = I_A \times 0.034 + (I_A - 30) 0.034 + (I_A - 80) 0.034 + (I_A - 180) 0.068 + (I_A - 200) 0.034$$

$$0 = 0.034 I_A - 22.78$$

$$I_A = 660 A$$

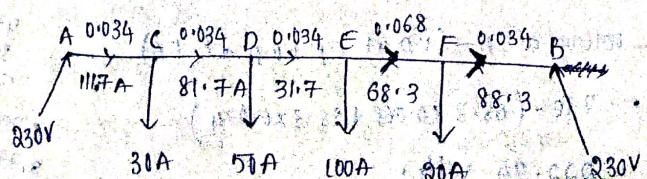


The point 'E' is the minimum value.

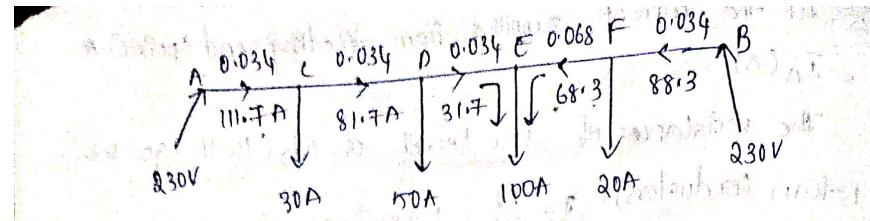

The actual current distributions of various sections of a D/S as shown in figure.

It is clear that the currents are coming to load point E from both sides i.e; from point D to point E hence, E is the min. point of potential.

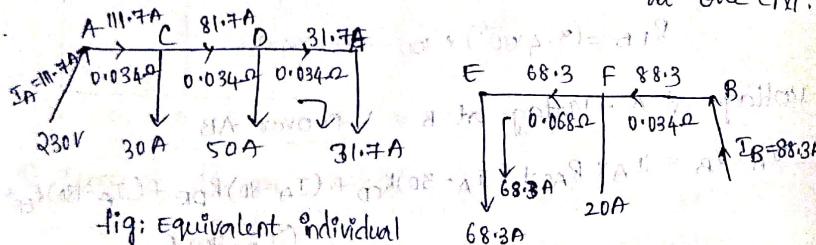The d/s fed at both ends AB under given load conditions, can be treated as d/s fed at one end.



d/s fed at one end: $\frac{230}{0.034} = 6765 \text{ ohms}$


Min. consumer voltage:

$$\begin{aligned} \text{From A: } V_E &= \text{voltage at point A} - (\text{v.d. at AC} + \text{v.d. at CD} + \text{v.d. at DE}) \\ &= 230 - (111.7 \times 0.034 + 81.7 \times 0.034 + 31.7 \times 0.034) \\ V_E &= 230 - 7.654 = 222.346 \text{ volt.} \end{aligned}$$

$$\begin{aligned} \text{From B: } V_E &= \text{voltage at B} - (\text{v.d. at EF} + \text{v.d. at FB}) \\ &= 230 - (68.3 \times 0.068 + 88.3 \times 0.034) \\ V_E &= 222.34 \text{ volt.} \end{aligned}$$

With maximum voltage drop at mid point

DC Ring main OLR

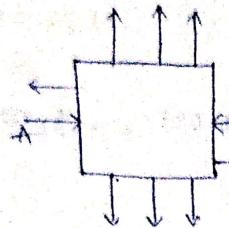

A ring dlr is arranged to form a closed loop & fed at one or more points is called Ring dlr.

A dlr starts from one point, makes a loop through the area to be served & returns to the original point.

Ex-1: A 2-wire ring dlr is 400m long & it is fed at 230V at point A. The various loads are connected as shown in figure. Find

- i) current in each section of OLR
- ii) voltage at load point
- iii) min. potential point

Resistance for 100m of single conductor is 0.01 Ω.

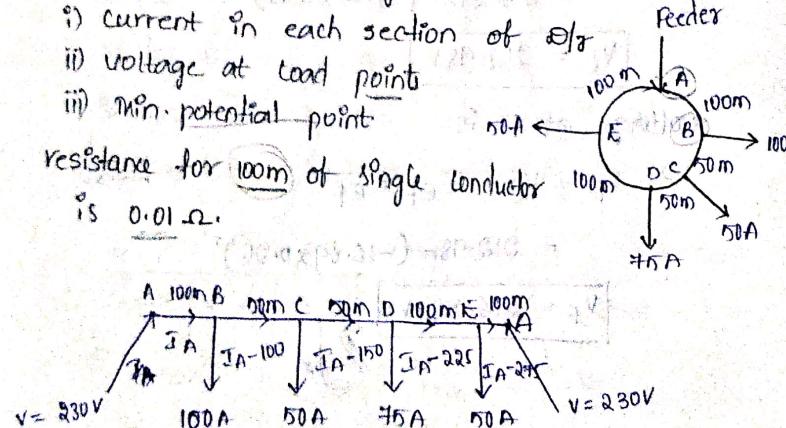


fig: OLR fed at both ends with equal voltages

$$\text{Resistance of single conductor} = 0.01\Omega / 100\text{m length}$$

The total resistance for both (go & return) conductors

$$R = 2 \times 0.01 = 0.02 / 100\text{m} = \underline{\quad}$$

Let 'x' be the current in section AB. The resistance & current in various sections.

<u>section</u>	<u>current</u>	<u>Resistance</u>	<u>Length</u>
AB	x	0.02	100
BC	$x - 100$	0.01	50
CD	$x - 150$	0.01	50
DE	$x - 225$	0.02	100
EA	$x - 275$	0.02	100

voltage drop in the closed loop ABCDEA = 0

$$\begin{aligned}
 \text{T.V.D} &= x \times 0.02 + (x - 100) 0.01 + (x - 150) 0.01 + (x - 225) 0.02 + \\
 &\quad (x - 275) 0.02 \\
 &= 0.08x + 0.08x + (-1 - 1.5 - 4.5 - 5.5) \\
 0 &= 0.08x - 12.5 \\
 0.08x &= 12.5 \\
 x &= 156.25 \text{ A}
 \end{aligned}$$

The current fed in section AB = 156.25 A

$$\begin{aligned}
 I_{AE} &= \text{Total load} - I_{AB} \\
 &= (100 + 50 + 150 + 100) - 156.25 \\
 \textcircled{1} \quad I_{AE} &= 118.75 \text{ A}
 \end{aligned}$$

∴ current in each section


$$AB \Rightarrow I_A = 156.25 \text{ A}$$

$$BC \Rightarrow I_A - 100 = 56.25 \text{ A}$$

$$CD \Rightarrow I_A - 150 = 6.25 \text{ A}$$

$$DE \Rightarrow I_A - 225 = -68.75 \text{ A}$$
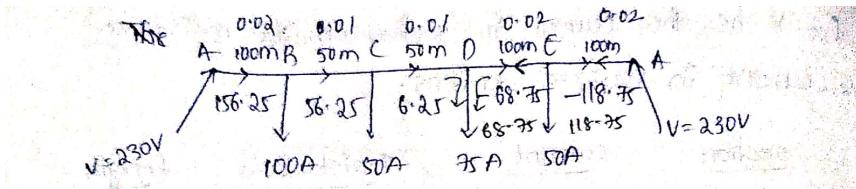
$$EA \Rightarrow I_A - 275 = -118.75 \text{ A}$$



③ The currents are coming to load point D from both sides so, D is the point of minimum potential.

Hence, the currents in ring d/r,

$$I_{AB} = 156.25 \text{ A} \quad | \quad I_{DE} = 68.75 \text{ A}$$

$$I_{BC} = 56.25 \text{ A} \quad | \quad I_{EA} = 118.75 \text{ A}$$

$$I_{CD} = 6.25 \text{ A}$$

② Voltage at point A = 230V

$$V_B = (\text{Voltage at A} - V_D \text{ at AB})$$

$$= 230 - (0.02 \times 156.25)$$

$$= 230 - 3.125$$

$$V_B = 226.875 \text{ V}$$

$$V_C = 230 - (156.25 + 56.25) 0.01 \times 0.02$$

$$= 226.31 \text{ V}$$

$$V_D = V \text{ at A} - (V_D \text{ at AB} + BC + CD)$$

$$= 226.247 \text{ V}$$

$$V_E = V_A - V_D \text{ at AE}$$

$$= 230 - (406.25)$$


$$= 227.625 \text{ V}$$

A two-wire DC Ω/r AB, 600m long is loaded as
10/10/2

Distance from A	150 m	300m	350m	450m
Loads in Amps	100	200	250	300

A feeding point A is maintained at 240V & feeding point B at 230V if each conductor has a resistance of $0.01\Omega/100m$. calculate

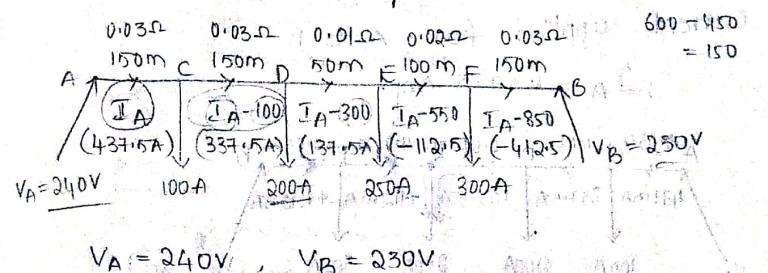- The current supplied from A & B
- The min. voltage & the point at which it occurs
- voltage at each load point.



The total resistance for both (go & return) conductors

$$R = 2 \times 0.01 \Omega / 100m = 2 \times 10^{-4} \Omega / m$$

Resistance at section Ac is

$$R_{AC} = 2 \times 10^{-4} \times 150 = 0.03 \Omega$$

$$R_{CD} = 2 \times 10^{-4} \times 150 = 0.03 \Omega$$

$$R_{DE} = 2 \times 10^{-4} \times 50 = 0.01 \Omega$$

$$R_{EF} = 2 \times 10^{-4} \times 100 = 0.02 \Omega$$

$$R_{FB} = 2 \times 10^{-4} \times 150 = 0.03 \Omega$$

V_D over AB = voltage at A - voltage at B

$$V_A - V_B = I_A \cdot R_{AC} + (I_A - 100) R_{CD} + (I_A - 300) R_{DE} + (I_A - 550)$$

$$REF + (I_A - 850) R_{EB}$$

$$240 - 230 = I_A \times 0.03 + (I_A - 100) 0.03 + (I_A - 300) 0.01 +$$

$$(I_A - 550) 0.02 + (I_A - 850) 0.03$$

$$240 - 230 = 0.03 I_A + 0.03 I_A - 3 + 0.01 I_A - 3 + 0.02 I_A - 11 + 0.03 I_A$$


$$0 = 0.12 I_A - 52.5$$

$$0.12 I_A = 52.5$$

$$I_A = 437.5 \text{ Amps}$$

i) Current supplied from A to B

$$I_A = 437.5 \text{ Amps}$$

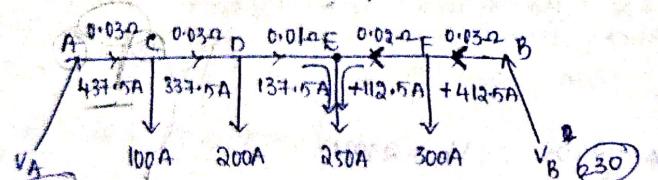

ii) Voltage at point A = 240V

iii) Minimum voltage

$$V_A - V_E = 437.5 \times 0.03 + 337.5 \times 0.03 + 137.5 \times 0.0$$

$$V_E = 240 - 24.625$$

$$V_E = 215.375 \text{ Volts}$$

& E is the min. potential.

iv) Voltage at point A = 240V

voltage at C is

$$V_C = V_A - I_{AC} R_{AC}$$

$$= 240 - (437.5 \times 0.03)$$

13.125

$$V_C = 226.875V$$

$$\begin{aligned} V_D &= V_C - I_{CD} R_{CD} \\ &= 226.87 - (337.5 \times 0.03) \end{aligned}$$


$$V_D = 216.745V$$

$$\begin{aligned} V_E &= V_D - I_{DE} R_{DE} \\ &= 216.74 - (137.5 \times 0.01) \end{aligned}$$

$$V_E = 215.365V$$

$$\begin{aligned} V_F &= V_E - I_{EF} R_{EF} \\ &= 215.365 - (-112.5 \times 0.02) \end{aligned}$$

$$V_F = 217.61V$$

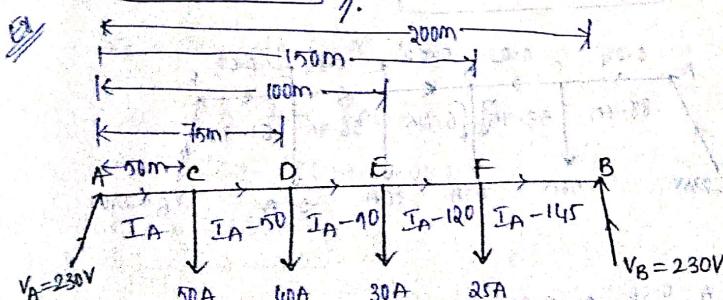

Let the current supplied from feeding point A
is I_A amp.

Resistance of conductor (both go & return)

$$= 0.8 \Omega / \text{km} = 0.8 \times 10^3 \Omega / \text{m}$$

The resistances of sections & currents
flowing are:

<u>section</u>	<u>length</u>	<u>Resistance</u>	<u>current</u>
AC	50	0.04 Ω	I _A
CD	25	0.02 Ω	I _A -50
DE	25	0.02 Ω	I _A -90
EF	50	0.04 Ω	I _A -120
FB	50	0.04 Ω	I _A -145

Voltage drop across AB = voltage at A - voltage at B



$$V_A - V_B = I_A \times 0.04 + (I_A - 50) 0.02 + (I_A - 90) 0.02 + (I_A - 120) 0.04 + (I_A - 145) 0.04$$

$$0 = 0.16 I_A - (1.0 + 1.8 + 4.8 + 5.8)$$

$$0.16 I_A = 13.4$$

$$\boxed{I_A = 83.75 \text{ Amp}}$$

$$\boxed{V_A = 230 \text{ V}}$$

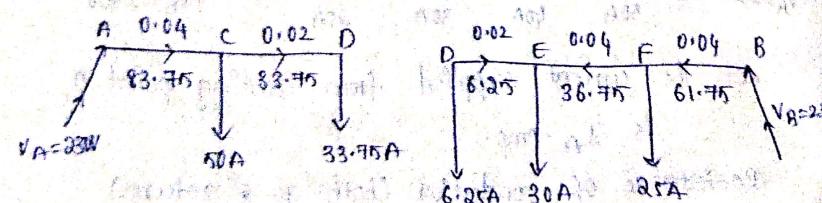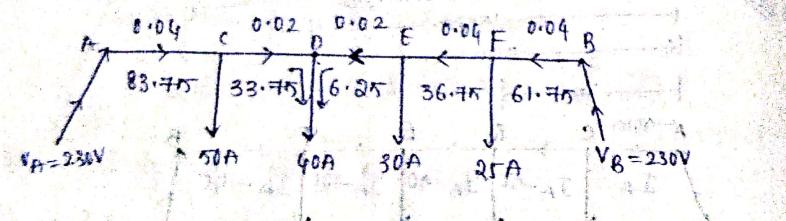

The currents are coming to the load point D from both sides i.e; from point C & point E & Hence
'D' is the point of minimum potential.

From A Minimum consumer voltage,

$$\begin{aligned}
 V_D &= V_A - (V.D \text{ at AC} + V.D \text{ at CD}) \\
 &= 230 - (I_{AC} \cdot R_{AC} + I_{CD} \cdot R_{CD}) \\
 &= 230 - (83.75 \times 0.04 + 33.75 \times 0.02) \\
 &= 230 - (3.35 + 0.675) \\
 V_D &= 225.98V
 \end{aligned}$$

From B

$$\begin{aligned}
 V_D &= V_B - (I_{BF} \cdot R_{BF} + I_{FE} \cdot R_{EF} + I_{ED} \cdot R_{ED}) \\
 &= 230 - (61.75 \times 0.04 + 36.75 \times 0.04 + 6.25 \times 0.02) \\
 &= 230 - (2.47 + 1.47 + 0.125) \\
 V_D &= 225.94V
 \end{aligned}$$


Voltage at point C,

$$\begin{aligned}
 V_C &= V_A - [V.D \text{ at AC}] \\
 &= V_A - I_{AC} \cdot R_{AC} \\
 &= 230 - (83.75 \times 0.04) \\
 V_C &= 226.65V
 \end{aligned}$$

$$\begin{aligned}
 V_F &= V_B - [V.D \text{ at BF}] \\
 &= V_B - I_{BF} \cdot R_{BF} \\
 &= 230 - (61.75 \times 0.04) \\
 V_F &= 227.53V
 \end{aligned}$$

$$\begin{aligned}
 V_E &= V_B - (\text{voltage drop at BE}) \\
 &= V_B - (I_{BF} \cdot R_{BF} + I_{FE} \cdot R_{EF}) \Rightarrow V_E = 226.06V \\
 &= 230 - (61.75 \times 0.04 + 36.75 \times 0.04)
 \end{aligned}$$

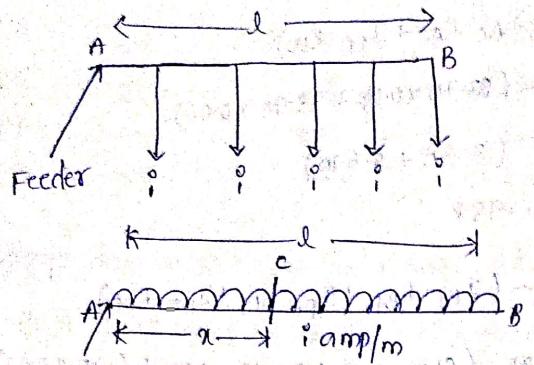Ω/m^2 fed at one end with uniform loading:



Let us consider, a 2-wire dc d/lr AB fed at one-end 'A' and uniformly loaded with ' i ' amp/m length. It means that at every one metre Length of d/lr the load tapped is i amp
Let, length of d/lr = 'l' meters

Resistance of d/lr = $8 \cdot 2 \text{ m run}$ (Both go &

Consider, a point 'c' on the d/lr at a distance 'x' m from feeding point 'A' then, current flowing at point c = Load current supplied over remaining length of d/lr CB.

$$i_c = i(l-x) \text{ amperes}$$

Now, Consider a small length 'dx' near point c its resistance is ' $8 \cdot dx \Omega$ ' & the voltage drop over the length 'dx' is dv

$$v = i(l-x)8$$

$$dv = i(l-x)8 \cdot dx$$

$du = i_r(1-x)dx$
 total voltage drop in the d/r from feeding point A
 upto point 'c'.

$$\begin{aligned} \text{V.D across } AB &= \int_0^x du \\ &= \int_0^x i_r(1-x)dx \end{aligned}$$

$$= i_r \left(lx - \frac{x^2}{2} \right)$$

$$\text{V.D a/c AB} = i_r lx - \frac{x^2}{2}, \text{ i.e.}$$

The V.D upto point 'B' can be obtained by
 letting $x = l$ in above equation.

Voltage drop over the d/r AB, similarly
 upto point AB = $i_r lx - \frac{l^2}{2}$

$$AB = \frac{1}{2} i_r l^2$$

$$= \frac{1}{2} (\pi l) \cdot (li)$$

$$= \frac{1}{2} R \times I$$

$$AB = \frac{1}{2} IR = V$$

where,

$\pi l = R$, the total resistance of the d/r


$il = I$, the total current entering at
 point A.

power loss in element 'dx' at distance

$$x = [i(1-x)]^2 r$$


$$\text{total power loss in d/r} = \int [i(1-x)]^2 r dx$$
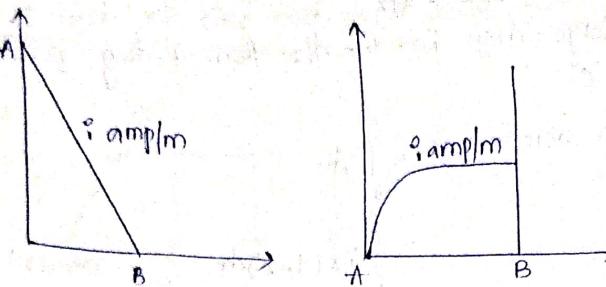
$$(i^2 - (il)^2) \boxed{AB = i^2 \pi l^3 / 3}$$



current in various sections voltage drop in various sections

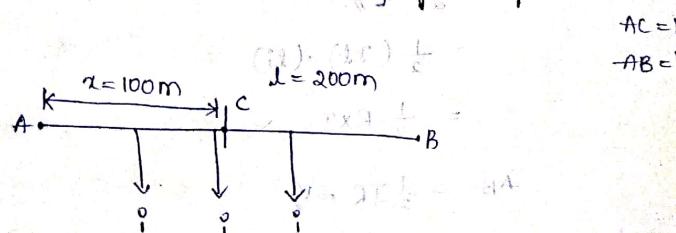- Q. A 2-wire DC dl/r 200m long is uniformly loaded with 2 amp/m. Resistance of single wire is 0.2 Ω/km, if the dl/r fed at one end. calculate : 1. The voltage drop upto a distance of 100 m from the feeding point. 2. The max. voltage drop.



$$\text{Resistance } R = 0.2 \Omega/\text{km}$$

$$\text{Both (go & return)} = r = 0.2 \times 2$$

$$r = 0.4 \times 10^{-3} \Omega$$

$$i = 2 \text{ A/m (load current)}$$

$$\text{i) Voltage drop across } [AC] \text{ is } ir \left(l x - \frac{x^2}{2} \right)$$

$$\text{at } C \text{ is } = \frac{1}{2} \left(lx - \frac{x^2}{2} \right) \text{ if load removed}$$

$$= 2 \times 0.4 \times 10^{-3} \left(200(100) - \frac{(100)^2}{2} \right)$$

$$= 8 \times 10^{-4} \left(20,000 - \frac{(100)^2}{2} \right)$$

$$= 8 \times 10^{-4} (20,000 - \frac{100 \times 100}{2})$$

$$\Delta V = 1.2 \text{ V}$$

ii) Total current entering the d/lz

$$I = i_x l = 2 \times 200 = 400 \text{ A}$$

$$R = r \times l = 0.0004 \times 200 = 0.08 \Omega$$

Total drop over the d/lz = $\frac{1}{2} IR$


$$29/10/22 \quad \Delta V = \frac{1}{2} \times 400 \times 0.08 = 16 \text{ V}$$

d/lz fed at Both sides ends with uniform loading:

The d/lz is classified into 2 ways depending on feeder points:

1. with equal voltages

2. with un-equal voltages

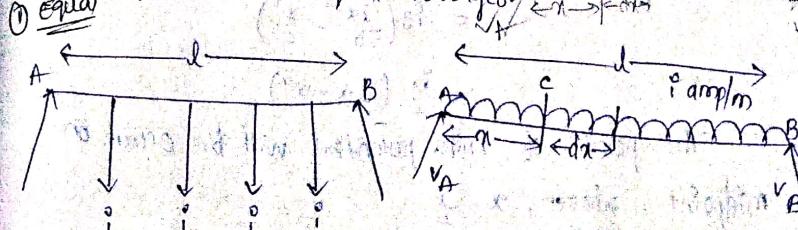

consider, a d/lz AB of length 'l' meters, having resistances $r = 2 \Omega/\text{m run}$ (both go & return conductors).

with uniform loading of $i = 1 \text{ amp}/\text{m run}$.

Let the dl s fed at feeding point A & B
at equal voltages with 'V' volts.

Total current supplied to $dl \Rightarrow i_l = I$

As end voltages are equal the current supplied
from each feeding point $= \frac{i_l}{2}$.

Consider, a point 'c' at the distance 'x' m from
feeding point A.

The current flowing at point C $= \frac{i_l}{2} - ix$

$$I_C = i\left(\frac{l}{2} - x\right)$$

Now, consider small length dx from point 'C' its
resistance is ' $r \cdot dx$ ', voltage drop over the length
 dx is $dr = i(1/2 - x)r \cdot dx$

$$= ir\left(\frac{1}{2} - x\right)dx$$

$$\begin{aligned}\text{Voltage drop upto point } C = AB &= \int dr\left(\frac{1}{2} - x\right)dx \\ &= ir\left(\frac{1}{2} - \frac{x^2}{2}\right) \\ &\quad \left.\begin{array}{l} \downarrow \\ \frac{\partial r}{\partial x} (1x - x^2) \end{array}\right.\end{aligned}$$

The point of min. potential will be occurs on
midpoint where, $x = \frac{l}{2}$

Sub. $x = \frac{l}{2}$ in above eqn.

$$\begin{aligned}V.D. \text{ at } AB &= \frac{ir}{2} \left(l \cdot \frac{1}{2} - \left(\frac{l}{2} \right)^2 \right) \\ &= \frac{ir}{2} \left(\frac{l}{2} - \frac{l^2}{4} \right) \\ &= \frac{ir}{2} \left(\frac{l^2}{4} \right) = \frac{ir l^2}{8} = \frac{1}{8} (i)(r)l = \frac{1}{8} IR\end{aligned}$$

$$V.D \text{ at } AB = \frac{1}{8} iR$$

where, $i_l = \frac{i}{2}$, The total current fed to d/π from both ends.

$r_l = R$, The total resistance of the d/π .

$$\text{The min. voltage} = V - \frac{iR}{8}$$

$$\text{power loss in a } d/\pi \text{ element, } dR = \frac{iR}{8}$$

$$dx = \frac{R}{2}$$



$$= \left[i \left(\frac{1}{2} - x \right) \right]^2 \cdot \frac{R}{2} dx$$

Total power loss in a d/π ,

$$P = \int_0^l dp$$


$$= \int_0^l \left[i \left(\frac{1}{2} - x \right) \right]^2 \cdot \frac{R}{2} dx$$

$$P = \frac{1}{12} i^2 r_l^2 l$$

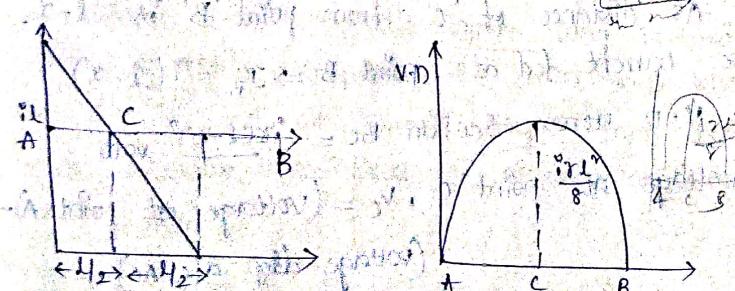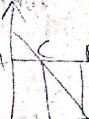

Current in various sections

Voltage drop in various sections.

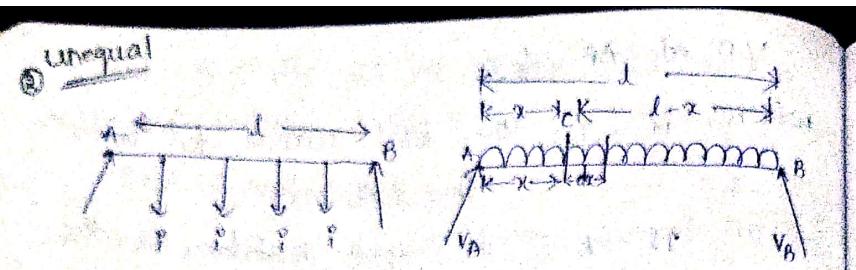

Consider, a d/l₂ AB of length 'l' m having resistance of ' r ' Ω /m run (Both go & return conductor) with uniform loading of 'i' amp/m run.

Let the d/l₂ fed from A & B at v_A & v_B respectively.

Suppose the point of min. potential 'C' situated (located) at the distance of 'x' m from point A.

The current supplied by feeding point, $I_A = i \cdot x$

Voltage drop at section AC,

$$AC = \frac{i \cdot x^2}{2} \text{ volts}$$

As distance of 'C' from point 'B' is " $l-x$ ".

The current fed at point B $\Rightarrow I_B = i(l-x)$

V.D across section BC = $\frac{i \cdot x(l-x)}{2}$ volts

Voltage at point C, $v_C = (\text{voltage at point A}) - (\text{voltage drop at C AC})$

$$v_C = v_A - \frac{i \cdot x^2}{2} \rightarrow ①$$

Voltage at point C, $v_C = (v_A \text{ at } B - v_A \text{ at BC})$

$$v_C = v_B - \frac{i \cdot x(l-x)}{2} \rightarrow ②$$

from ① & ②

$$V_A - \frac{\pi r x^2}{2} = V_B - \frac{\pi r (1-x)^2}{2}$$

$$V_A - V_B = \frac{\pi r x^2}{2} - \frac{\pi r (1-x)^2}{2}$$

$$= \frac{\pi r}{2} [x^2 - (1-x)^2]$$

$$= \frac{\pi r}{2} [x^2 - (1 - x^2 + 2x)]$$

$$= \frac{\pi r}{2} [-2x + 1]$$

$$= \frac{\pi r l}{2} [-2x + 1] \quad \text{where } V_B = \frac{V_A + V_B}{2}$$

$$\therefore \frac{V_A - V_B}{l} = \frac{\pi r}{2}$$

All the quantities V_A, V_B, π, r, l are the known quantities.

∴ The point on the d/r where min. potential occurs can be calculated by using 'x' formulae.

Q: A uniform ϱ -wire d.c d/r 200m long is loaded with 2 amp/m. calculate the more V.D when the d/r is fed at equal $\frac{IR}{AB}$ voltage's from both ends. Assume resistance of single wire is 0.5 Ω /km

Given, length of d/r $l = 200\text{ m}$

current $i = 2 \text{ amp/m}$

$$\varrho = 0.5 \times 2 \Omega/\text{km}$$

$$\varrho = 1 \times 10^{-3} \Omega/\text{m}$$

$$0.001 \Omega/\text{m}$$

The max. V.D at AB = $\frac{1}{8} IR$

$$= \frac{1}{8} (1)(71)$$

$$= \frac{1}{8} (0.2 \times 100) (1 \times 10^3 \times 200)$$

$$V.D \text{ at } AB = 10 \text{ volts},$$

A 600m d.l.r fed from both ends A & B is loaded uniformly at the rate of 1 amp/m run, the resistance of each conductor being $0.05 \Omega/\text{km}$. The d.l.r. is fed at both ends A & B at 235V & 230V respectively.

Determine: 1. The min. voltage & the point where it occurs.

2. The current supplied from feeding point P-A & B.


Given, $v_A = 235V$

$v_B = 230V$

$l = 600\text{m}$

$i = 1\text{amp/m}$ (as per question)

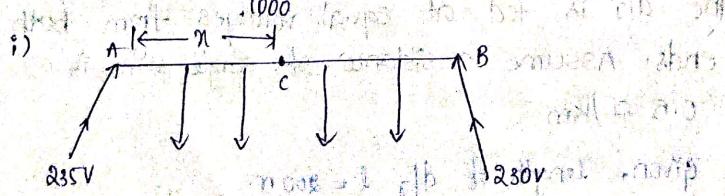$r = 0.05 \times 2 = 1 \times 10^{-4} \text{ ohm m} = 0.0012\text{/m}$



det, the min. potential occur at point c distant 'x' m from the f. point A.

$$x = \frac{V_A - V_B}{i_R l} + \frac{l}{2}$$

$$= \frac{235 - 230}{1 \times 0.0001 \times 600} + \frac{600}{2}$$

$$= 83.3 + 300$$

$$\boxed{x = 383 \text{ m}}$$

i.e; minimum potential occurs at 383 m from point A.

$$\text{min. voltage, } V_C = V_A - \frac{i_R x^r}{2}$$

$$= 235 - \frac{1 \times 0.0001 \times (383)^2}{2} - 14.6689$$

$$= 235 - 4.3$$

$$V_C = 227.7 \text{ V} \approx 228 \text{ V}$$


ii) current supplied from A

$$= i_R = 1 \times 383 = 383 \text{ A}$$

current supplied from B

$$= i(l-x) = 1 \times (600-383)$$

$$= 217 \text{ A}$$

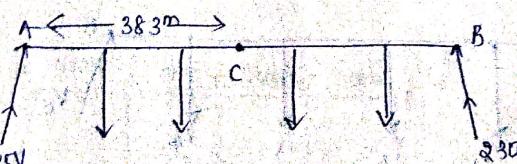

DC d/c with both C.L & U.L:-

1. concentrated loading

2. uniform loading


D.C is fed with

1. At one end
2. At Both ends
 - a) with equal voltages
 - b) with un-equal voltages.


Procedure:

The given C.L & V.L on d.c d.l.r are independently & the voltage drops b/w feeding point A & B are calculated separately.

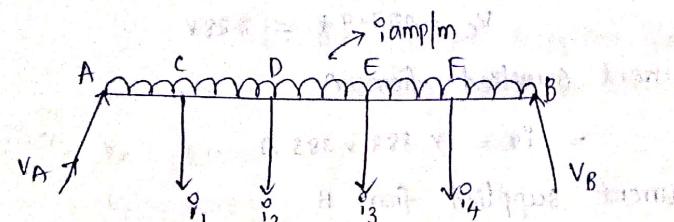
Resultant V.D due to both C.L & V.L is equal to V.D due to C.L + V.D due to V.L



a) D.c d.l.r fed both C.L & V.L

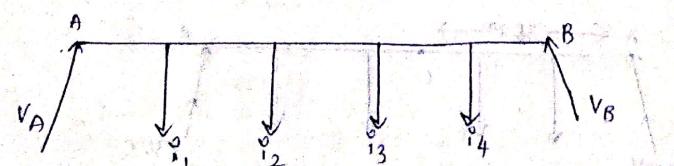

b) D.l.r fed at only C.L

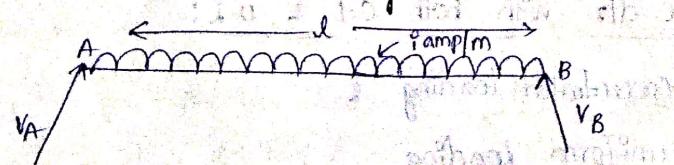

c) D.l.r fed at only V.L

Procedure:

Dc d/lr fed at one-end with c.l & v.l.
consider, a d/lr having length 'l' m and let us consider
a point 'x' from distance of 'x' m & current
flowing through the d/lr is 'i' amp/m

$$V.D \text{ from point } x = \int_0^x [I - ix] r \cdot dx$$

$$= \left[Ix - \frac{ix^2}{2} \right] r$$


$$= \left[Ix - \frac{i^2 x^2}{2} \right] x \cdot r$$

$$\boxed{x = l}$$

$$V.D \text{ in length } l = \left(I - \frac{il^2}{2} \right) l \cdot r$$

Q. A 2-wire dc d/lr is supplying loads are 50A, 100A, 200A, & 150A located at 500m, 900m, 1700m & 2000m respectively from fig. A.

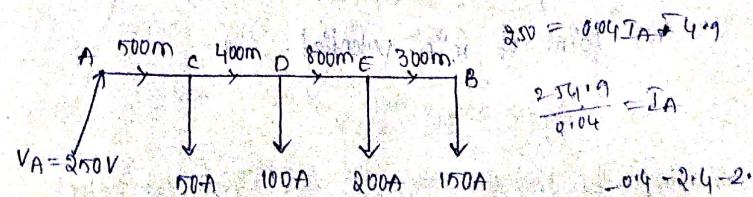The resistance of each conductor is 0.01 Ω/km
the potential diff. at f.p is 250V. Find the p.d at
each load point.



$$r = 0.01 \Omega/\text{km} = \frac{0.01}{1000} \times 2 \quad (\text{Both go & return})$$

$$r = 2 \times 10^{-5} \Omega/\text{m}$$

$$V_A - V_B = I_A \times 0.01 + (I_A - 50) \times 0.008 + (I_A - 150) \times 0.016 \\ + (I_A - 350) \times 0.006$$

$$250 = 0.01 I_A + 0.008 I_A - 50 \times 0.008 + 0.016 I_A - 150 \times 0.016 \\ + 0.006 I_A - 350 \times 0.006$$


$$250 = 0.04 I_A + (-0.4 - 2.4 - 2.1)$$

$$250 = 0.04 I_A - 4.9$$

$$254.9 = 0.04 I_A$$

$$\boxed{I_A = 122.5 A}$$

Q. Slope test

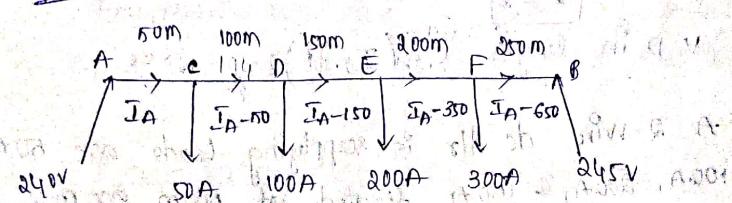

$$r = \text{for single conductor} = 0.15 \Omega/km$$

i) V.D at d/r ✓

ii) I at each loads ✓

iii) voltage at each load ✓

iv) point of min. potential ✓

$$V_A = 240V, V_B = 245V$$

$$r = 0.15 \Omega/km \quad (\text{for single conductor})$$

$$\text{for both (go & return)} r = 0.5 \times 10^{-3} \Omega/m \Rightarrow 1 \times 10^{-3}$$

\Rightarrow Resistance at section AC

$$R_{AC} = 1 \times 10^{-3} \times 50 = 0.05 \Omega$$

$$R_{CD} = 1 \times 10^{-3} \times 100 = 0.1 \Omega$$

$$K_{DE} = 1 \times 10^{-3} \times 150 = 0.15 \Omega$$

$$R_{EF} = 1 \times 10^{-3} \times 200 = 0.2 \Omega$$

$$R_{FB} = 1 \times 10^{-3} \times 250 = 0.25 \Omega$$

$$V_D \text{ over } AB = V_A - V_B$$

$$V_A - V_B = I_A \cdot R_{AC} + (I_A - 50) R_{CD} + (I_A - 150) R_{DE} + (I_A - 350)$$

$$R_{EF} + (I_A - 650) R_{FB}$$

$$240 - 245 = I_A \cdot 0.05 + (I_A - 50) 0.1 + (I_A - 150) 0.15 +$$

$$(I_A - 350) 0.2 + (I_A - 650) 0.25$$

$$= 0.05 I_A + 0.1 I_A - 5 + 0.15 I_A - 22.5 + 0.2 I_A$$

$$- 70 + 0.25 I_A - 162.5$$

$$- 5 = 0.75 I_A - 260$$

$$255 = 0.75 I_A$$

$$\boxed{I_A = 340 \text{ A}}$$


$$\text{ii) } I_A = 340 \text{ A}$$

$$I_A - 350 = -10 \text{ A}$$

$$I_A - 50 = 290 \text{ A}$$

$$I_A - 650 = -310 \text{ A}$$

$$I_A - 150 = 190 \text{ A}$$

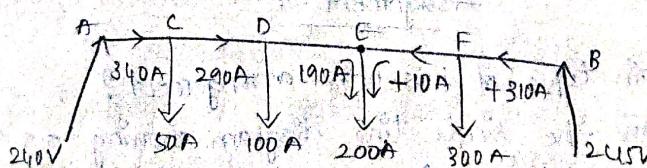

E is the minimum point of potential.

$$\text{iii) Voltage at A} = 240 \text{ V}$$

Voltage at C is

$$V_C = V_A - I_A R_{AC}$$

$$= 240 - 340(0.05)$$

$$V_D = V_C - I_{CD} R_{CD}$$

$$= 223 - 290(0.1)$$

$$\boxed{V_D = 194 \text{ V}}$$

$$V_E = V_D - I_{DE} R_{DE}$$

$$= 194 - 190(0.15)$$

$$\boxed{V_E = 165.5 \text{ V}}$$

$$V_F = V_E - I_{EF} R_{EF}$$

$$= 165.5 - (-10)(0.2)$$

$$\boxed{V_F = 167.5 \text{ V}}$$

9) V.D at d/r AB = $V_A + V_B + V_C + V_D + V_E + V_F$

$$= 240 + 245 + 223 + 194 + 165.5 + 167.5$$

$$= 1235 \text{ V}$$

Assignment - 4

1. Explain types of bus-bars arrangement?
2. Draw the single line diagram showing s.s appara.
3. Explain classification of s.s depends on service requirement & constructional features?

Assign - 5

1. Improving methods of p.F?
2. Most economical p.F?
3. Methods of voltage control?

UNIT-3

AC DISTRIBUTION SYSTEMS

generating station:

In generating station electric power is produced by 3- ϕ alternators operating in parallel. Normally, the generation voltage is 11kv (33/66kv in some cases).

primary transmission:

The electric power at 132 kv is supplied to other s/m by 3- ϕ , 3 wire overhead lines. The 11kv voltage is stepped up upto 132 kv, 66kv, 220kv (or 400 kv).

secondary transmission:

The primary t/m line terminates the receiving station where, the voltage is reduced to 33kv by step down transformers.

primary distribution:

The secondary t/m line terminates at substation where voltage is reduced from 33kv to 11kv.

secondary distribution:

The electric power available at 11kv from primary d/s line is delivered to d/s substations which step down the voltages to 400v (or 230v).

* The secondary d/s s/m consists of feeders, d/s's and service mains.

Feeders:

These are line conductors which connects the substation to d/lr lines.

Distributors:

These are the conductors from which various tappings for the supply to the consumers are taken.

Service Mains:

These are the conductors which connects the consumer terminals to the d/lr's.

Requirements and design features of primary feeder:

a) Factors affecting selection of primary feeder rating:

There are various and yet interrelated factors affecting the selection of a primary - feeder rating.


Examples are:

1. The nature of the load connected.
2. The load density of the area served.
3. The growth rate of the load.
4. The need for providing spare capacity for emergency operations.
5. The type and cost of circuit construction employed.
6. The design and capacity of the substation involved.
7. The type of regulating equipment used.

- a) The quality of service required.
 - b) The continuity of service required.
- b) Improvement in voltage conditions on primary feeders:

By using shunt capacitors we are improving the voltage of primary feeders.

Radial - Type primary Feeder:

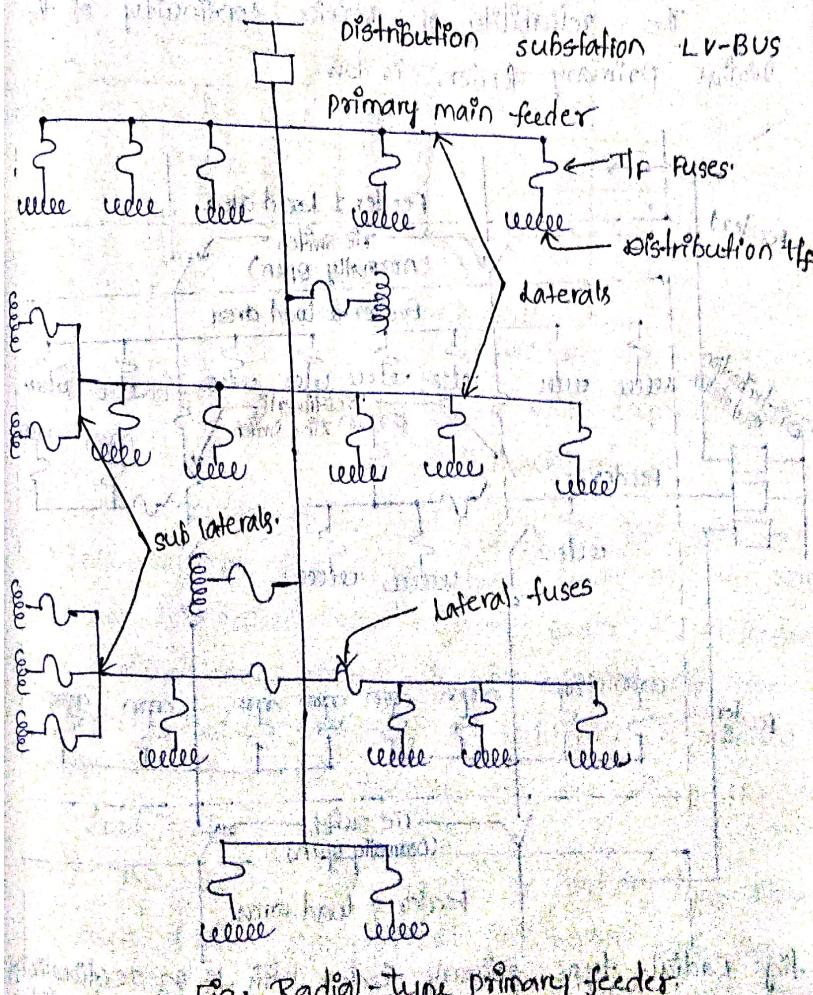

Ex. Radial-type primary feeder.

The main primary feeder branches into various primary laterals, which in turn separates into several sublaterals to serve all the dls-transformers.

In general, the main feeder & subfeeders are 3-φ, three con 4-wire ckt's & the laterals are 3 on 1-φ. The current magnitude is the greatest in the ckt conductors that leave the substation.

The reliability of service continuity of the radial primary feeders is low.

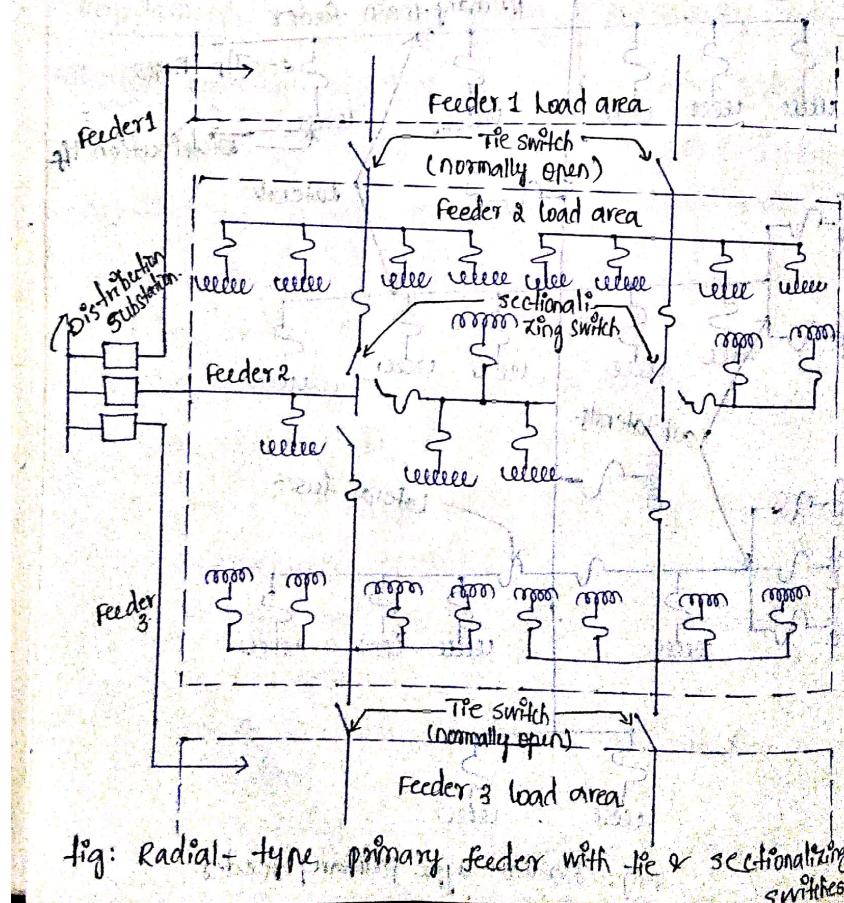


fig: Radial-type primary feeder with tie & sectionalizing switches

→ To provide fast restoration of service to customers by switching unfaulted sections of the feeder to an adjacent primary feeder or feeders. The fault can be isolated by opening the associated disconnecting devices on each side of the faulted section.


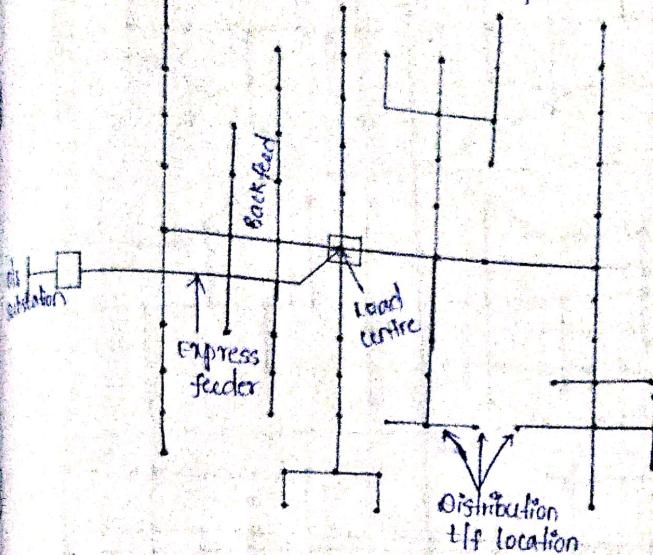



fig: Radial-type primary feeder with express feeder & backfeed.


⇒ The section of the feeder b/n the substation low-voltage bus & the load centre of the service area is called as express feeder. No subfeeders
(a) Laterals are allowed to be tapped off the 'express feeder'. However, a subfeeder is allowed to provide a backfeed toward the s.s. from the load center.

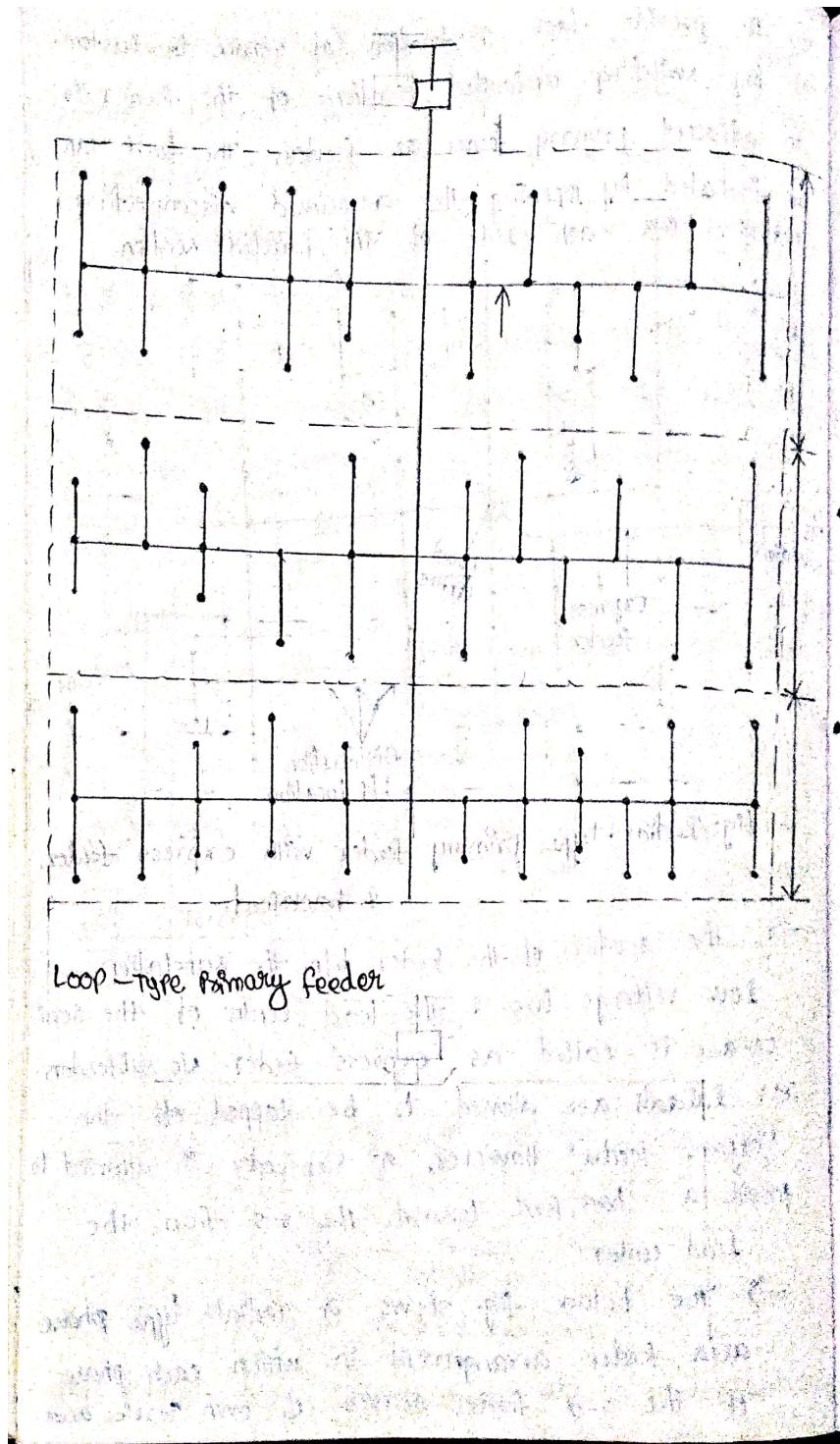⇒ The below fig. shows a radial-type phase area feeder arrangement in which each phase of the 3- ϕ feeder serves its own service area.




Loop-type primary feeder

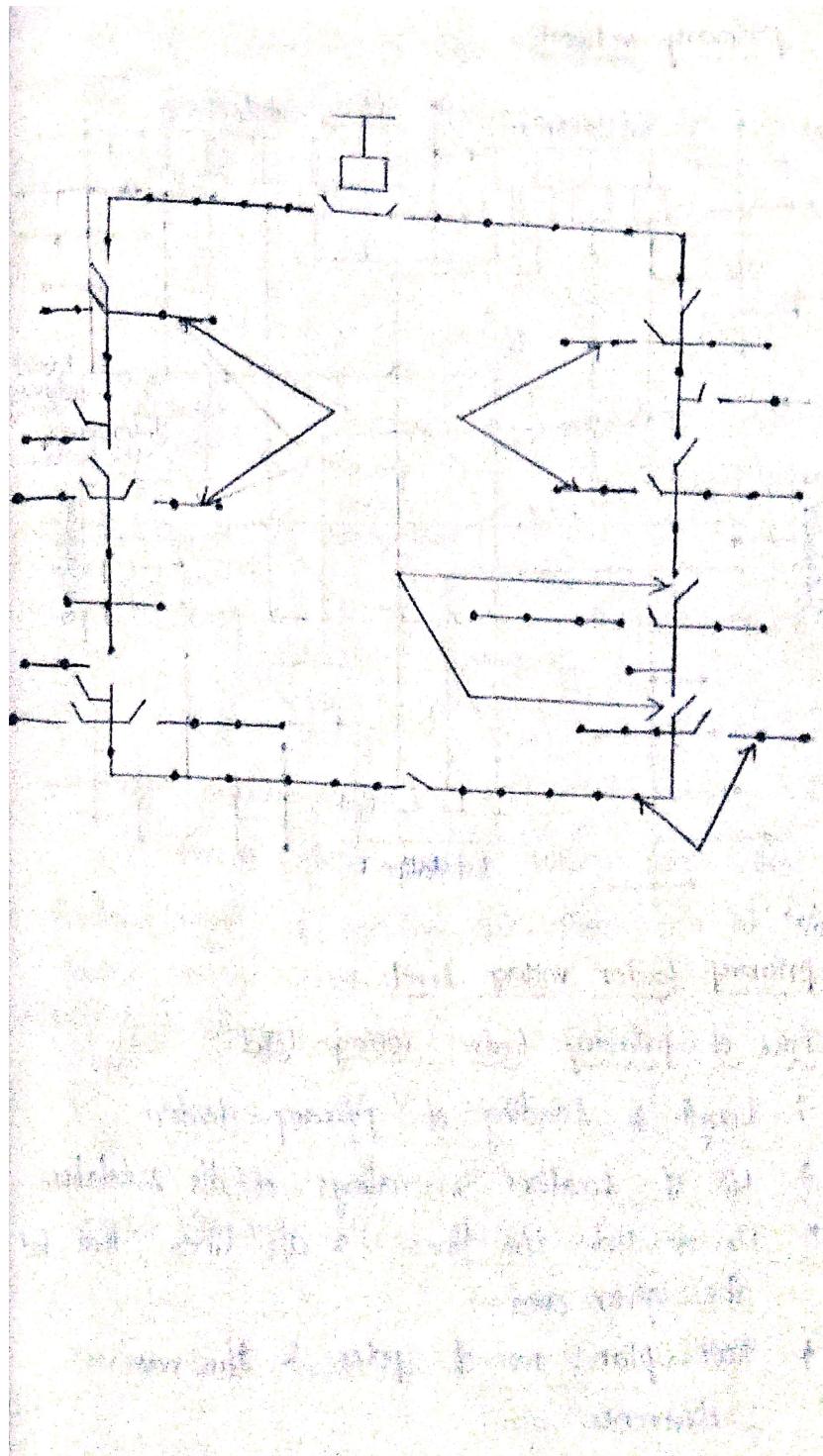

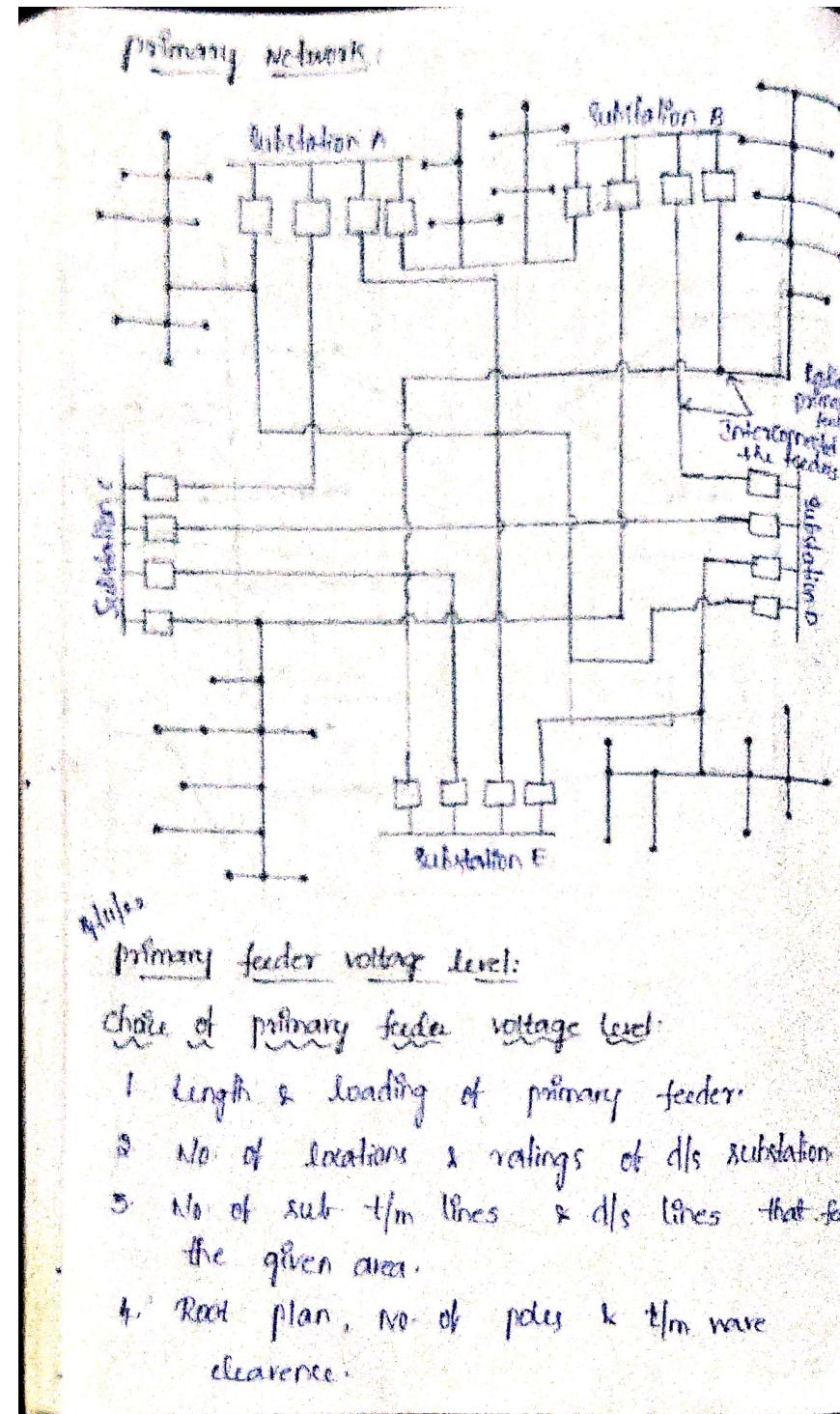

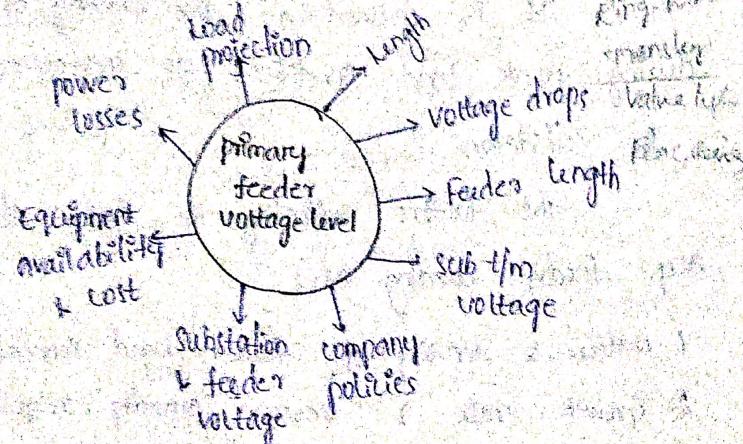5. No. of customers & their importance
 6. The additional factors for primary feeder voltage level are



Voltage square rule:

For a given percent voltage drop the feeder length & loading are direct functions of feeder voltage level.

Voltage-square factor rule:

$$V.S \text{ factor} = \left(\frac{V_L - N \text{ New}}{V_L - N \text{ Old}} \right)^2$$

$$\text{Feeder distance ratio} = \frac{\text{Feeder New distance}}{\text{Feeder old distance}}$$

$$\text{Feeder load ratio} = \frac{\text{Feeder New loading}}{\text{Feeder old loading}}$$

Feeder service area coverage principle:

$$\text{Feeder service area} \propto \left[\left(\frac{V_{L-N} \text{ new}}{V_{L-N} \text{ old}} \right)^r \right]^{2/3}$$

26-11-22

Primary feeder loading:

It is defined as the loading of feeder during peak load conditions as measured at the substation.

The factors affecting the design of primary feeder loading are:


1. Nature & density of feeder load connected.
2. Growth rate & reserve capacity requirement for emergency.
3. Continuity, reliability ^{the efficiency & values} & quality of service.
4. Primary feeder voltage level & regulation requirements. (based on specifications)
5. Location & capacity of the d/s substation.
6. Type of cost of construction & operating cost.
7. Alternate supply provisions made.

Additional factors affecting design of feeder:


1. Feeder routing decisions.
2. No. of feeders.

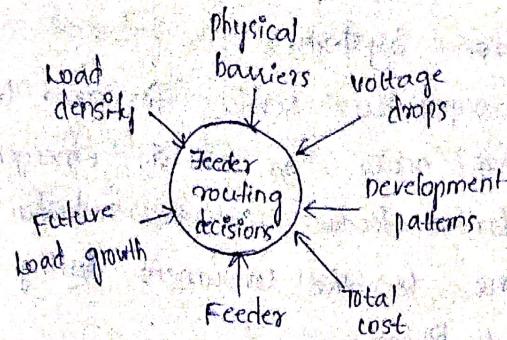3. conductor size selection.


factors affecting feeder routing decisions:



factors affecting no. of feeders:

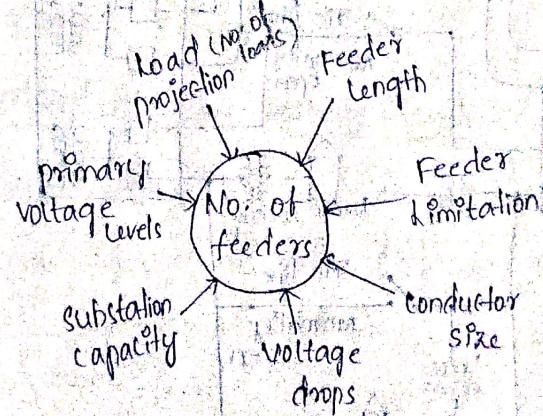

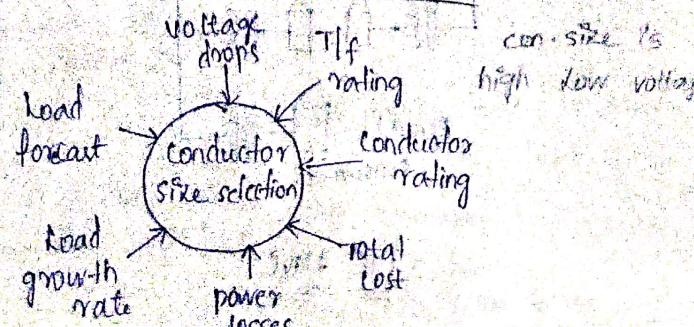
factors affecting conductor size selection:



Tie Line:

It is a line that connects a supply system to that provides emergency service to one system from another system.

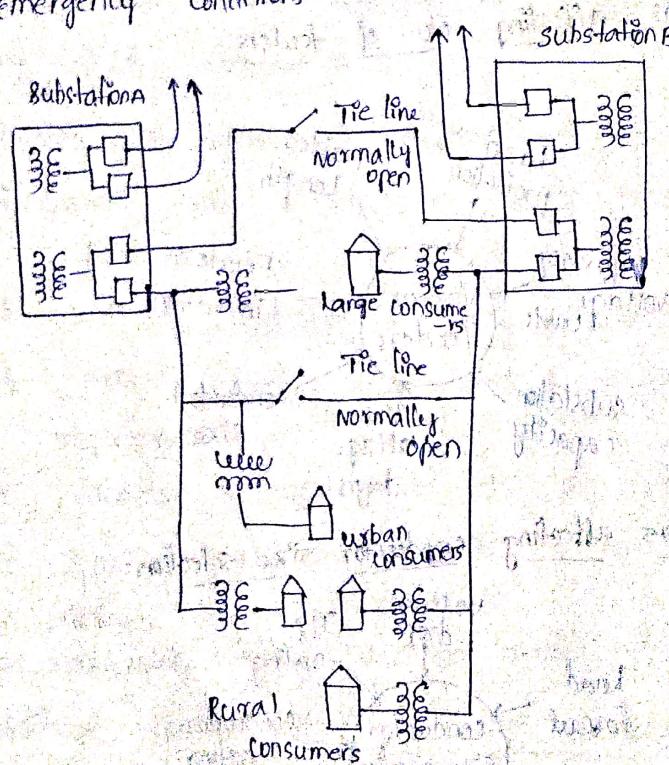- * A tie line provides service for area loads along with routes as well as emergency service for a feeder for the reduction of outage time to the consumers during emergency conditions.



TIE LINES

secondary dls system


which is connected b/w the primary system & consumer is called secondary dls system.

The secondary dls feeds the electrical energy to consumers depending on no. of consumers and area, load requirements.

- This includes:
1. step down dls eff's
 2. consumer services (service mains)
 3. secondary ckts
 4. Energy meters to measure consumer energy conversion.

secondary dls s/m voltage levels

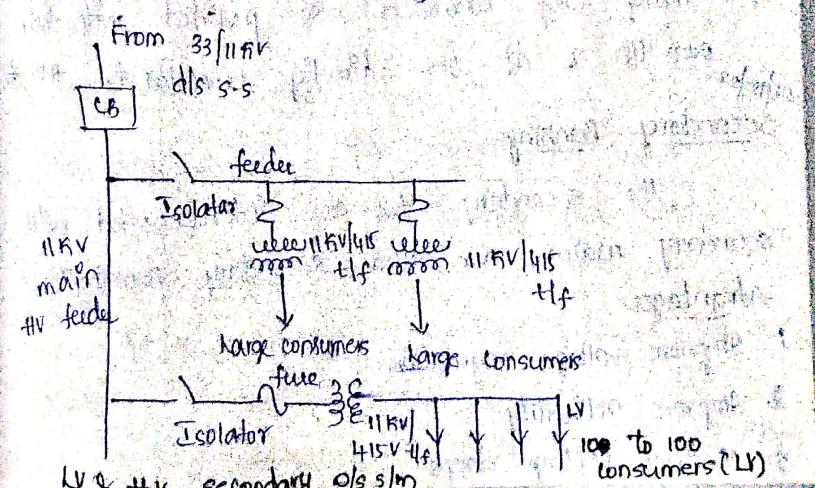1. High voltage dls s/m (11 KV, 33 KV, 66 KV)
2. Low voltage dls s/m (400 - 450 V, 3- ϕ , 230 - 240, 1- ϕ s/m).



Requirements of Secondary distribution system:

1. Most economic size & combination of line networks along t/f's and service mains.
2. Min. ckt length, voltage drop & power losses
3. Easy route location & maintenance
4. To provide possibility of easy t/f management

Design practices of secondary dls s/m:


1. Individual consumers is provided separate service connection.
2. A group consumers [like domestic supply, commercial load, small industries] are supplied from a t/f ss
3. Large Consumers with loads of 25 KVA and more (Flats in cities, residential building, hospitals, medium size commercial buildings) provided with their own t/f.
4. Heavy large consumers also provided with their own t/f & dls s.s directly connected to the all

Secondary Banking:


The secondary n/w are interconnected with secondary mains are called "Secondary Banking".

Advantages:

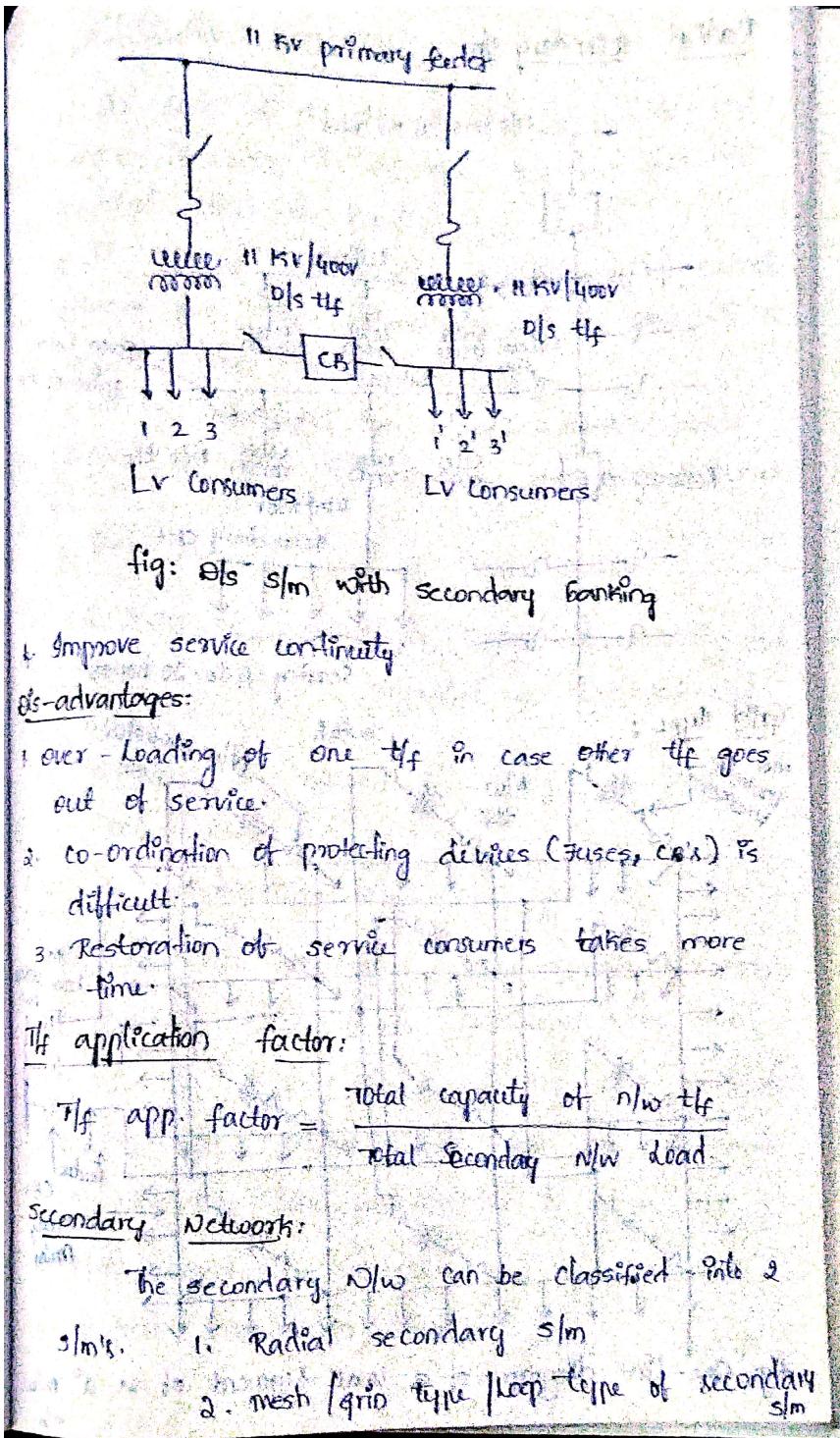1. Improve voltage regulation.
2. Improve reliability
3. Reduce voltage drops.



Radial secondary s/m:

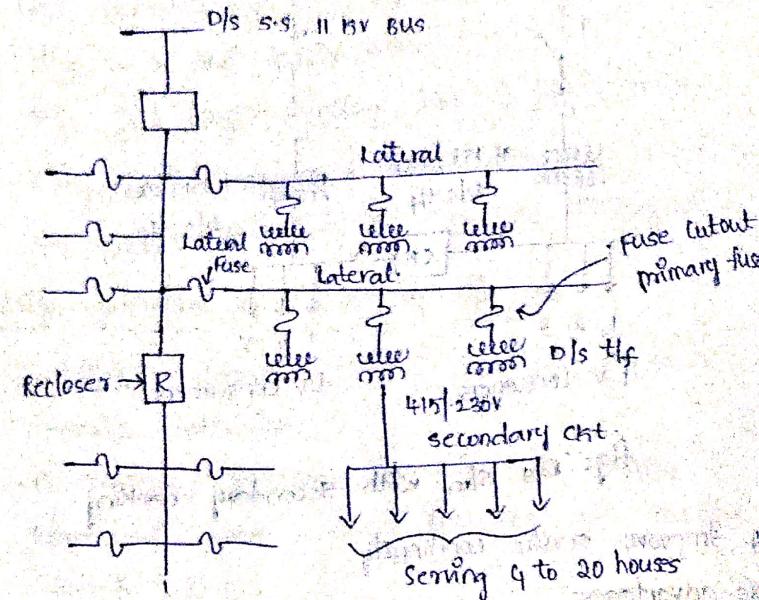

Grid type:

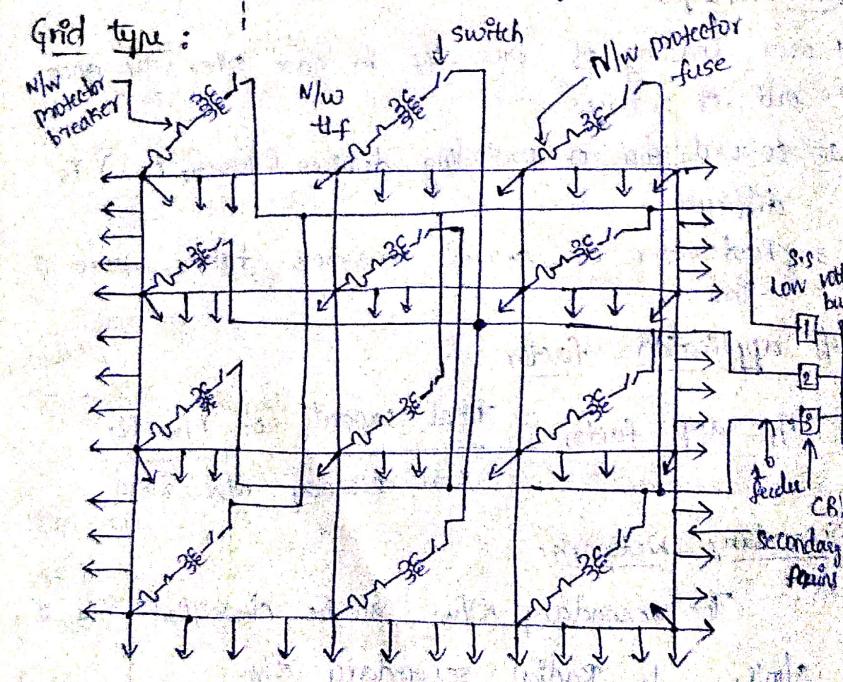


fig: One-line diagrams of a small segment. of a 2° N/w s/m


AC distribution calculations:

1. In case of dc s/m the V.D is due to resist alone. However, in ac s/m the V.D are due combined effect of R,L,C.
2. In dc s/m additions or subtractions of currents voltages are done arithmetically but in case of ac the operations are done vectorially.
3. In ac s/m p.F has to be taken, loads are tapped off from the d/lr are generally different if k.
4. there are 2 types of power factors:
 - a) It may be referred to supply or receiving end voltage, which is regarded as the reference vector.
 - b) It may be referred to voltage at load point itself.

1- ϕ AC distribution s/m:

In ac d/l's calculations p.F of various (vectors) load currents have to be considered since the currents in diff sections of d/lr will be vector sum of load currents and not the arithmetic sum, the p.F load currents can be given by:

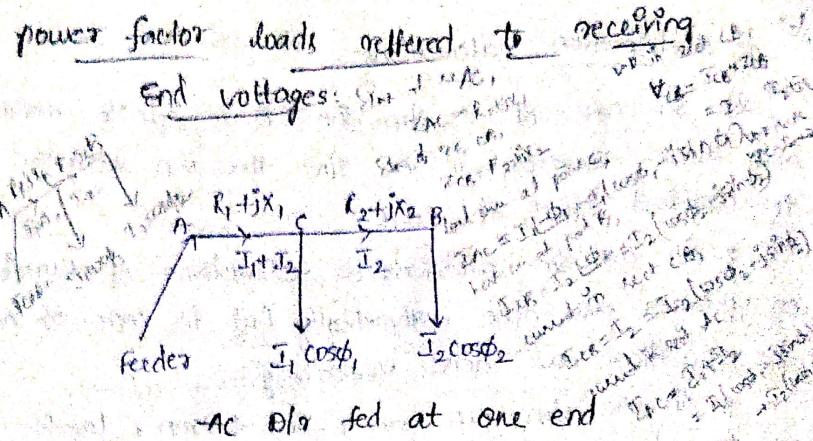1. with respect to receiving end voltage
2. w.r.t. load voltage itself.



Consider, AC d/l with conc. loads of I_1 & I_2 tapped off at point C & B taking a receiving end voltage V_B as the reference voltage.

Let the p.F of load points C & B, be $\cos\phi_1$ & $\cos\phi_2$ lagging (w.r.t. V_B)

Let R_1, X_1 & R_2, X_2 be the resistance & reactance of sections AC & CB of d/l.

Impedance of section AC, $Z_{AC} \Rightarrow$

$$Z_{AC} = R_1 + jX_1$$

Impedance of section CB,

$$Z_{CB} = R_2 + jX_2$$

Load current at point C, $I_{AC} = I_1 (\underline{-\phi_1})$

$$I_{AC} = I_1 (\underline{-\phi_1}) = I_1 (\cos\phi_1 - j\sin\phi_1)$$

Load current at point B,

$$I_{CB} = I_2 (\underline{-\phi_2}) = I_2 (\cos\phi_2 - j\sin\phi_2)$$

Current in section CB,

$$I_{CB} = I_2 = I_2 (\cos\phi_2 - j\sin\phi_2)$$

current in section AC.

$$I_{AC} = I_1 + I_2$$

$$= I_1 (\cos\phi_1 - j\sin\phi_1) + I_2 (\cos\phi_2 - j\sin\phi_2)$$

V.D in section CB,

$$V_{CB} = I_{CB} \times Z_{CB}$$

$$= I_2 (\cos\phi_2 - j\sin\phi_2) \times R_2 + jX_2$$

V.D in section AC,

$$V_{AC} = Z_{AC} \times I_{AC}$$

$$= I_1 (\cos\phi_1 - j\sin\phi_1) (R_1 + jX_1)$$

$V_A = V_B + V_{AC} + V_{CB}$
Reference voltage


The sending end voltage $V_A = V_B + V_{AC} + V_{CB}$

where, V_B - Reference voltage & same

\Rightarrow sending End current $I_{AC} = I_1 + I_2$

$$= I_1 (\cos\phi_1 - j\sin\phi_1) +$$


$$I_2 (\cos\phi_2 - j\sin\phi_2)$$

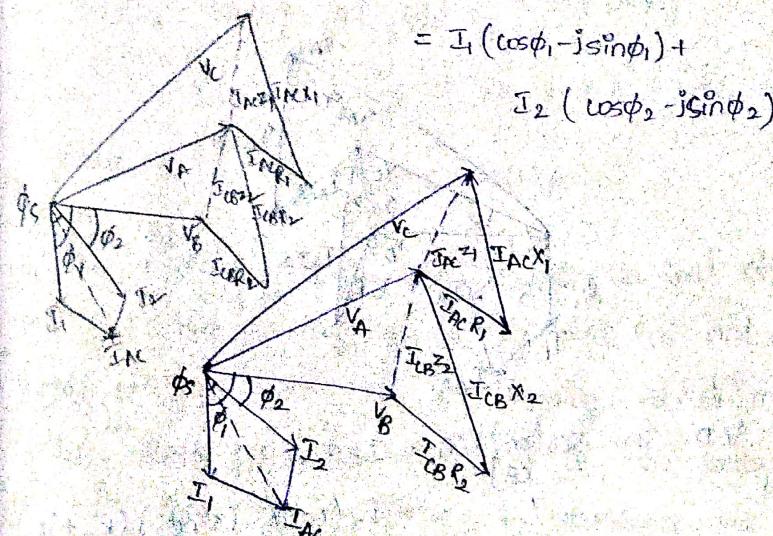


Hence, the p.f of loads are given the reference

voltage w.r.t to V_B . & I_1, I_2 lag behind V_B with
 $\cos\phi_1$ & $\cos\phi_2$ respectively.
 3/10/22

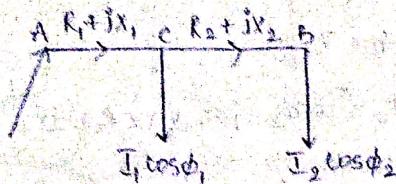power factor loads referred to respective load
 voltage:



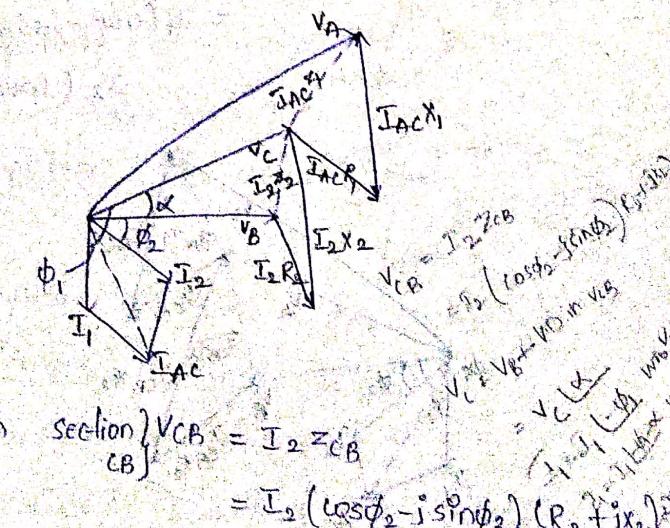Consider, a delta AB with conc. loading of
 I_1 & I_2 tapped off at point C & B. suppose the
 P.F. of loads are referred to their respective
 load voltages then ϕ_1 is the phase-angle b/w
 V_C & I_1 and ϕ_2 is the phase-angle b/w V_B & I_1



$$\begin{aligned} \text{V.D in section CB} \quad V_{CB} &= I_2 Z_{CB} \\ &= I_2 (\cos\phi_2 - j \sin\phi_2) (R_2 + jX_2) \end{aligned}$$

Voltage at point C,

$$V_C = \text{Voltage at } B + V.D \text{ in section CB}$$

$$= V_B + V.D \text{ in CB}$$

$$= V_C (\underline{\alpha})$$

$$I_1 = I_1 (\underline{-\phi_1}) \text{ w.r.t } V_C$$

$$I_1 = I_1 (\underline{-\phi_1 - \alpha}) \text{ w.r.t } V_B$$

$$I_1 = I_1 [\cos(\phi_1 - \alpha) - j \sin(\phi_1 - \alpha)]$$

current in section AC,

$$I_{AC} = I_1 + I_2$$

$$= I_1 [\cos(\phi_1 - \alpha) - j \sin(\phi_1 - \alpha)] +$$

$$\text{voltage drop in section AC, } I_2 (\cos \phi_2 - j \sin \phi_2)$$

$$V_{AC} = I_A \cdot Z_{AC}$$

$$= I_1 [\cos(\phi_1 - \alpha) - j \sin(\phi_1 - \alpha)] (R_1 + jX_1)$$

$$\text{Finally, voltage at point A, } I_2 (\cos \phi_2 - j \sin \phi_2)$$

$$V_A = V_B + V.D \text{ in CB} + V.D \text{ in AC}$$

where, V_B is the reference voltage


problem:

Q1. A $1-\phi$ d/c 2 km long supplies a load of 100A at 0.8 PF lagging at its far end and a load of 80A at 0.9 PF lagging at its mid point. Both P.F.'s are referred to the voltage at far end. The resistance & reactance per km (both go & return) are 0.05Ω & 0.1Ω respectively. If the voltage at far end is

Maintained at 230V - calculate :

- voltage at sending end.
- phase-angle b/w voltages at two ends.

Given,

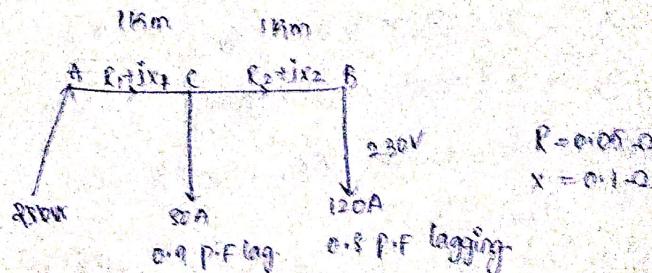

$$\text{Impedance of } AB, Z = (0.05 + j0.1) \Omega$$

Impedance of section AC,

$$Z_{AC} = R_1 + jX_1 = (0.05 + j0.1) \Omega$$

$$Z_{CB} = (0.05 + j0.1) \Omega$$

$$\text{Reference vector } V_B = 230V \angle 0^\circ = 230 + j0$$

$$\begin{aligned}\text{current at point } B, I_2 &= I_2 (\cos\phi_2 - j\sin\phi_2) \\ &= 120 (0.8 - j0.6)\end{aligned}$$

$$\text{at bus } A, \text{ reference phasor} = 230 - j0$$

Current at point C, I_1 (reference phasor)

$$\begin{aligned}I_1 &= I_1 (\cos\phi_1 - j\sin\phi_1) \\ &= 80 (0.9 - j0.43) = 72 - j34.4\end{aligned}$$

$$\begin{aligned}\Rightarrow I_{AC} &= I_1 + I_2 \\ &= 168 - j106.4\end{aligned}$$

$$\text{V.D a/c } AC = I_{AC} \cdot Z_{AC} = 168 - j106.94 (0.05 + j0.1) \\ = 19.04 + j11.48$$

$$\text{V.D a/c } CB = I_{CB} \cdot Z_{CB} = 96 - j72 (0.05 + j0.1) \\ = 12 + j6.$$

$$V_A = \text{V.D } AC + \text{V.D } BC + V_B \\ = 19.04 + j11.48 + 12 + j6 + 230 + j0. \\ = \underbrace{261.04}_{R} + \underbrace{j17.48}_{X}$$


$$\text{Magnitude} = \sqrt{(261.04)^2 + (17.48)^2} \\ = 261.62$$

$$\phi = \tan^{-1} \left(\frac{x}{R} \right) \\ \phi = \tan^{-1} \left(\frac{17.48}{261.04} \right)$$

$$= 3^\circ 83'$$

Q. A 1- ϕ d/a AB 1 km long has a resistance & reactance / conductor of 0.1Ω & 0.15Ω respectively at the far end B, the voltage $V_B = 200V$ & the current tapped is $100A$ at a power factor of 0.8 lagging. At the midpoint C of the d/a a current of $100A$ is tapped at p.f of 0.6 lagging with reference to the voltage V_C at the midpoint. Calculate:

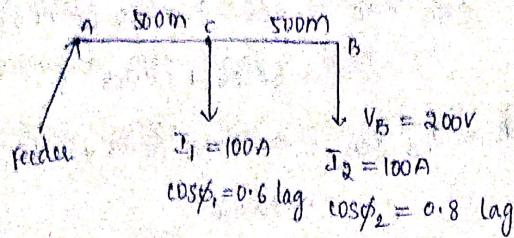- voltage at mid point
- sending end voltage
- phase angle b/w V_A & V_B .



Total Impedance of the conductor (Both go & return)

$$Z_{AB} \Rightarrow Z_{AB} = 2(0.1 + j0.15) = 0.2 + j0.3$$

$$Z_{AC} = 0.1 + j0.15 - 2$$

$$Z_{CB} = 0.1 + j0.15 - 2$$

current a/c section AC,

$$\begin{aligned} J_{AC} &= I_1 + I_2 & 0.594 \\ \text{current a/c section BC,} \\ \Rightarrow J_{BC} &= I_2 & 0.783 \\ &= 100(0.8 - j0.6) \end{aligned}$$

$$I_2 = 80 - j60$$

$$\begin{aligned} \text{Voltage a/c CB.} &= I_{CB} Z_{CB} \\ &= (80 - j60)(0.1 + j0.15) \\ &= (14 + j6) \end{aligned}$$

$$\begin{aligned} \text{i) Voltage point C} &= V_B + V.D \text{ a/c BC} \\ &= (200 + j0) + (14 + j6) \\ &= 214 + j6 \end{aligned}$$

$$V_B = 200\angle 0^\circ = 200 + j0$$

magnitude

$$\Rightarrow V_C = \sqrt{(214)^2 + 6^2} = 214.1 V_i$$

phase angle b/w V_C & V_B

$$\alpha = \tan^{-1} \left(\frac{6}{214} \right) = 1^\circ 58'$$

- ii) The load current I_1 has a lagging P.F of 0.6 w.r.t V_C & it lags behind V_C by an angle $\phi_1 = \cos^{-1}(0.6) = 53^\circ 13'$

phase angle b/w I_1 & V_B ,

$$\phi_1 = \phi_1 - \alpha = 53^\circ 13' - 1^\circ 58' \\ = 51^\circ 55'$$

$$I_1 = I_1 [\cos \phi_1 - j \sin \phi_1]$$

$$= 100 (\cos 51^\circ 55' - j \sin 51^\circ 55')$$

$$= 62.18 - j 78.3$$

$$I_{AC} = I_1 + I_2$$

$$= (62.18 - j 78.3) + (80 - j 60)$$

$$= (142.18 - j 138.3) A$$

V.D a/c AC,

$$V_{AC} = I_{AC} \cdot Z_{AC}$$

$$= (142.18 - j 138.3) (0.1 + j 0.15)$$

$$= (34.96 + j 7.49) V$$

Sending end voltage $V_A = V_B + V.D \text{ a/c AC} + V.D \text{ a/c BC}$

$$= (200 + j 0) (34.96 + j 7.49) + (17 + j 0)$$

$$= (251.96 + j 134.49) V$$

$$V_{NL} = \sqrt{(251.96)^2 + (13.49)^2}$$

$$\approx 252.32\text{V}$$

iii) The phase diff b/w V_A & V_B


$$\theta = \tan^{-1} \left(\frac{13.49}{251.96} \right)$$

$$\approx 3^\circ 64^\circ$$

Hence, the supply voltage,

~~Ans~~
Solve A 1-φ line having $R + jX$ (both go & return) conductor having $0.06 + j0.11\Omega/\text{km}$ the length of section AB & BC are 1.0 km each. The voltage at further end is 220V. Find the voltage at sending end and the phase angle difference b/w the voltage of 2 ends if

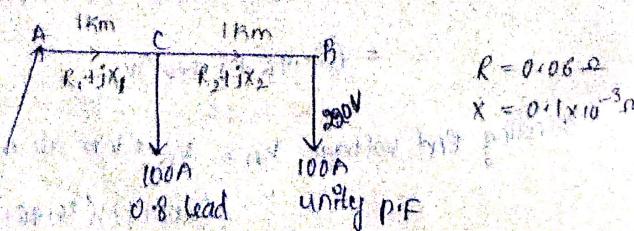- i) The p.F's of loads are reference to further end voltage.
- ii) P.F's of loads are reference with to its load points (on load voltages).



$$R = 0.106\Omega$$

$$X = 0.1 \times 10^{-3}\Omega$$

Impedance of d/r $Z = (0.06 + j0.1) \times 10^3 \Omega$
current at point B,

$$I_B = 100 (0.8 + j0.6) A$$

current at point C,

$$I_C = 100 (1.0 + j0.0) A$$

Impedance of section BC,

$$Z_{BC} = (0.06 + j0.10) \Omega$$

Impedance of section AB,

$$Z_{AB} = 0.06 + j0.10$$

64°
(retcon)

length

The

the

defl.

?

to

to

ages.

$10^{-3} \Omega$

voltage drop in section BC

$$V_{BC} = I_C Z_{BC}$$
$$= 100 (0.06 + j0.10)$$
$$= (6 + j10) \text{ volt}$$

Reference vector $V_B = 220 + (6 + j10)$
potential at point B


$$= 226 + j10$$
$$= 226.22 \angle 2.53^\circ \text{ volt.}$$

$Z_{AB} = (0.06 + j0.1)$

$$V_A = V_B + V.D \alpha / (A.C + V.D.B.C)$$
$$= (200 + j0) + (0.06 - j0.0128) + (0.01 + j0.02)$$
$$= (200.026 + j0.031) V$$
$$= \sqrt{(200.026)^2 + (0.031)^2} = 200.026$$

SUBSTATIONS

typical layout of distribution system:

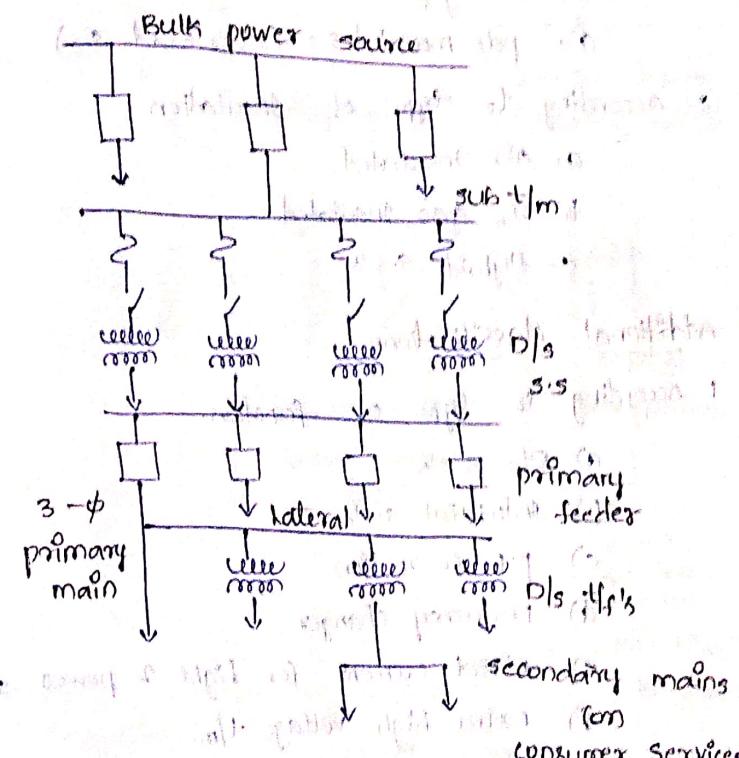

The diagram illustrates the typical layout of a distribution system. It shows the connection between bulk power sources and consumer terminals via a distribution main, lateral lines, distribution substations (D/s), primary feeders, secondary mains, and service points.

Classification of substations:

1. According to service requirement:
 - a) static s/b.

- b. converting s.s.
- 2. according to constructional features
 - a. Indoor s.s.
 - b. outdoor s.s.
 - c. underground s.s.
 - d. pole mounted s.s. (over head s.s.)

- 3. according to type of insulation
 - a. air insulated
 - b. SF₆ gas insulated
 - c. Hybrid s.s's

Additional classifications

- 1. according to type of function
 - a) E.L.s s.s's
 - b) Industrial s.s's
 - c) p.F. correction
 - d) Frequency changer
 - e) Direct current for light & power s.s's
 - f) Extra high voltage t.l.m.

- 2. according to type of operators required
 - a) T/f
 - b) Rotary converter
 - c) Rectifiers
 - d) motor generator
 - e) Frequency changer

- 3. according to type of control
 - a) manual control

b) Automatic control

c) supervisory control

symbol for circuit Elements

bus-bar
transformer

single-break
isolating switch

double-break
isolating switch

on-load
isolating switch

isolating switch
with earth
blade

current
transformer

potential
transformer


oil-circuit
Breaker

capacitive voltage
transformer


Air-circuit breaker
with over current
tripping device

air blast
circuit
breaker

lightning
arrester
(active gap)

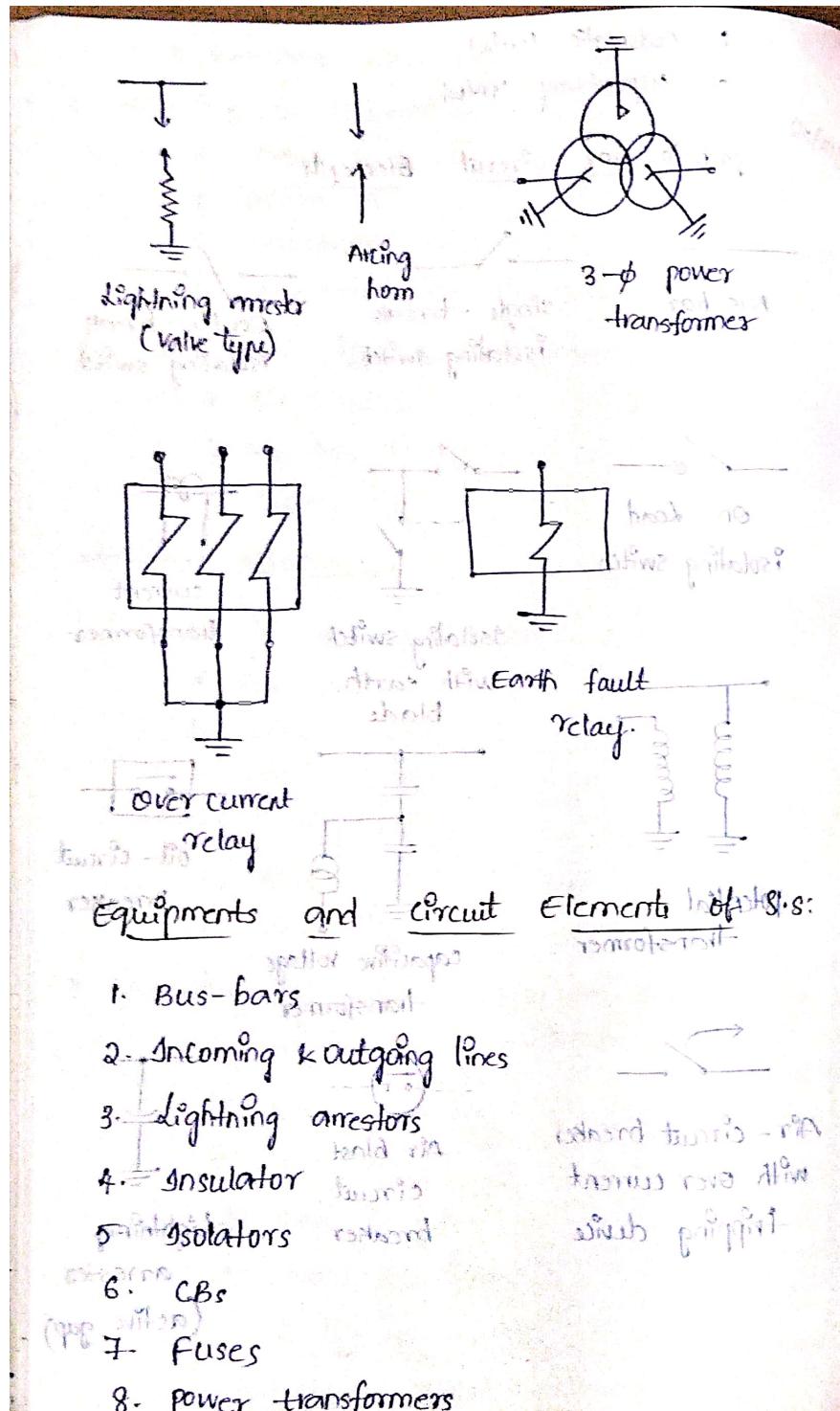

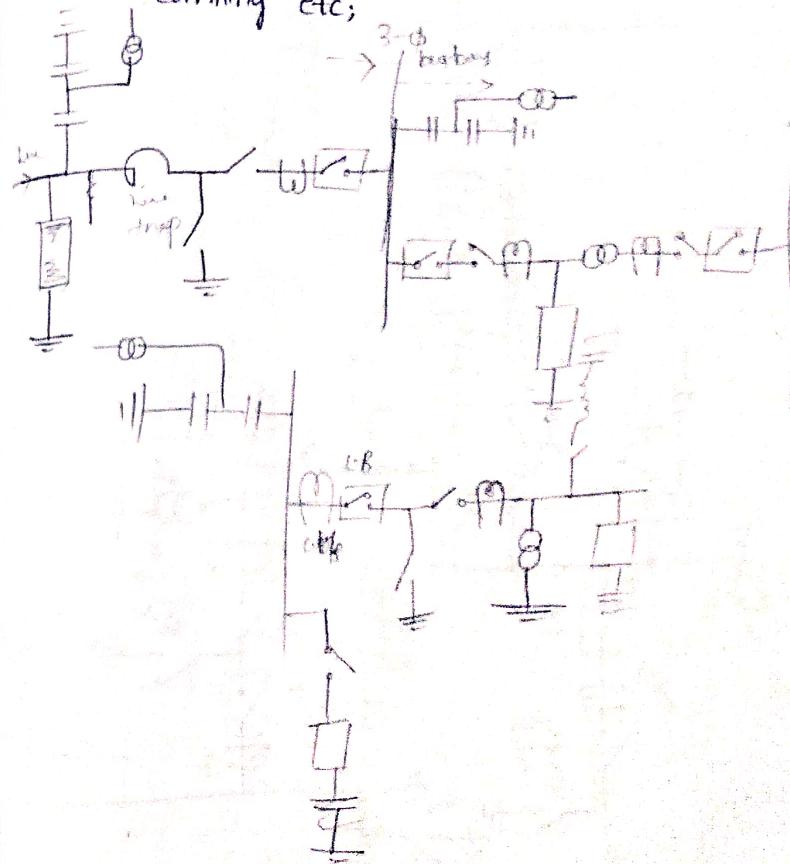9. Instrument Transformers (CT's & PT's)
10. Metering & Indicating Instruments
11. Protective Relays
12. Other equipment such as carrier current equipment, S.S., auxiliary power supply, earthing etc;



Equipments and circuit Elements of substation

- (1) Bus bar
- (2) Incoming and outgoing lines
- (3) lightning arrester
- (4) breaker
- (5) isolator (Isolating switch)
- (6) circuit breakers
- (7) fuses
- (8) power transformer
- (9) instrument transformers (CT & PT)
- (10) metering and indicating instruments
- (11) protective relays
- (12) other equipment such as carrier current equipments, substation auxiliary power supply, earthing etc.

The Busbar Arrangements


- * Single Bus System * Ring main Bus System
- * main & transfer system * Half & A full Bus System
- * Double Bus System


Busbar: It is a conductor, which distributes the power to a equipments in a bus or grid system

Bus Coupler: It is a device, which is used to connect 2 or more Busbar. It transfers the load from one busbar to another busbar.

C.B.: It is a device, which protects the electrical equipment from fault such as overload & short

H.B SF₆CB VCB A.CB - etc.

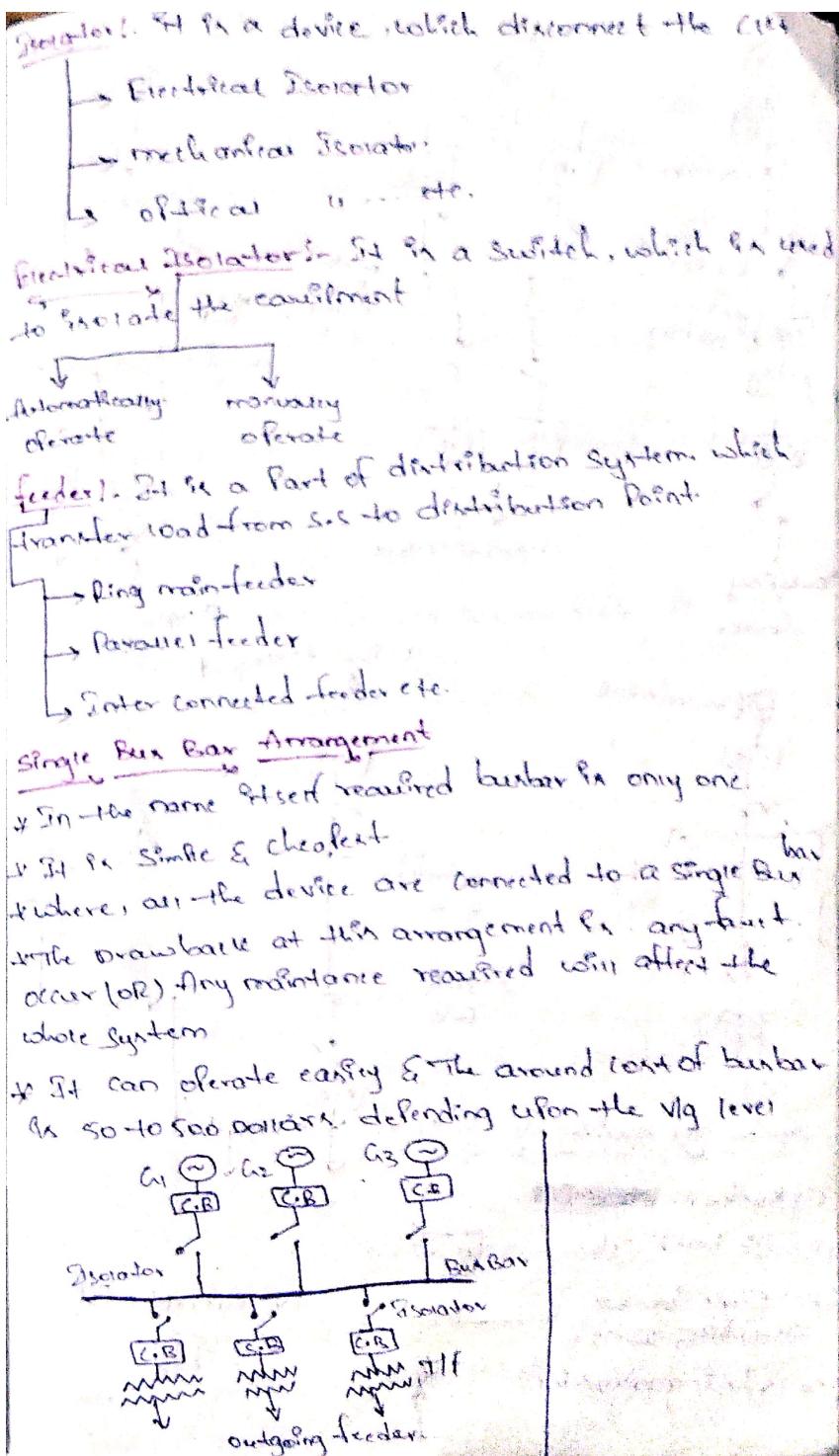

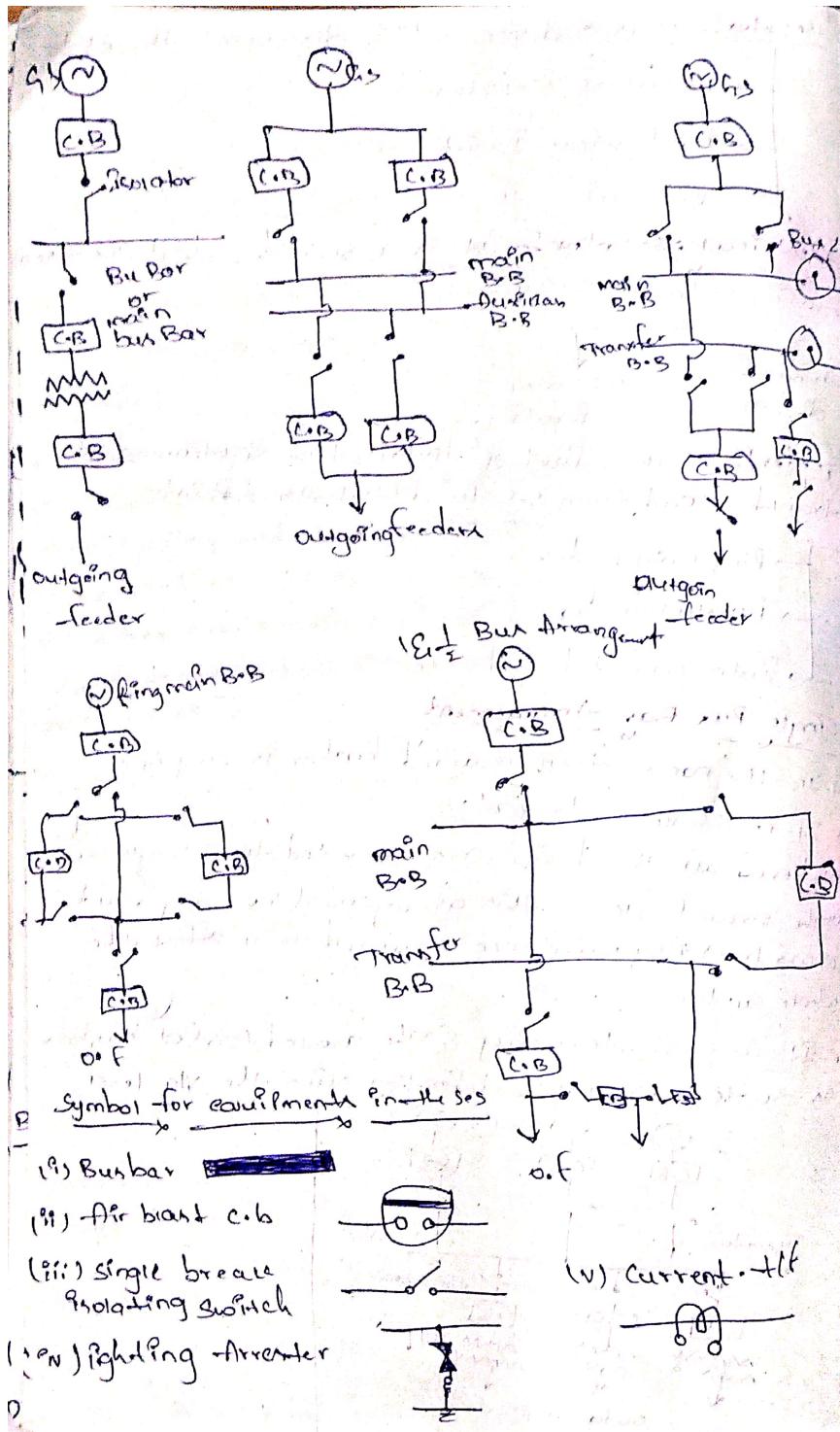

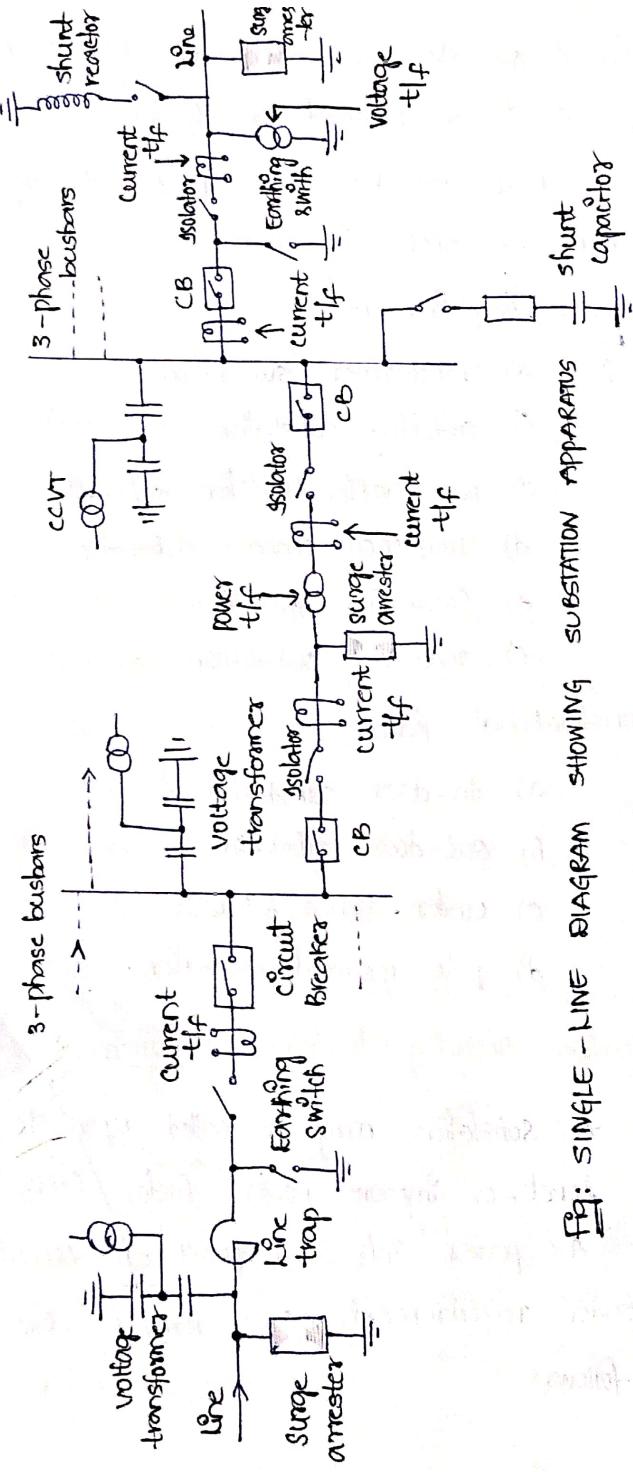


Fig.: SINGLE-LINE DIAGRAM SHOWING SUBSTATION APPARATUS

Improvement of methods of power factor.

The problems pertaining to power factor improvement using static capacitors can be dealt with in the following two ways:

a) Constant kW load assumption


b) Constant kVA load assumption.

P.F Improvement for constant kW load


Consider an inductive load taking a lagging current I at a power-factor $\cos\phi_1$. In order to improve the power factor of the circuit, the solution is to connect such an equipment in parallel with the load which takes a leading reactive component and thus partly cancels the lagging reactive component of the load current.

The capacitor takes a current I_c which leads the supply voltage V by 90° . The current I_c partly cancels the lagging reactive component of the load total current as shown in fig.

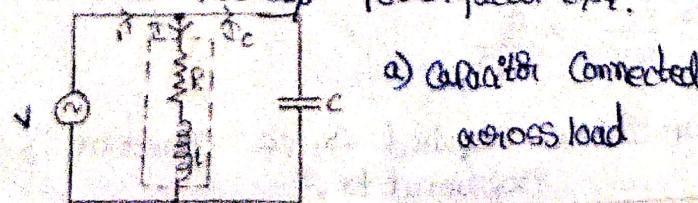The resultant circuit current becomes ' I' ' & its angle is $\log\phi_2$. It is clear that ϕ_2 is less than ϕ_1 , so that new power factor $\cos\phi_2$ is more than previous power factor $\cos\phi_1$.



a) Capacitor Connected
across load

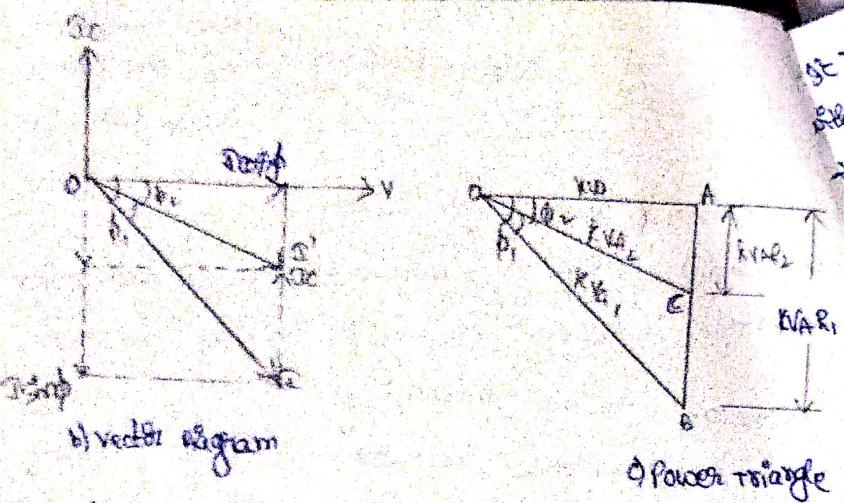

Power factor correction, when kw demand is constant

a) From the vector diagram, it is clear that after pf correction, the lagging reactive component of the load is reduced to $I \sin \phi_2$.

It may be seen

$$I' \sin \phi_2 = I \cdot \sin \phi_1 - I_c$$

$$\text{So } I_c = I \sin \phi_1 - I' \sin \phi_2$$

b) Calculations of capacitance and varying

change in capacitance $\Delta C = V P_C$

$$= V \omega C$$

$$= \omega C V^2$$

\therefore Capacitance of capacitor to improve pf from $\cos \phi_1$ to $\cos \phi_2$

$$\therefore \frac{\Delta C}{\omega C V^2} = \frac{\phi_2 - \phi_1}{\omega V^2}$$

The capacitance required for pf correction is inversely proportional to V^2 .

It may be seen that in this case, active power (P) does not change with power factor improvement.

The lagging KVAR of the load is reduced by the power factor correction equipment, thus improving the power factor to $\cos\phi_2$.

From the power triangle, it is clear that leading KVAR supplied by P.F correction equipment.

$$Q_c = BC = AB - AC \quad \text{and} \quad \tan\phi_2 = \frac{BC}{AC}$$

$$Q_c = KVAR_1 - KVAR_2 \quad \text{and} \quad \tan\phi_2 = \frac{KVAR_1 - KVAR_2}{KVA_1}$$

$$= OA(\tan\phi_1 - \tan\phi_2) \quad \text{and} \quad \tan\phi_2 = \frac{KVA_1(\tan\phi_1 - \tan\phi_2)}{KVA_1}$$


$$= KVA_1(\tan\phi_1 - \tan\phi_2) \quad \text{and} \quad \tan\phi_2 = \frac{KVA_1(\tan\phi_1 - \tan\phi_2)}{KVA_1}$$

$$\text{Active power, } P = KW = V^2 P \cos\phi_1 \quad \text{and} \quad \tan\phi_2 = \frac{KVA_1(\tan\phi_1 - \tan\phi_2)}{KVA_1}$$

$$\therefore \phi_c = \arctan(\tan\phi_1 - \tan\phi_2) = \arctan\left(\frac{KVA_1(\tan\phi_1 - \tan\phi_2)}{KVA_1}\right)$$

Knowing the leading KVAR supplied by the P.F correction equipment, the results can be obtained:

Improvement by KVA demand constant

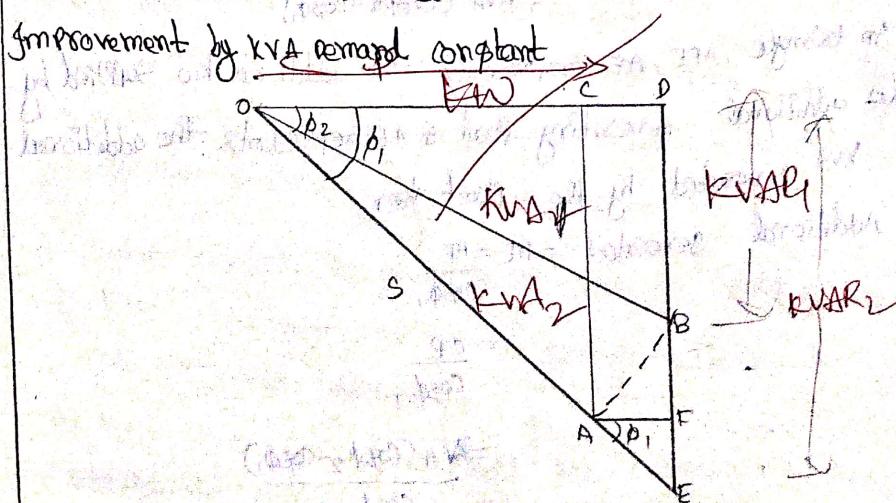

Power triangles in pf improvement when kVA demand constant.

Case I : additional kw and kVA required are supplied by installation of new generation.

Let us first consider the case when the additional kw capacity is also met by the installation of new generating plant.

Referring to

$$OC = \text{original kw output} = k_{w1}$$

$$OD = \text{the kw output after installation new plant} = k_{w2}$$

$$OA = \text{original kVA} = S_{kVA}$$

$$OB = \text{the final kVA} = S_{kVA}$$

$$\cos\phi_1 = \text{original p.f.}$$

$$\cos\phi_2 = \text{the final p.f.}$$

$$\text{Additional generated kw} = CD = OD - OC$$

$$\begin{aligned} &= OB \cdot \cos\phi_2 - OA \cdot \cos\phi_1 \\ &= kVA (\cos\phi_2 - \cos\phi_1) \end{aligned}$$

In triangle, AF, AF represents the additional kw supplied by the additional generating plant & AE represents the additional kVA generated by the plant. Then,

$$\text{Additional generated} = AE = \frac{AF}{\cos\phi_1}$$

$$= \frac{CD}{\cos\phi_1}$$

$$= \frac{kVA (\cos\phi_2 - \cos\phi_1)}{\cos\phi_1}$$

Case II : Addition Generated KVA can be kept down to the original KVA value by installation of a phase advancing plant. ③

Consider the case when generated KVA can be kept down to the original value by the installation of a phase advancing plant having KVAR rating equal to EB.

Additional KVAR rating of phase advancing plant = EB = ED - BD

$$= \text{EF} \cdot \sin\phi_1 - \text{OB} \cdot \sin\phi_2$$

$$= \frac{\text{ED}}{\cos\phi_1} \cdot \sin\phi_1 - \text{OB} \cdot \sin\phi_2$$

$$= \frac{\text{OB} \cdot \cos\phi_2}{\cos\phi_1} \cdot \sin\phi_1 - \text{OB} \cdot \sin\phi_2$$

$$= \frac{\text{KVA} \cdot \cos\phi_2}{\cos\phi_1} \cdot \sin\phi_1 - \text{KVA} \cdot \sin\phi_2$$

$$= \text{KVA} (\tan\phi_1 \cdot \cos\phi_2 - \sin\phi_1)$$

3) Derive the most economical power factor.

If a consumer improves the power factor, there is reduction to the maximum KVA demand and hence there will be annual saving over the maximum demand charges.

The value to which the power factor should be improved so as to have maximum net annual saving is known as most economical power factor.

The most economical power factor for a customer can be found by the following two causes.

1) Kw demand constant


2) KVA demand constant.

most economical pf by 'Kw' demand constant'

For a peak load P_{kw} at a power factor $\cos\phi_1$, the power loss
to be improved to most economical power factor $\cos\phi_2$. It may be
proved that the most economical power factor.

$$\cos\phi_2 = \sqrt{1 - (\frac{y}{x})^2}$$

Proof:

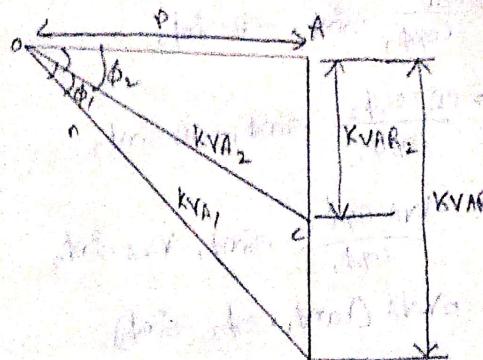

Power triangle in Power factor improvement when Kw
demand is constant.

Consider a consumer taking a peak load P_{kw} at a power factor
KVA max. demand at $\cos\phi_1$.

$$KVA_1 = \frac{P}{\cos\phi_1} = P \cdot \sec\phi_1$$

KVA max. demand at $\cos\phi_2$

$$KVA_2 = \frac{P}{\cos\phi_2} = P \cdot \sec\phi_2$$

: Annual saving in maximum demand charges.

$$= R_s \times \{XVA_1 - XVA_2\} \quad (4)$$

$$= R_s \times \{P \sec \phi_1 - P \sec \phi_2\}$$

$$= R_s \times P (\sec \phi_1 - \sec \phi_2)$$

Reactive power at $\cos \phi$,

$$kVAR_1 = P \tan \phi_1$$

Reactive power at $\cos \phi$.

$$kVAR_2 = P \tan \phi_2$$

using eqn

leading kVAR supplied by p.f correction equipment = $kVAR_1 - kVAR_2$

$$= P (\tan \phi_1 - \tan \phi_2)$$

\therefore Annual expenditure incurred on p.f correction equipment

$$= R_s \cdot Y P (\tan \phi_1 - \tan \phi_2)$$

From earn

Net annual saving

$$S = R_s \cdot Y P \{\sec \phi_1 - \sec \phi_2\} - Y P \{\tan \phi_1 - \tan \phi_2\}$$

$$\frac{d(S)}{d\phi_2} = 0$$

$$\therefore \frac{d}{d\phi_2} \{Y P (\sec \phi_1 - \sec \phi_2) - Y P (\tan \phi_1 - \tan \phi_2)\} = 0$$

$$\therefore \frac{d}{d\phi_2} (Y P \sec \phi_1) - \frac{d}{d\phi_2} (Y P \sec \phi_2) - \frac{d}{d\phi_2} (Y P \tan \phi_1) + \frac{d}{d\phi_2} (Y P \tan \phi_2) = 0$$

$$\therefore 0 - Y P \sec \phi_2 \tan \phi_2 - 0 + Y P \sec^2 \phi_2 = 0$$

$$\therefore -Y P \tan \phi_2 + Y P \sec^2 \phi_2 = 0$$

$$\therefore \tan \phi_2 = \frac{y}{x} \operatorname{cosec} \phi_2$$

$$\therefore \sin \phi_2 = \frac{y}{\sqrt{x^2 + y^2}}$$

: most economical power factor.

$$\cos \phi_2 = \sqrt{1 - \sin^2 \phi_2}$$

$$= \sqrt{1 - \left(\frac{y}{\sqrt{x^2 + y^2}}\right)^2}$$

3) Methods of Voltage Control

The voltage at different buses of the power system vary with the change in load.

The following methods are used for voltage control in a power system:

1) Excitation control of generators

2) Tap-changing transformer

3) Shunt reactors

4) Synchronous phase modulators

5) Induction regulators

6) Shunt capacitors

7) Series capacitors

8) Static VAR systems

Adjusting the system voltage by means of shunt reactive elements is known as shunt compensation.
Excitation control.


The voltage of the alternator can be kept constant by changing the field current of the alternator in accordance with the load. This is known as excitation control method.

There are two main types of automatic voltage regulators viz

(i) Thyristor regulator

(ii) SCR-Brown-Boveri regulator.

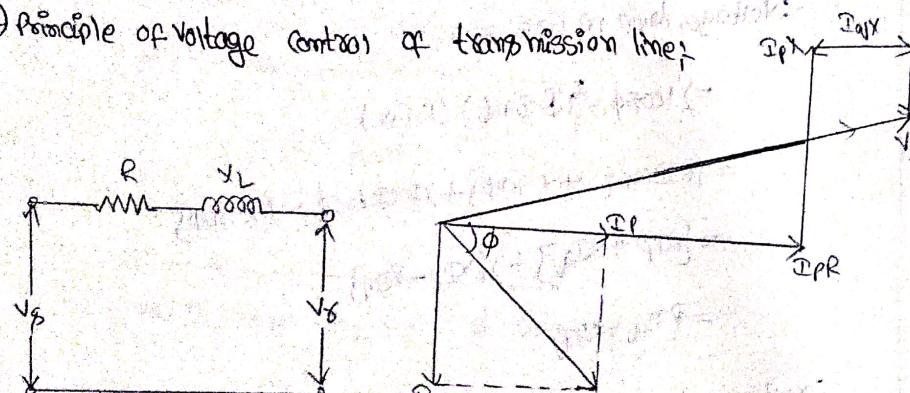2) Principle of voltage control of transmission line:



(a) equivalent circuit.

vector diagram

short transmission line.

R = Resistance of line

X = Reactance of line

$$= X_L - X_C$$

V_s = Sending end voltage per phase

V_r = Receiving end voltage per phase

I = Line current having power factor cos phi at receiving end

Load

$$= I \cdot \cos \phi + j I \cdot \sin \phi$$

$$= I_P + j Q_V$$

where $I_P = I \cdot \cos \phi$

= in-phase component of line current.

$$Q_V = I \cdot \sin \phi$$

= quadrature component of line current I .

\therefore Voltage drop in line $= I_Z$

$$= \{ I(\cos \phi - j I \cdot \sin \phi) (R + j X) \}$$

$$= \{ R I \cos \phi + X I \sin \phi \} + j \{ X I \cos \phi - R I \sin \phi \}$$


$$= [R I_P + X I_Q] + j [X I_P - R I_Q]$$

$$= R I_Q + j X I_Q$$

\therefore Voltage at receiving end = $(\text{Voltage at sending end}) - (\text{Voltage drop in line})$

3) Use of shunt reactors and shunt capacitors.

a) Shunt reactors:

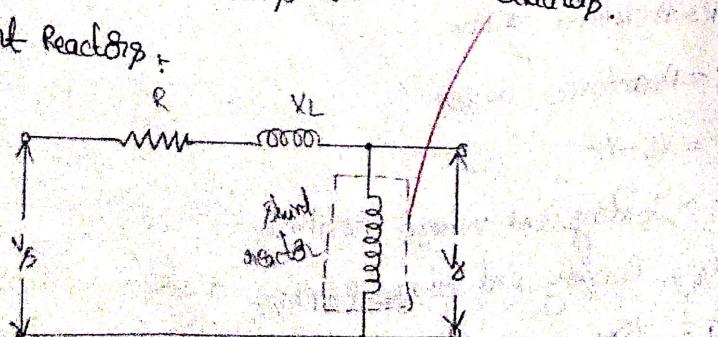

use of shunt reactance of receiving end.

Reactive power absorbed by the reactor ⑥

$$Q_L = -V \cdot I_L = \frac{-V^2}{X_L} = \frac{-V^2}{\omega L} \text{ VAR/Phase}$$


where

L = Inductance of reactor.

X_L = Reactance of reactor $= \omega L$

V = Phase voltage.

b) Shunt capacitor:

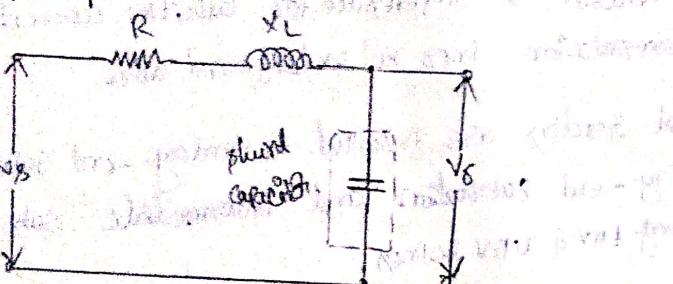

use of shunt capacitor at receiving end.


$$Q_C = V \cdot I_C = \frac{V^2}{X_C} = V^2 \cdot \omega C \text{ VAR/Phase}$$

where V = phase voltage

C = Capacitance per phase

X_C = shunt capacitive reactance per phase.

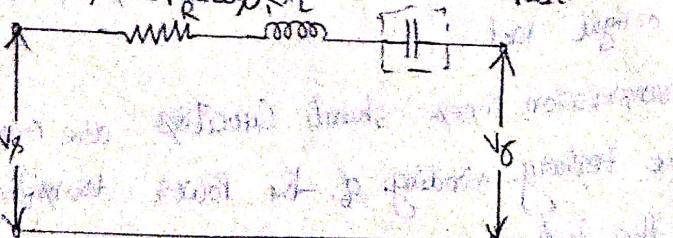4) use of series capacitor, X_L = series inductor.



use of series.

the series capacitors may be located at the sending end,
receiving-end or at centre of the line.

Rating of series capacitor

$$Q_C = I^2 X_C \text{ VAR}$$

5) Shunt Reactors:

* Shunt reactor is an inductive current element connected b/w
line & neutral in compensate for capacitive current from
transmission lines or underground cables.

* Shunt reactors are installed in sending-end substations,
receiving-end substation and intermediate substations of
long EHV & UHV ac lines.

* It is difficult to switch off large shunt reactors as the
switching overvoltages are of high magnitudes.

6) Shunt Capacitors:

* Installed near the load terminals, in receiving-end
substations, distribution substations & in switching substations.

* A serious disadvantage with shunt capacitors is that at no
load or light load.

* In transmission lines shunt capacitors are connected either
to the tertiary winding of the power transformers
or to the busses.

1) series Compensation

a) Increase in Power Transfer Capability.

The power transfer over a line given by:

$$P_s = \frac{V_s V_r}{X_L} \sin \delta$$

Where P_s = Power transferred per phase (W)


V_s = sending-end phase voltage (V)

V_r = receiving-end phase voltage (V)

X_L = series inductive reactance of the line per phase (Ω)

δ = phase angle b/w V_s & V_r

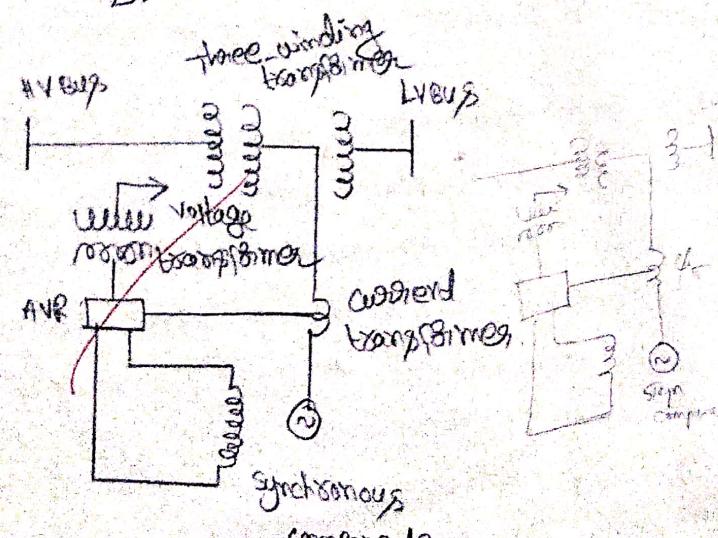b) Synchronous Capacitor (Synchronous condenser or Synchronous phase modifier).



connection of Synchronous phase modifier.

* A synchronous phase modifier is a synchronous motor.

Running without a mechanical load.

* The other common names given to a synchronous phase modifier are 'synchronous condenser'.

* It is a very convenient device to keep the receiving-end voltage constant under any condition of load.