

① → Two stage RC coupled CE-CE cascade Amplifier.

→ As shown in fig below the two stage RC coupled common emitter amplifier. The two transistors are identical and a common power supply is used. R_{C1} and R_{C2} is collector resistors [load]. Resistors R_{11} , R_{12} , R_{21} , R_{22} and R_E provide the required bias. The output of the first stage gets coupled to the input of the second stage via coupling capacitor (C_c) which also serves as the blocking capacitor to keep the dc component of the output of the first stage from reaching the input of the second stage and to pass ac component.



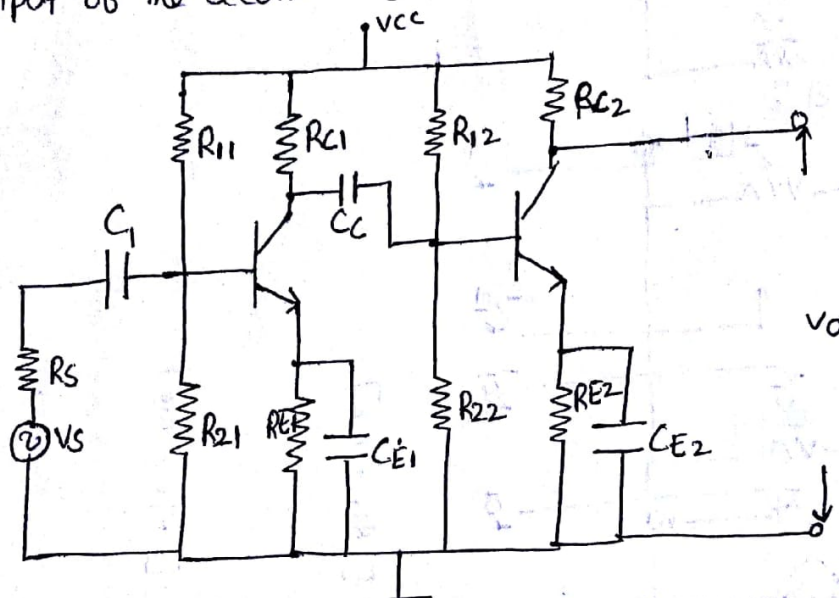


Fig: CE-CE cascade Amplifier.

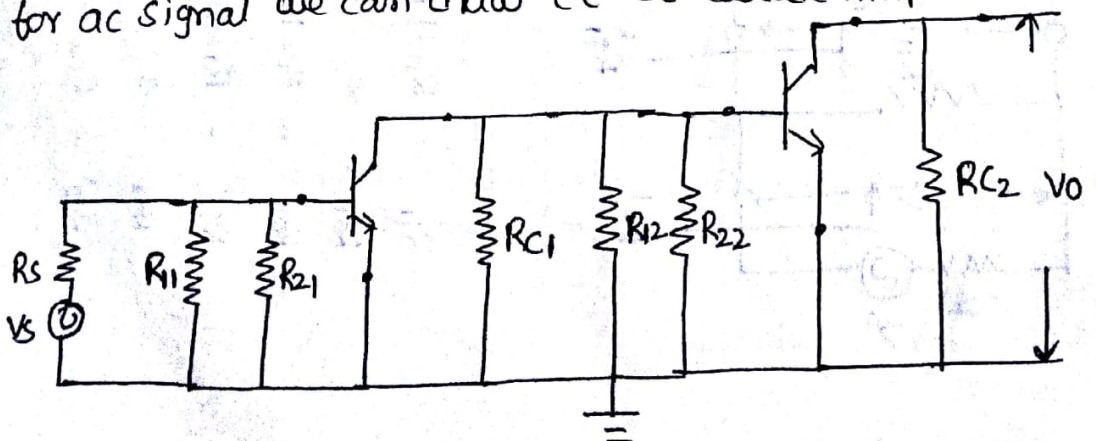Assuming all capacitors arbitrarily large and act as a short circuit for ac signal we can draw CE-CE cascade Amplifier.



[approximate
analysis].

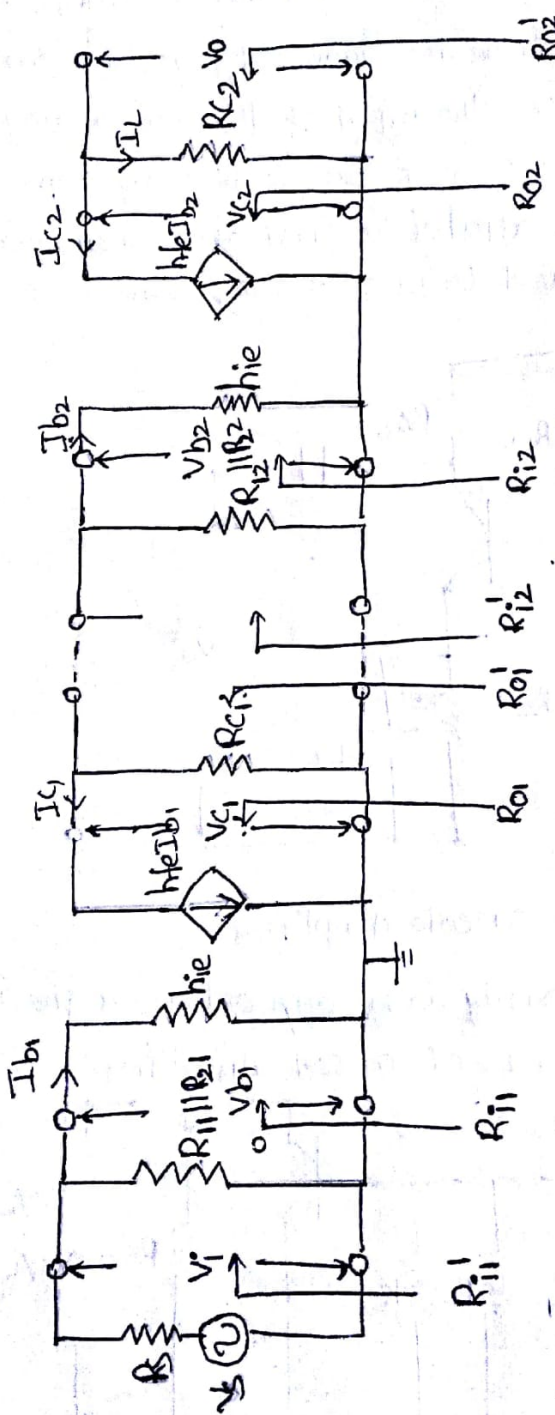

$$-R_{ij} = h_{ie}$$

$$R_1 \parallel R_2 \parallel R_3$$

8
11
D

1000

$$-p_{i+1} = h_{i+1}$$

0-112-11 Biz

$$= 0$$

$$= R_{CZ} \cdot$$

→ Analysis of second stage CE Amplifier.

(2)

$$(1) \text{ Current gain } (A_{i2}) = \frac{I_o}{I_{b2}} = -\frac{I_{c2}}{I_{b2}} = -\frac{h_{fe} I_{b2}}{I_{b2}} = -h_{fe}.$$

$$(2) \text{ Input Resistance } (R_{i2}) = \frac{V_{b2}}{I_{b2}} = \frac{h_{ie} I_{b2}}{I_{b2}} = h_{ie}.$$

$$(3) \text{ Overall input resistance } R_{i2}' = R_{i2} \parallel R_{22} \parallel R_{i2}$$

$$(4) \text{ Voltage gain } (A_{v2}) = A_{i2} \times \left[\frac{R_{c2}}{R_{i2}} \right]$$

$$\left[\begin{array}{l} \text{we know that} \\ A_v = A_i \left[\frac{R_L'}{R_i} \right] \end{array} \right]$$

→ Analysis of First stage :-

$$(5) A_{i1} = -\frac{I_{c1}}{I_{b1}} = -\frac{h_{fe} I_{b1}}{I_{b1}} = -h_{fe} =$$

$$(6) \text{ Input Resistance } (R_{i1}) = \frac{V_{b1}}{I_{b1}} = \frac{h_{ie} I_{b1}}{I_{b1}} = h_{ie}.$$

$$(7) \text{ overall input resistance } R_{i1}' = R_{i1} \parallel R_{21} \parallel R_{i1}$$

$$(8) \text{ Voltage gain } (A_{v1}) = \dots$$

$$\text{we know that voltage gain } (A_v) = A_i \left[\frac{R_L'}{R_i} \right]$$

$$\text{so } A_{v1} = A_{i1} \left[\frac{R_L'}{R_{i1}} \right]$$


$$R_L' = R_{c1} \parallel R_{i2} \parallel R_{22} \parallel R_{i2}$$

⑨ overall voltage gain ~~with~~ (A_{Vs}) (or) voltage gain with source resistance.

$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_{C2}}{V_s} = \frac{V_{C2}}{V_{B2}} \times \frac{V_{B2}}{V_{C1}} \times \frac{V_{C1}}{V_{B1}} \times \frac{V_{B1}}{V_s} \quad [\because V_{B2} = V_{C1}]$$

$$= \frac{V_{C2}}{V_{B2}} \times \frac{V_{C1}}{V_{C1}} \times \frac{V_{C1}}{V_{B1}} \times \frac{V_{B1}}{V_s}$$
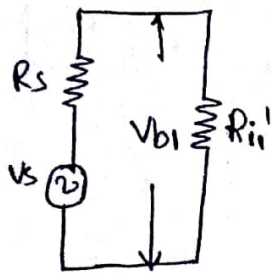
$$= A_{V2} \times A_{V1} \times \left[\frac{V_{B1}}{V_s} \right]$$



$$V_{B1} = V_s \times \left[\frac{R_{i1}'}{R_s + R_{i1}'} \right]$$

$$\frac{V_{B1}}{V_s} = \left[\frac{R_{i1}'}{R_s + R_{i1}'} \right]$$

$$A_{Vs} = A_{V1} \times A_{V2} \times \left[\frac{R_{i1}'}{R_s + R_{i1}'} \right]$$


⑩ overall current gain (A_{is}) (or) current gain with source resistance.

$$A_{is} = \frac{I_L}{I_s} = \frac{I_L}{I_{C2}} \times \frac{I_{C2}}{I_{B2}} \times \frac{I_{B2}}{I_{C1}} \times \frac{I_{C1}}{I_{B1}} \times \frac{I_{B1}}{I_s}$$


$$I_L = -I_{C2}$$

$$= \left(-\frac{I_{C2}}{I_{C2}} \right) \times A_{i2} \times \frac{I_{B2}}{I_{C1}} \times (-A_{i1}) \times \left[\frac{I_{B1}}{I_s} \right]$$
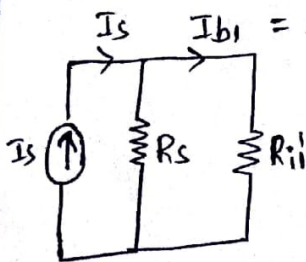
$$= (-1) \times A_{i2} \times \left[\frac{I_{B2}}{I_{C1}} \right] \times A_{i1} \times \left[\frac{I_{B1}}{I_s} \right]$$


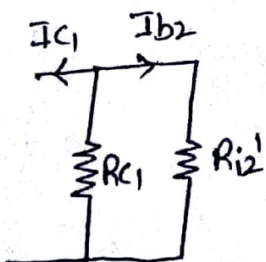
$$I_{B1} = I_s \times \left[\frac{R_s}{R_s + R_{i1}'} \right] \Rightarrow \frac{I_{B1}}{I_s} = \left[\frac{R_s}{R_s + R_{i1}'} \right]$$



$$I_{B2} = (-I_{C1}) \times \left[\frac{R_{C1}}{R_{C1} + R_{i2}'} \right] \Rightarrow \frac{I_{B2}}{I_{C1}} = - \left[\frac{R_{C1}}{R_{C1} + R_{i2}'} \right]$$

$$A_{is} = A_{i1} \times A_{i2} \times \left[\frac{R_s}{R_s + R_{i1}'} \right] \times \left[\frac{R_{C1}}{R_{C1} + R_{i2}'} \right]$$

→ Cascode Amplifier [CE- CB Amplifier]

(3)

→ The cascode amplifier consists of a common emitter amplifier stage in series with a common base amplifier stage. The cascode amplifier gives the high input impedance of a common emitter amplifier as well as good voltage gain and high frequency performance of a common base circuit.

→ It is a composite Amplifier pair with large Bandwidth, used for radio frequency applications and as a video amplifier.

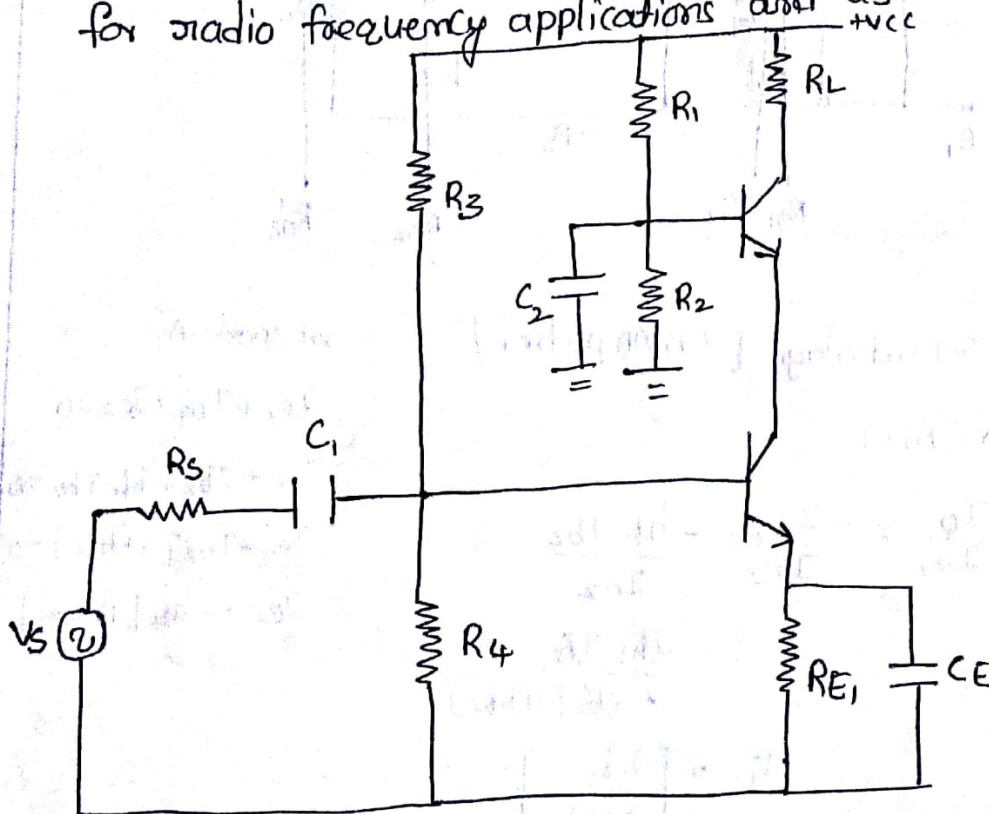


Fig: Cascode Amplifier


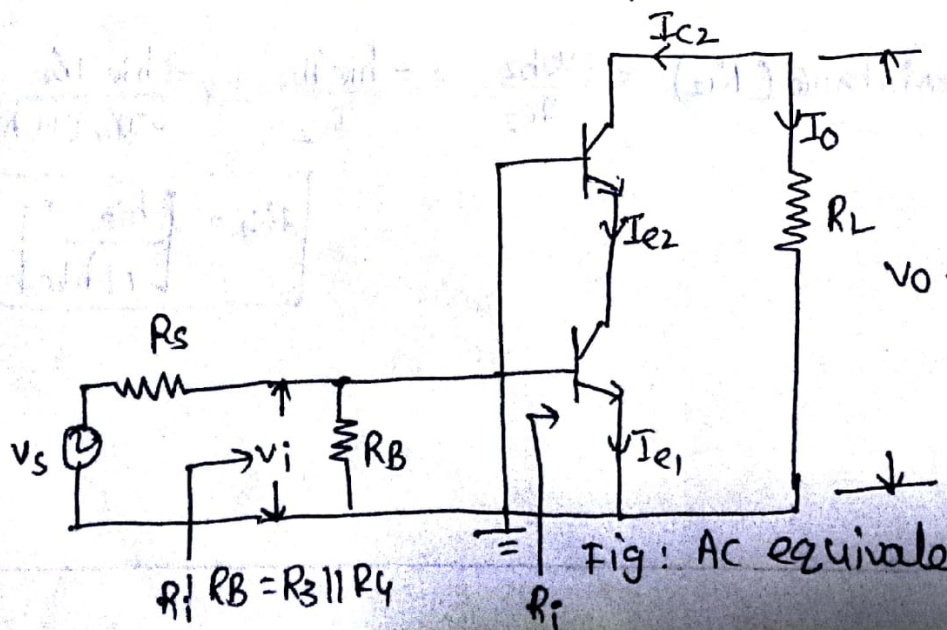


Fig: AC equivalent circuit.

→ collector current $I_{C1} \approx I_{E1}$ & I_{E2} is same as I_{C1} ,

$$\therefore I_{C2} \approx I_{E1}$$

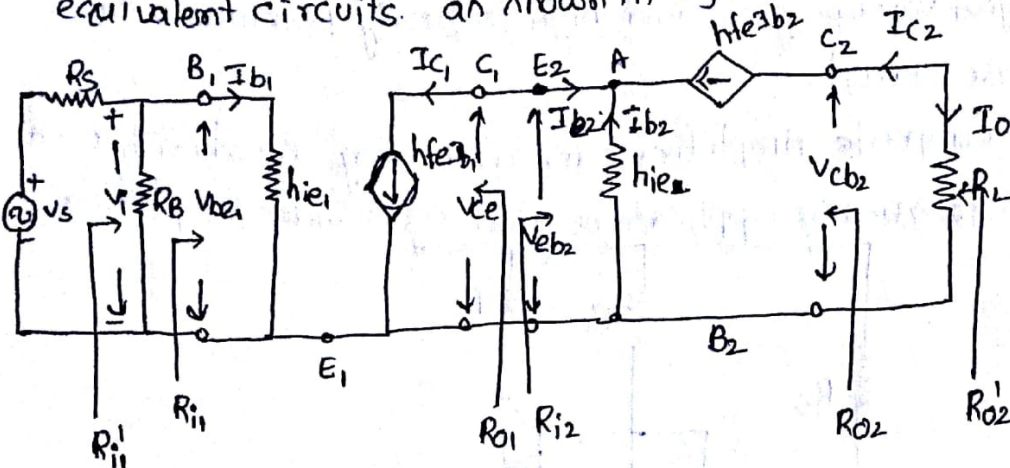→ The simplified h-Parameter equivalent circuit for cascode Amplifier is drawn by replacing transistor with their simplified equivalent circuits as shown in fig below.



→ Analysis of second stage [CB Amplifier]

(a) current gain (A_{i2})

$$\begin{aligned} A_{i2} &= \frac{I_o}{I_{E2}} = -\frac{I_{C2}}{I_{E2}} = -\frac{h_{fe} I_{b2}}{I_{E2}} \\ &= \frac{+h_{fe} I_{b2}}{+I_{b2} [1+h_{fe}]} \\ A_{i2} &= \left[\frac{h_{fe}}{1+h_{fe}} \right] \end{aligned}$$

At node A

$$I_{E2} + I_{b2} + I_{C2} = 0$$

$$I_{E2} + I_{b2} + h_{fe} I_{b2} = 0$$

$$I_{E2} + I_{b2} [1+h_{fe}] = 0$$

$$I_{E2} = -I_{b2} [1+h_{fe}]$$

(b) Input resistance (R_{i2}) = $\frac{V_{b2}}{I_{E2}} = -\frac{h_{ie} I_{b2}}{I_{E2}} = \frac{-h_{ie} I_{b2}}{+I_{b2} [1+h_{fe}]}$

$$R_{i2} = \left[\frac{h_{ie}}{1+h_{fe}} \right]$$

(4)

⑤ voltage gain

$$A_{v2} = \frac{V_{cb2}}{V_{eb2}} = \frac{I_{o2} R_L}{V_{eb2}} = \frac{-I_{c2} R_L}{-h_{ie2} I_{b2}} = \frac{-[h_{fe} R_L I_{b2}]}{-[h_{ie2} I_{b2}]} = \left[\frac{h_{fe}}{h_{ie2}} \right] R_L$$

→ Analysis of first stage (CE Amplifier)

⑥ current gain (A_{i1})

$$① \quad A_{i1} = -\frac{I_{c1}}{I_{b1}} = -\frac{h_{fe} I_{b1}}{I_{b1}} = -h_{fe}$$

$$② \quad \text{Input resistance } (R_{i1}) = \frac{V_{be1}}{I_{b1}} = \frac{h_{ie} I_{b1}}{I_{b1}} = h_{ie}$$

⑦ voltage gain (A_{v1}) :

while calculating A_{v1} , the load resistance of 1st stage =

$$R_L = R_{i2}$$

input resistance 2nd stage.

$$A_{v1} = -A_{i1} \times \frac{R_L}{R_{i1}} = A_{i2} \times \frac{R_{i2}}{R_{i1}} = -h_{fe} \times \left[\frac{R_{i2}}{R_{i1}} \right]$$

$$R_{i1} = h_{ie}$$

$$R_{i1}' = R_B \parallel R_{i1} = R_3 \parallel R_4 \parallel R_{i1}$$

$$⑧ \quad \text{overall voltage input resistance: } R_{i1}' = R_B \parallel R_{i1} \\ = R_3 \parallel R_4 \parallel R_{i1}$$

$$⑨ \quad \text{overall output resistance } R_{o2}' = R_{o2} \parallel R_L$$


$$R_{o2} = \infty$$

$$\therefore R_{o2}' = \infty \parallel R_L = R_L$$

overall voltage gain (A_v) = $A_{v1} \times A_{v2}$

overall voltage gain (A_v) with source resistance (A_{vs}) = $\frac{V_o}{V_s}$
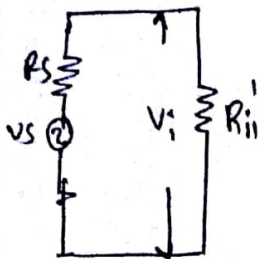
$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \left[\frac{V_i}{V_s} \right] = A_v \left[\frac{V_i}{V_s} \right] = A_{v1} \times A_{v2} \left[\frac{V_i}{V_s} \right]$$



$$V_i = V_s \times \left[\frac{R_i'}{R_i' + R_s} \right]$$

$$\frac{V_i}{V_s} = \left[\frac{R_i'}{R_i' + R_s} \right]$$

$$A_{vs} = A_v \times \left[\frac{R_i'}{R_i' + R_s} \right]$$

$$R_i' = R_{i1} \parallel R_3 \parallel R_4$$

→ overall current gain (A_i) with source resistance =


$$A_{is} = \frac{I_o}{I_s} = \frac{I_o}{I_{c2}} \times \frac{I_{c2}}{I_{e2}} \times \frac{I_{e2}}{I_{c1}} \times \frac{I_{c1}}{I_b} \times \frac{I_b}{I_s}$$

$$= \left[\left[\frac{-I_b}{I_{c2}} \right] \times (-A_{i2}) \times \left(\frac{I_{e2}}{I_{c1}} \right) \times (-A_{i1}) \times \frac{I_b}{I_s} \right]$$

$$= (+) (A_{i1} \times A_{i2}) \left[\frac{I_{e2}}{I_{c1}} \right] \times \left[\frac{I_b}{I_s} \right]$$

$$I_{e2} = -I_{c1}$$
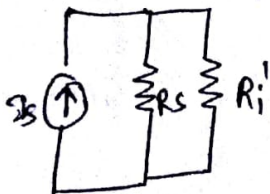
$$= (+) A_{i1} \times A_{i2} \times \left[\frac{I_b}{I_s} \right]$$




$$I_{b1} = I_s \times \left[\frac{R_s}{R_s + R_i'} \right]$$

$$\frac{I_{b1}}{I_s} = \left[\frac{R_s}{R_s + R_i'} \right]$$


$$A_{is} = A_{i1} \times A_{i2} \times \left[\frac{R_s}{R_s + R_i'} \right]$$

→ Two stage RC coupled CE-CC Amplifier by using h-parameters
[Approximate analysis].

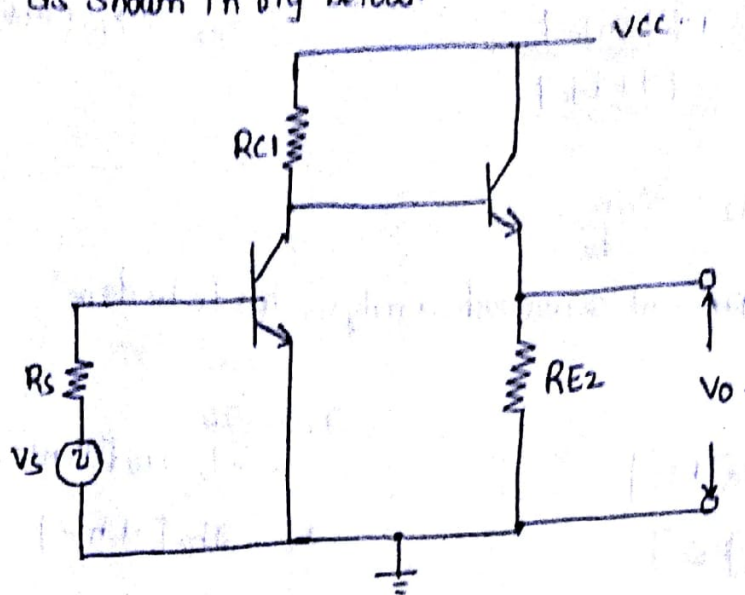
→ Consider a two stage amplifier circuit in CE-CC configuration as shown in fig below.



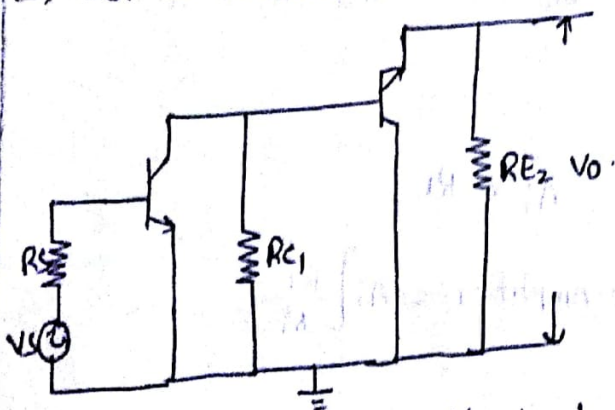→ Let us Redraw the circuit. V_{CC} is ground.



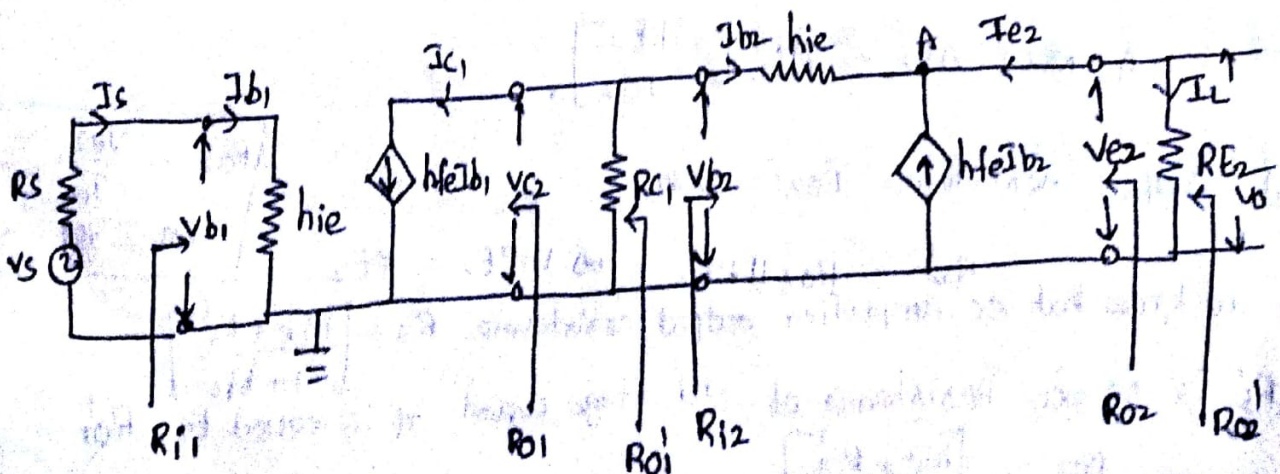→ Let us Redraw the circuit The h-Parameters equivalent circuit.



Analysis of second stage CC Amplifier :-

Apply KCL at node A

$$I_{b2} + I_{e2} + I_{c2} = 0$$

$$I_{b2} + I_{e2} + h_{fe} I_{b2} = 0$$

$$I_{b2} [1 + h_{fe}] + I_{e2} = 0$$

$$I_{e2} = -I_{b2} [1 + h_{fe}]$$

$$(1) \text{ current gain } (A_{i2}) = \frac{I_L}{I_{b2}} = -\frac{I_{e2}}{I_{b2}} \\ = -\frac{I_{b2} [1 + h_{fe}]}{I_{b2}}$$

$$A_{i2} = +[1 + h_{fe}]$$

$$\boxed{A_{i2} = [1 + h_{fe}]}$$

$$(2) \text{ Input resistance } (R_{i2}) : R_{i2} = \frac{V_{b2}}{I_{b2}}$$

Since the current source is present supermesh analysis has to be done

$$V_{b2} = h_{ie} I_{b2} + I_L R_{E2} \\ = h_{ie} I_{b2} + [I_{b2} [1 + h_{fe}]] R_{E2} \\ V_{b2} = I_{b2} [h_{ie} + [1 + h_{fe}] R_{E2}]$$

$$I_L = -I_{e2} \\ = -[-I_{b2} [1 + h_{fe}]]$$

$$I_L = I_{b2} [1 + h_{fe}]$$

$$R_{i2} = \frac{V_{b2}}{I_{b2}} = \frac{I_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]}{I_{b2}} = h_{ie} + [1 + h_{fe}] R_{E2}$$

$$\boxed{R_{i2} = h_{ie} + [1 + h_{fe}] R_{E2}}$$

$$(3) \text{ voltage gain } (R_{i2}) [A_{V2}] : \frac{V_{e2}}{V_{b2}} = \dots$$

we know that voltage gain of CC Amplifier = $A_i \left[\frac{R_L'}{R_i} \right]$

here $R_L' = R_{E2}$

$R_i = R_{i2}$

A now $A_{V2} = A_{i2} \left[\frac{R_{E2}}{R_{i2}} \right]$

$$(4) \text{ output resistance } R_{o2} = \infty$$



we know that CC Amplifier output resistance $R_o = \left[\frac{h_{ie} + R_s'}{1 + h_{fe}} \right]$

R_s' is source resistance of 2nd stage and it is equal to R_{o1}

$$\therefore R_{o2} = \left[\frac{h_{ie} + R_{o1}}{1 + h_{fe}} \right]$$

→ Analysis 1st stage CE Amplifier

(6)

(5) current gain $A_{i1} = -\frac{I_{c1}}{I_{b1}} = -\frac{h_{fe} I_{b1}}{I_{b1}} = -h_{fe}$

(6) Input resistance (R_{i1}) = $\frac{V_{b1}}{I_{b1}} = \frac{h_{ie} I_{b1}}{I_{b1}} = h_{ie}$

(7) voltage gain $[A_{v1}] =$
we know that voltage gain of CE Amplifier is $A_v = A_i \times \left[\frac{R_L'}{R_i} \right]$

Here $R_L' = R_E \parallel R_{C1} \parallel R_{i2}$

$R_{i1} = R_{i1}$

$$A_{v1} = A_{i1} \left[\frac{R_{C1} \parallel R_{i2}}{R_{i1}} \right]$$

(8) output resistance of CE Amplifier $R_{o1} = \left. \frac{V_{c1}}{I_{c1}} \right|_{V_S=0}$

$V_S=0, I_S=0, I_{b1}=0, I_{c1}=0$

$R_{o1} = \frac{V_{c1}}{0} = \infty \Rightarrow R_{o1} = \infty$


(9) overall voltage gain (A_v) = $\frac{V_{e2}}{V_S} = \frac{V_{e2}}{V_{b2}} \times \frac{V_{b2}}{V_{c2}} \times \frac{V_{c2}}{V_{b1}} \times \frac{V_{b1}}{V_S}$

$V_{b2} = V_{c2}$

$$A_v = \frac{V_{e2}}{V_{b2}} \times \frac{V_{b2}}{V_{b2}} \times \frac{V_{c2}}{V_{b1}} \times \frac{V_{b1}}{V_S}$$

$$A_v = A_{v2} \times A_{v1} \times \left[\frac{V_{b1}}{V_S} \right]$$
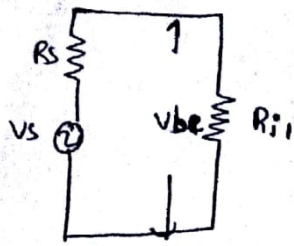
$$A_v = A_{v1} \times A_{v2} \times \left[\frac{V_{b1}}{V_S} \right]$$




$$V_{b1} = V_S \times \left[\frac{R_{i1}}{R_S + R_{i1}} \right]$$

$$\frac{V_{b1}}{V_S} = \left[\frac{R_{i1}}{R_S + R_{i1}} \right]$$


$$A_{VS} = A_{V1} \times A_{V2} \times \left[\frac{R_{i1}}{R_S + R_{i1}} \right]$$

$$\begin{aligned} \rightarrow \text{Overall current gain (A}_{IS}) &= \frac{I_O}{I_S} = \frac{I_O}{I_{e2}} \times \frac{I_{e2}}{I_{b2}} \times \frac{I_{b2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}} \times \frac{I_{b1}}{I_S} \\ &= -\frac{I_{b2}}{I_{e2}} \times (A_{i2}) \times \frac{I_{b2}}{I_{c1}} \times [-A_{i1}] \times \left[\frac{I_{b1}}{I_S} \right] \\ &= A_{i1} \times A_{i2} \times [-1] \times \frac{I_{b2}}{I_{c1}} \times \left[\frac{I_{b1}}{I_S} \right] \end{aligned}$$

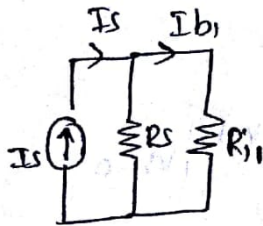

$$I_{b1} = I_S \times \left[\frac{R_S}{R_S + R_{i1}} \right]$$
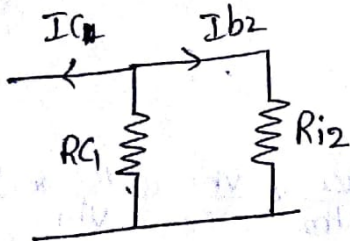
$$\frac{I_{b1}}{I_S} = \left[\frac{R_S}{R_S + R_{i1}} \right]$$



$$I_{b2} = [-I_{c1}] \times \left[\frac{R_{c1}}{R_{i2} + R_{c1}} \right]$$

$$\frac{I_{b2}}{I_{c1}} = (-) \left[\frac{R_{c1}}{R_{i2} + R_{c1}} \right]$$

$$A_{IS} = A_{i1} \times A_{i2} \times \left[\frac{R_S}{R_S + R_{i1}} \right] \left[\frac{R_{c1}}{R_{i2} + R_{c1}} \right]$$

Darlington Pair :-

we have seen that out of three configuration (CB, CC and CE), Common collector has high input impedance. The input impedance considering biasing resistance is significantly less because

$$R_i' = R_1 \parallel R_2 \parallel R_i$$


→ Typically it is $200k\Omega$ to $300k\Omega$. A single stage emitter follower circuit can give input impedance up to $500k\Omega$.

→ The input impedance of the circuit can be improved by direct coupling of two stages of emitter follower amplifier.

① The input impedance can be increased using two techniques.

- ① using direct coupling (Darlington connection) Emitter follower
- ② Bootstrap Emitter follower.

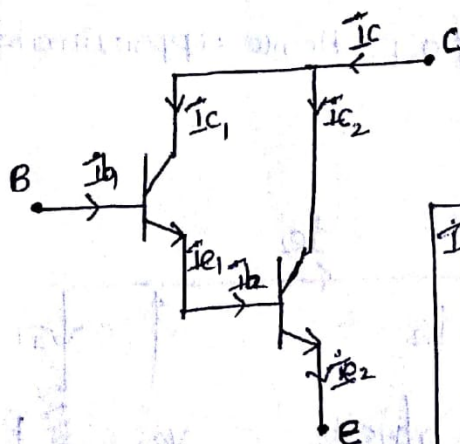① Darlington connection (or) Super β transistor :-



$$I_c = I_{c1} + I_{c2}$$

$$= \beta_1 I_{b1} + \beta_2 I_{b2}$$

$$I_c = \beta_1 I_{b1} + \beta_2 (\beta_1 + 1) I_{b1}$$

$$\begin{aligned} I_{b2} &= I_{e1} \\ &= I_{b1} + I_{c1} \\ &= I_{b1} + \beta_1 I_{b1} \\ I_{b2} &= I_{b1} [1 + \beta_1] \end{aligned}$$

$$I_c = \beta_1 I_{b1} + \beta_2 \beta_1 I_{b1}$$

$$= \beta_1 I_{b1} [1 + \beta_2]$$

$$I_c = \beta_1 \beta_2 I_{b1}$$

$$\beta_D = A_i = \frac{I_c}{I_{b1}}$$


$$\frac{I_c}{I_{b1}} = \beta_1 \beta_2$$

$$\therefore \beta_D = \beta_1 \beta_2$$

If transistor β values are same

$$\beta_D = \beta \times \beta = \beta^2$$

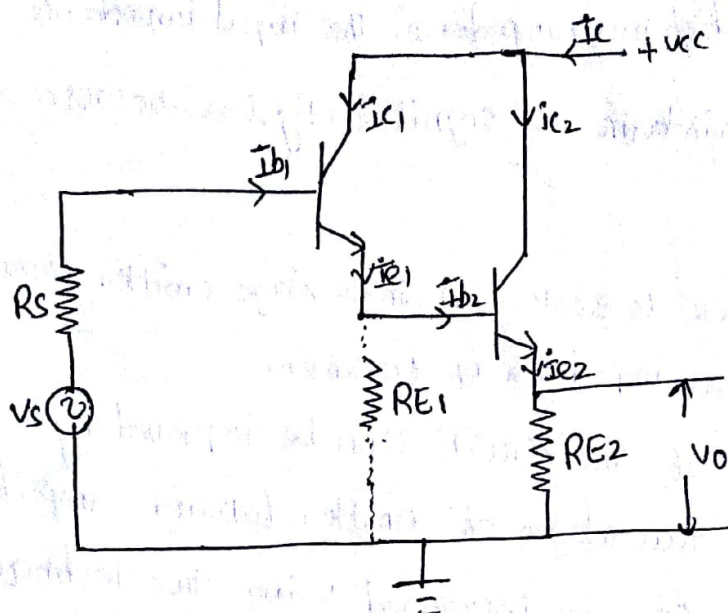
*** Darlington composite emitter follower



- Emitter follower is used to have R_i of $500k\Omega$,
- By using Darlington connection to get larger impedance Mega Ω
- The input resistance of 2nd stage is equal to the load resistance of 1st stage.

Analysis of second stage :-

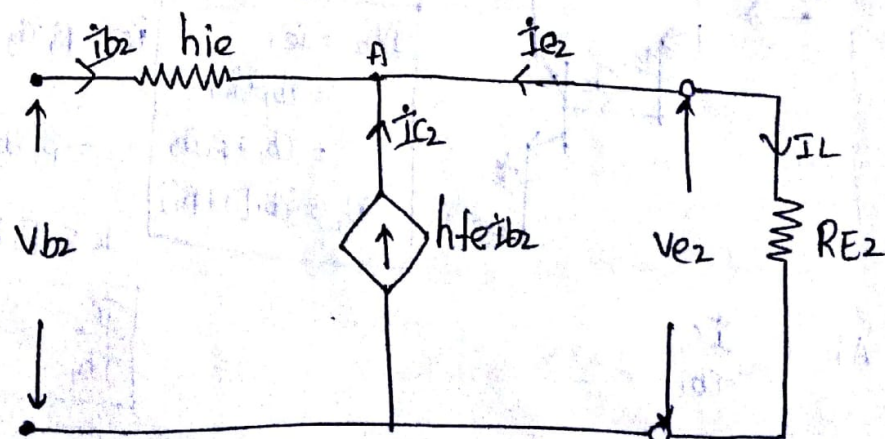- Assume $h_{oe} \cdot R_L = h_{oe} \cdot R_{E2} \leq 0.1$. Hence approximate Analysis is used.



Applying KCL at node A

(6)

$$i_{b2} + i_{e2} + i_{c2} = 0$$

$$i_{b2} + i_{e2} + h_{fe} i_{b2} = 0$$

$$i_{e2} = -i_{b2} [1 + h_{fe}]$$

$$\text{① Current gain } (A_{i2}) = \frac{i_L}{i_{b2}} = \frac{-i_{e2}}{i_{b2}} = \frac{i_{b2} [1 + h_{fe}]}{i_{b2}} = [1 + h_{fe}]$$

② Input resistance (R_{i2})

$$R_{i2} = \frac{V_{b2}}{i_{b2}}$$

$$V_{b2} = h_{ie} i_{b2} + i_L R_{E2} \quad [\text{since from super mesh analysis}]$$

$$= h_{ie} i_{b2} + (-i_{e2}) R_{E2}$$

$$= h_{ie} i_{b2} + (-i_{b2}) (1 + h_{fe}) R_{E2}$$

$$V_{b2} = i_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]$$

$$R_{i2} = \frac{V_{b2}}{i_{b2}} = \frac{i_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]}{i_{b2}}$$

$$R_{i2} = h_{ie} + (1 + h_{fe}) R_{E2}$$

If h_{ie} is less than $(1 + h_{fe}) R_{E2}$

$$R_{i2} = (1 + h_{fe}) R_{E2}$$

$$\text{③ Voltage gain } (A_{V2}) = \frac{V_{e2}}{V_{b2}} = \frac{i_L R_{E2}}{i_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]}$$

$$= \frac{-i_{e2} R_{E2}}{i_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]}$$

$$= \frac{i_{b2} [1 + h_{fe}] R_{E2}}{i_{b2} [h_{ie} + (1 + h_{fe}) R_{E2}]} = \frac{(1 + h_{fe}) R_{E2}}{h_{ie} + (1 + h_{fe}) R_{E2}}$$

Add & Subtract h_{ie} with h_{ie}

$$A_{v2} = \frac{(1+h_{fe})R_{E2} + h_{ie} - h_{ie}}{h_{ie} + (1+h_{fe})R_{E2}}$$

$$= 1 - \left[\frac{h_{ie}}{h_{ie} + (1+h_{fe})R_{E2}} \right]$$

$$A_{v2} = 1 - \left[\frac{h_{ie}}{R_{i2}} \right]$$


$$A_{v2} = 1 - \left[\frac{h_{ie}}{R_{i2}} \right]$$

Analysis of 1st stage :-

* load resistance of 1st stage is equal to the input resistance of 2nd stage R_{i2} as R_{i2} is high

$h_{oe}R_L \geq 0.1$ & hence we have to do exact Analysis.

$h_{oe}R_{E2} \geq 0.1$

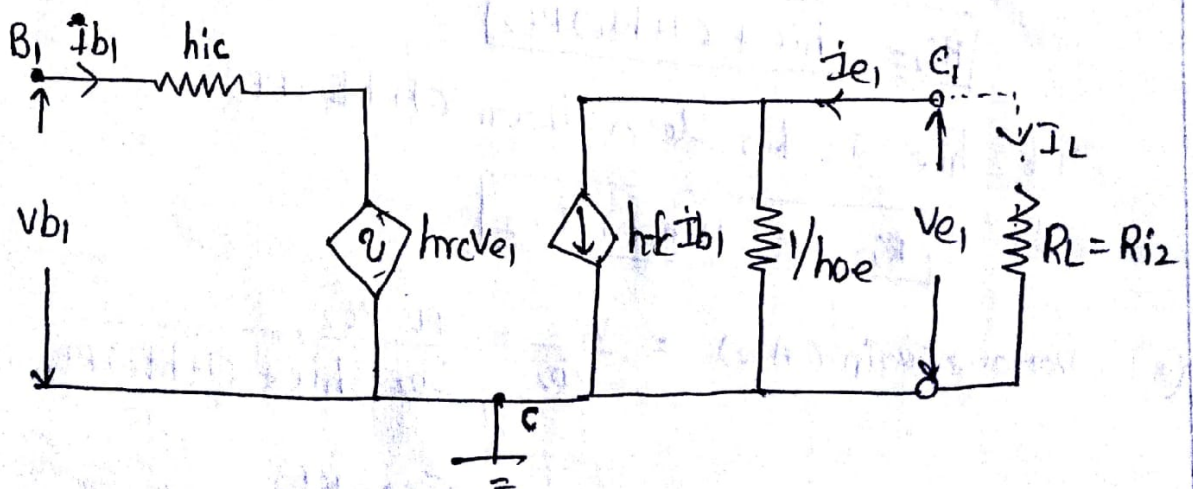

Conversion formula

⑨

$$h_{ic} = h_{ie}$$

$$h_{rc} = 1$$

$$h_{fc} = -(1 + h_{fe})$$

$$h_{oc} = h_{oe}$$

$$V_{b1} = h_{ic} I_{b1} + h_{rc} V_{e1}$$

$$I_{e1} = h_{fc} I_{b1} + h_{oc} V_{e1}$$

$$\text{Current gain } (A_{ii}) = \frac{I_L}{I_{b1}} = -\frac{I_{e1}}{I_{b1}}$$

$$= -\frac{[h_{fc} I_{b1} + h_{oc} V_{e1}]}{I_{b1}}$$

$$= -\frac{[h_{fc} I_{b1} + h_{oc} V_{e1}]}{I_{b1}}$$

$$I_{e1} = h_{fc} I_{b1} + h_{oc} V_{e1}$$

$$= h_{fc} I_{b1} + h_{oc} [I_L R_{i2}]$$

$$= h_{fc} I_{b1} + h_{oc} [-I_{e1} R_{i2}]$$

$$I_{e1} + h_{oc} I_{e1} R_{i2} = h_{fc} I_{b1}$$

$$I_{e1} [1 + h_{oc} R_{i2}] = h_{fc} I_{b1}$$

$$\frac{I_{e1}}{I_{b1}} = \left[\frac{h_{fc}}{1 + h_{oc} R_{i2}} \right]$$

$$h_{fc} \approx h_{fe} - [1 + h_{fe}]$$

$$h_{oc} \approx h_{oe}$$

$$\frac{I_{e1}}{I_{b1}} = -\left[\frac{h_{fe}}{1 + h_{oe} R_{i2}} \right]$$

$$A_{ii} = +\left[\frac{h_{fe} + 1}{1 + h_{oe} R_{i2}} \right]$$

$$A_{iz} = \left[\frac{1 + h_{fe}}{1 + h_{oe} R_{i2}} \right]$$

when $R_{i2} = h_{ie} + (1 + h_{be}) R_E$

$$h_{ie} \ll (1 + h_{be}) R_E$$

$$R_{i2} = (1 + h_{be}) R_E$$

$$A_{i1} = \frac{[1 + h_{be}]}{1 + h_{oe}(1 + h_{be}) R_E}$$

$$1 + h_{be} = h_{be}$$

$$A_{i1} = \frac{1 + h_{be}}{1 + h_{oe} h_{be} R_E}$$

(ii) $R_{i1} = \frac{V_{b1}}{I_{b1}}$

$$V_{b1} = I_{b1} h_{ic} + h_{rc} V_{e1}$$

$$R_{i1} = \frac{V_{b1}}{I_{b1}} = \frac{I_{b1} h_{ic} + h_{rc} (-I_{e1} R_{i2})}{I_{b1}}$$

$$= \frac{I_{b1} h_{ic}}{I_{b1}} + h_{rc} \left[\frac{-I_{e1}}{I_{b1}} \right] \times R_{i2}$$

$$R_{i1} = h_{ic} + h_{rc} A_{i1} R_{i2}$$

from conversion $h_{ic} = h_{ie}$
 $h_{rc} = 1$

$$R_{i1} = h_{ie} + [A_{i1} \times R_{i2}]$$

$$= h_{ie} + \left[\frac{1 + h_{be}}{1 + h_{oe} h_{be} R_E} \right] [1 + h_{be}] R_E$$

$$R_{i1} = h_{ie} + \frac{[1 + h_{be}]^2 R_E}{1 + h_{oe} h_{be} R_E}$$

$$h_{ie} \ll \frac{[1 + h_{be}]^2 R_E}{1 + h_{oe} h_{be} R_E}$$

$$R_{i1} = \frac{[1 + h_{be}]^2 R_E}{1 + h_{oe} h_{be} R_E}$$

$$\begin{aligned}
 A_{V1} &= \frac{V_{e1}}{V_{b1}} = -\frac{I_{e1} R_{i2}}{I_{b1} (R_{i1})} \\
 &= A_{i1} \left[\frac{R_{i2}}{R_{i1}} \right] \\
 &= \left[\frac{1+h_{fe}}{1+h_{oe} h_{fe} R_E} \right] \left[\frac{(1+h_{fe}) R_E}{R_{i1}} \right]
 \end{aligned}$$

Add & sub num h_{ie} .

$$= \frac{(1+h_{fe})^2 R_E + h_{ie} - h_{ie}}{(1+h_{oe} h_{fe} R_E) R_{i1}}$$

$$= \frac{(1+h_{fe})^2 R_E + h_{ie}}{(1+h_{oe} h_{fe} R_E) R_{i1}} - \frac{h_{ie}}{R_{i1} (1+h_{oe} h_{fe} R_E)} \approx 1 - \frac{h_{ie}}{R_{i1}}$$

$$\approx \left[\frac{R_{i1}}{R_{i1}} - \frac{h_{ie}}{R_{i1}} \right]$$

$$\boxed{A_{V1} = \left[1 - \frac{h_{ie}}{R_{i1}} \right]}$$

overall voltage gain

$$A_V = A_{V1} \times A_{V2}$$

$$= \left[1 - \frac{h_{ie}}{R_{i1}} \right] \left[1 - \frac{h_{ie}}{R_{i2}} \right]$$

$$= 1 - \frac{h_{ie}}{R_{i2}} - \frac{h_{ie}}{R_{i1}} + \frac{h_{ie} \times h_{ie}}{R_{i1} \times R_{i2}}$$

$R_{i1} \gg R_{i2}$ neglecting 3rd & 4th terms

$$\boxed{A_V = 1 - \left[\frac{h_{ie}}{R_{i2}} \right]}$$

overall current gain (A_i) = $A_{i1} \times A_{i2}$

$$= \left[\frac{1+h_{be}}{1+h_{oe}[1+h_{be}]R_E} \right] \times (1+h_{be})$$

$$A_i = \frac{(1+h_{be})^2}{1+h_{oe}[1+h_{be}]R_E}$$

output impedance (R_{o2}) :-

For Exact Analysis $R_{o1} = \frac{1}{h_{oc} - \left[\frac{h_{bc}h_{rc}}{R_s + h_{ie}} \right]}$

For Conversion formula

$$h_{oc} = h_{oe}$$

$$h_{bc} = -(1+h_{be})$$

$$h_{rc} = 1$$

$$h_{ic} = h_{ie}$$

$$R_{o1} = \frac{1}{h_{oe} + \left[\frac{1+h_{be}}{h_{ie} + R_s} \right]}$$

$$h_{oe} \ll \left[\frac{1+h_{be}}{h_{ie} + R_s} \right]$$

$$R_{o1} = \left[\frac{h_{ie} + R_s}{1+h_{be}} \right]$$

we can see that R_{o1} the first stage is source impedance for second stage

$$R_{s2} = R_{o1}$$

$$R_{o2} = \frac{R_{s2} + h_{ie2}}{1+h_{be}} = \left[\frac{h_{ie} + R_s}{1+h_{be}} \right] + h_{ie} / [1+h_{be}]$$

$$= \frac{h_{ie} + R_s}{(1+h_{be})^2} + \frac{h_{ie}}{(1+h_{be})}$$

$$\frac{h_{ie} + R_s + h_{ie}(1+h_{be})}{(1+h_{be})^2} =$$

$$= \left[\frac{h_{ie2}}{1+h_{be}} \right] + \frac{R_s}{(1+h_{be})^2} + \frac{h_{ie2}}{(1+h_{be})}$$

$$R_{o2} = \frac{R_s}{(1+h_{be})^2} + 2 \left[\frac{h_{ie2}}{1+h_{be}} \right]$$

$$h_{ie1} = (1+h_{be})h_{ie2}$$


* Different Coupling Schemes Used in Amplifiers:-

In Multistage Amplifier, the Output Signal of Preceding (first) stage is to be coupled to the input circuit by succeeding stage. For this interstage coupling, different types of coupling elements can be employed. These are:

1. RC Coupling
2. Transformer Coupling
3. Direct Coupling

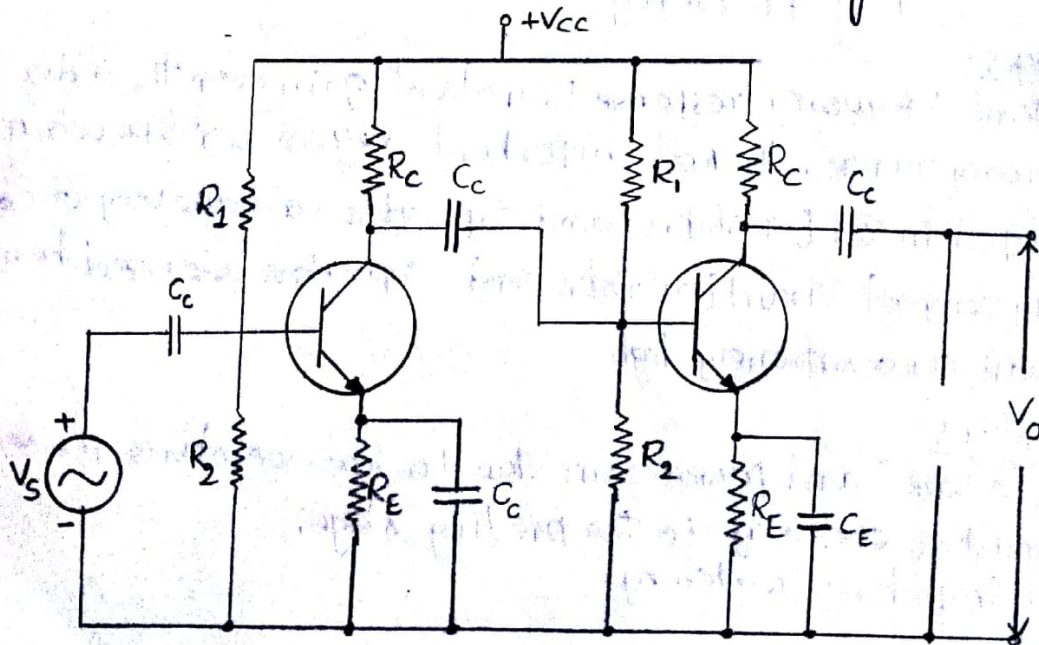(1) * RC Coupling:-


Circuit shows RC Coupled amplifier using transistors. As shown in below the output signal of first stage is coupled to the input of the next stage through coupling capacitor and resistive load at the output terminal of the first stage.



Two stage RC Coupled amplifier using transistors

The Coupling does not affect the quiescent point of the next stage since the Coupling Capacitor (C_c) blocks the d.c. voltage of the first stage from reaching the base of the Second Stage. The RC network is broadband in nature. Therefore, it gives a wideband frequency response without peak at any frequency and hence used to cover a complete AF amplifier bands. However its frequency response drop off at very low frequencies due to Coupling Capacitors and also at high frequencies due to Shunt Capacitors such as stray Capacitance.

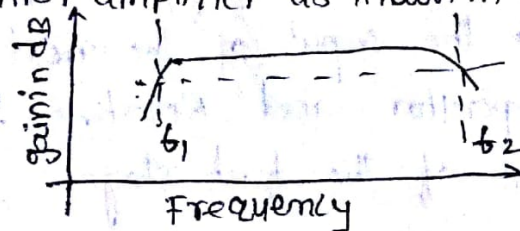→ The frequency response curve of a typical RC coupled transistor amplifier as shown in below.



Advantages:

- ① Excellent Frequency response [constant gain over the audio frequency range, the most important region for speech, music]
- ② cheaper in cost [resistors and capacitors used are very cheap.]
- ③ very compact circuit [resistors and capacitors are used being small and extremely high.]

Disadvantages:


- ① Low voltage and power gain due to low voltage drop across the input of each stage to the preceding stage.
- ② Poor impedance matching.

Application :-

- ① RC-coupled transistor amplifier are widely used as voltage amplifier.
- ② RC-coupling is rarely employed in the final stages.

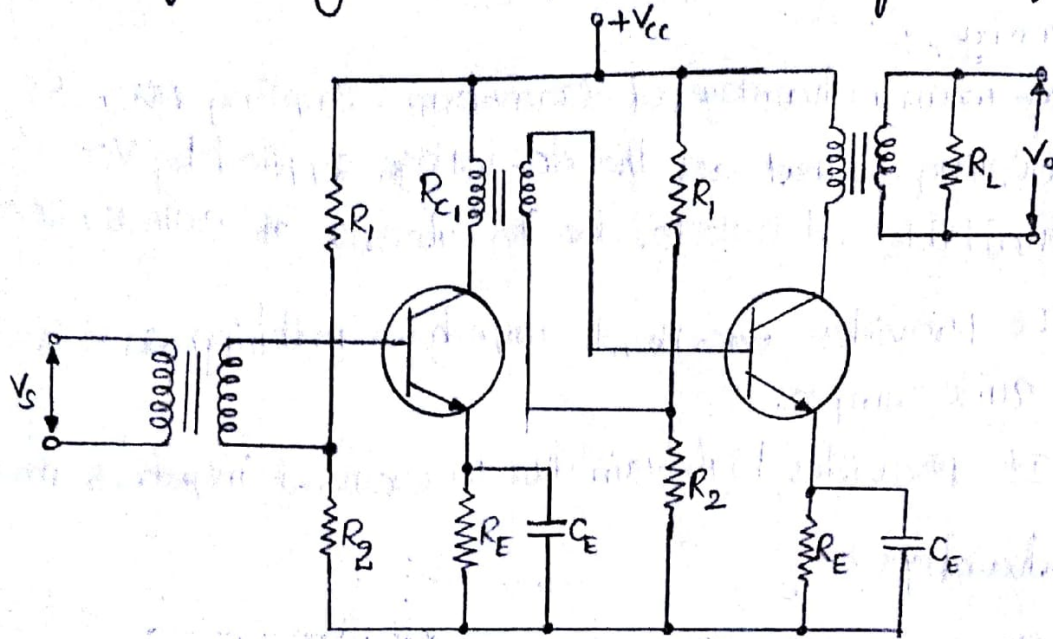(2) Transformer Coupling:-

Circuit shows transformer coupled amplifier using transistors. As shown in the circuit, the output signal of first stage is coupled to the input of the next stage through an impedance matching transformer.




Two stage Transformer Coupled amplifier using Transistors

This type of Coupling is used to match the impedance matching between output and input Cascaded stage. Usually, it is used to match the Larger output resistance of AF power Amplifier to a Low impedance Load Like LoudSpeaker.

Frequency Response of Transformer Coupled Amplifier is poor in Comparison with that of an Coupled Amplifier. Its Leakage Inductance and interwinding Capacitance does not allow amplifier to amplify the Signals of different frequencies equally well.

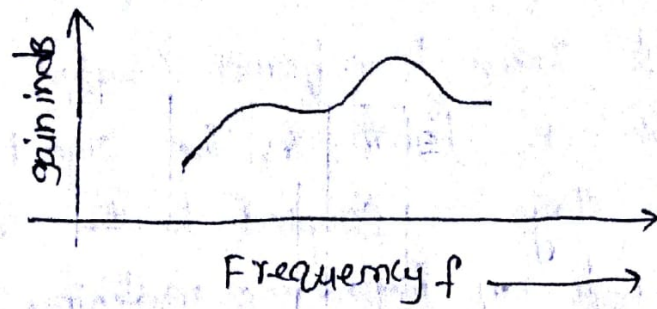Frequency Response of transformer coupled Amplifier



Advantages :-

- ① The main advantage of transformer coupling over RC-coupling is that all the dc-voltage supplied by V_{CC} is available at collector due to absence of collector resistor R_C .
- ② It provides excellent impedance matching as it is quite simple.
- ③ It provides high gain due to excellent impedance matching.

Disadvantages :

- ① Poor frequency response
- ② Bulky and costly system [transformers being bulky and costlier in comparison to resistors and capacitors]
- ③ At radio-frequencies, the inductance and interwinding capacitance presents lot of problems.

Applications :-

- ① Transformer coupled amplifiers are not used for amplifying low frequency [audio frequency] signal, they are widely used for amplifying radio-frequency [above 20 kHz]
- ② Transformer coupled amplifier is generally not used for intermediate stages in cascaded amplifiers. It is used at input (or) output stage where it can conveniently provide impedance matching.

(*) Comparison between Various Cascading Methods

Parameters	Rc coupled	Transformer Coupled	Direct Coupled
Coupling Components	Resistor and Capacitor	Impedance matching Transformer	—
Block d.c	Yes	Yes	No
Frequency Response	Flat at Middle Frequencies	Not Uniform, high at Resonant frequency and Low at other frequencies	Flat at middle frequency, and improvement in the Low frequency Response.
Impedance matching	Not achieved	Achieved	Not Achieved.
d.c. amplification	No	No	Yes
Weight	Light	Bulky and Heavy	—
Drift	Not present	Not present	Present
Hum	Not present	Present	Not present
Application	Used in all audio Small Signal amplifiers, Used in record players, tape recorders, Public Receivers and Television Receivers.	Used in amplifiers where impedance matching is an important criteria. Used in output stage of public address system to match the impedance of loudspeakers, as a tuned voltage amplifiers.	Used in amplification of Slow varying Parameters and where DC amplification is required.