
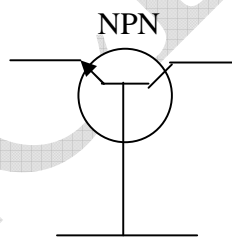
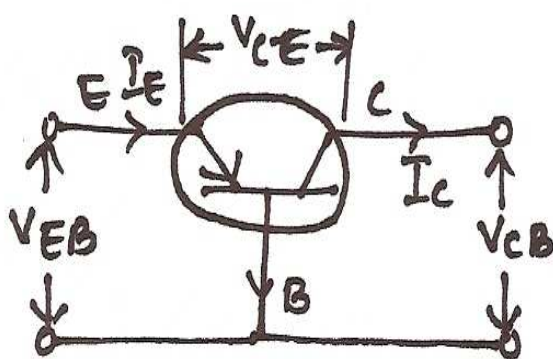


## DEPARTMENT OF ECE



UNIT-V&VI

Construction: -

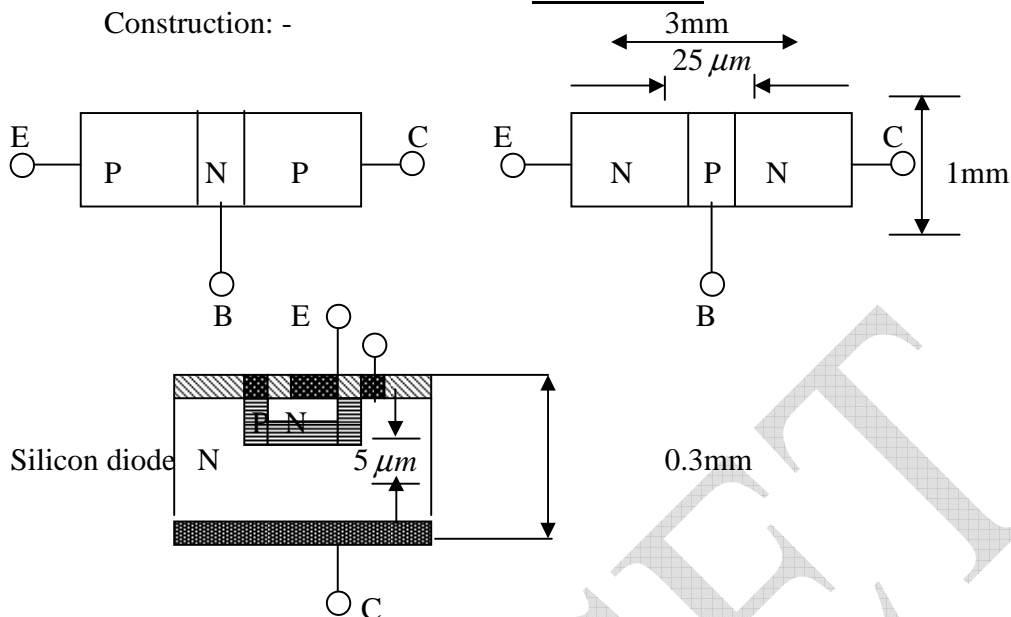

Potential barrier at the junctions of unbiased transistor.

Biasing.

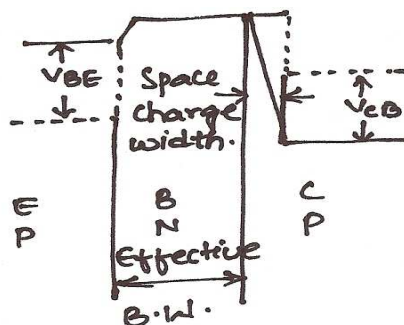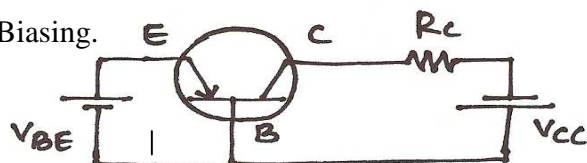

Currents in a Transistor.


$$I_E = I_C + I_B \quad \text{and} \quad I_C \approx I_E$$

$I_{CEO}$   $\equiv$  Collector current when base is open circuit  
(Reverse saturation current of B - C junction)  $\mu A$

$I_{CEO} = (\beta + 1) I_{CBO} =$  Collector current when Emitter is open circuited  
(very less current due to junction barriers)  $\mu A$ .

## DEPARTMENT OF ECE


$I_{EO}$  = Emitter base reverse (biased) saturation current when collector is open circuited.

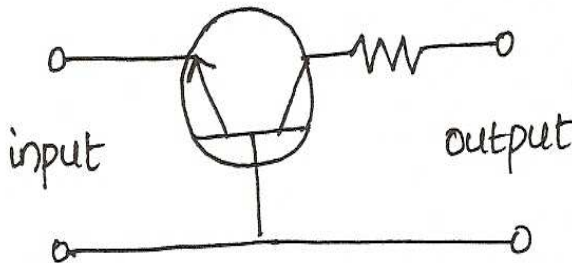**COMMON BASE CONFIGURATION: -**


Current gain( $\infty$ ) = Collector current

$$/ \text{ emitter current} = \frac{\Delta I_C}{\Delta I_E}$$

$\infty$  Varies from 0.9 to 0.95.

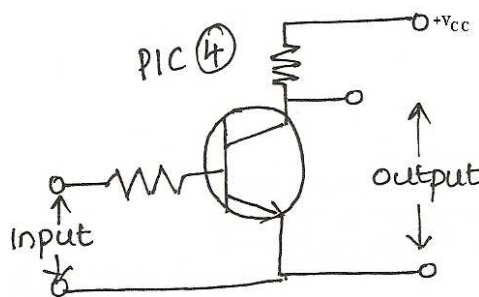**COMMON EMITTER CONFIGURATION:**

Current gain  
 $(\beta) = \frac{\text{Collector Current}}{\text{Base Current}} = \frac{\Delta I_C}{\Delta I_B}$   
 $\beta$  varies from 10 to 200 or 80.

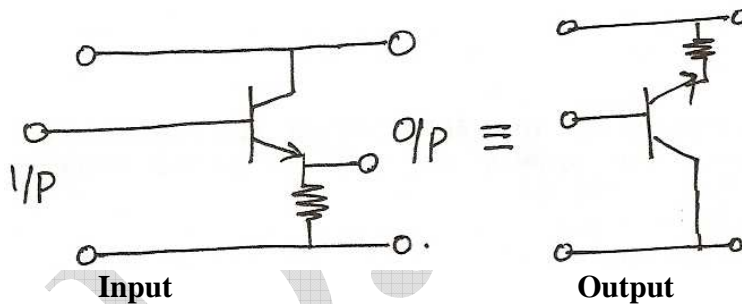**COMMON COLLECTOR CONFIGURATION: -**

Used for impedance matching

$\gamma$  = CC Current gain

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

Similarly we can get ii)  $\beta = \frac{I_C - I_{CBO}}{I_B}$

$$\text{iii) } I_C = \beta I_B + I_{CEO}$$

$$\text{iv) } I_{CEO} = (1 + \beta) I_{CBO}$$

$$\text{v) } I_E = \frac{1}{1 - \alpha} \cdot I_{CBO} + \frac{1}{1 - \alpha} \cdot I_B$$

**RELATION BETWEEN  $\alpha$ ,  $\beta$  &  $\gamma$** 

a) We know  $\Delta I_E = \Delta I_C + \Delta I_B$ , But  $\Delta I_C = \alpha \Delta I_E$ .

$$\therefore \Delta I_E = \alpha \Delta I_E + \Delta I_B$$

$$\Delta I_E - \alpha \Delta I_E = \Delta I_B \quad \text{or } \Delta I_B = \Delta I_E (1 - \alpha)$$

$$\text{Dividing both sides by } \Delta I_C, \frac{\Delta I_B}{\Delta I_C} = \frac{\Delta I_E}{\Delta I_C} (1 - \alpha)$$

## DEPARTMENT OF ECE

Or  $\frac{1}{\beta} = \frac{1}{\alpha}(1-\alpha)$  or  $\beta = \frac{\alpha}{1-\alpha}$

(b)  $\frac{\Delta I_E}{\Delta I_B} = \frac{\Delta I_C}{\Delta I_B} + \frac{\Delta I_B}{\Delta I_B}$  OR  $\frac{\Delta I_E}{\Delta I_B} = \beta + 1$

Or  $\frac{\Delta I_E}{\Delta I_C} \times \frac{\Delta I_C}{\Delta I_B} = \beta + 1$  OR  $\frac{\Delta I_E}{\Delta I_C} \times \frac{\Delta I_C}{\Delta I_B} = \beta + 1$

Or  $\frac{1}{\alpha} \cdot \beta = 1 + \beta$  or  $\alpha = \frac{\beta}{1 + \beta}$

(c)  $\gamma = \frac{\Delta I_E}{\Delta I_B}$ , Substituting  $\Delta I_B = \Delta I_E - \Delta I_C$ .

$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$ , by dividing N & D on R.H.S, by  $\Delta I_E$ .


$\gamma = \frac{\Delta I_E / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E} = \frac{1}{1 - \alpha}$

Putting the value of  $\alpha = \beta / \beta + 1$ .


$\gamma = \frac{1}{1 - \beta / \beta + 1}$

(or)  $\gamma = \frac{1}{\beta + 1 - \beta} = \frac{\beta + 1}{1} = \beta + 1$

(or)  $\gamma = \frac{1}{1 - \alpha} = \beta + 1$

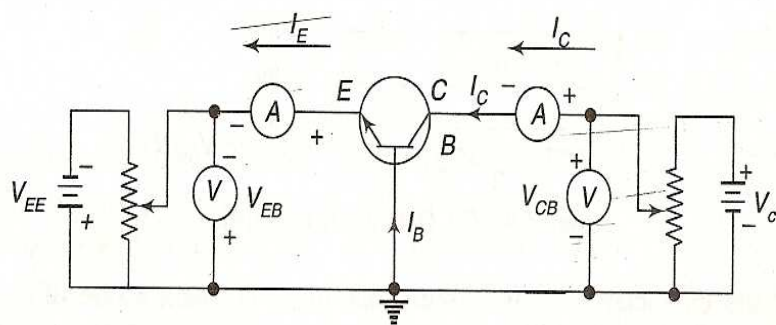**INPUT & OUTPUT CHARACTERISTICS OF CB CONFIGURATION.****Fig. 4.7** Circuit to Determine CB Static Characteristics

## DEPARTMENT OF ECE

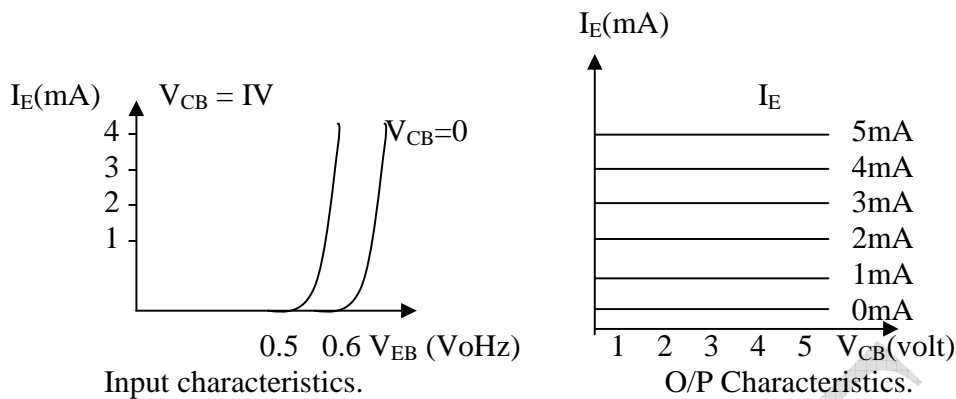

## CE CONFIGURATION

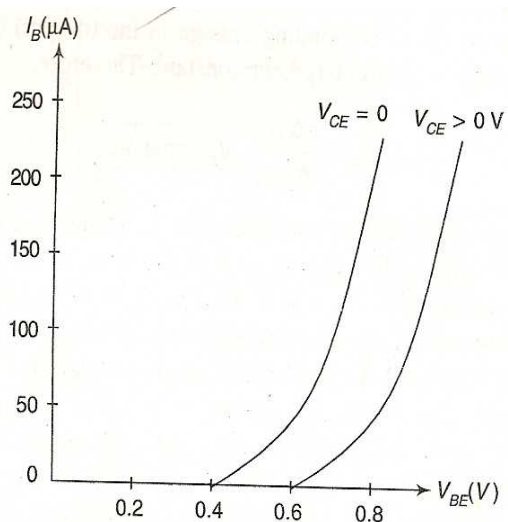


Fig. 4.11 CE Input Characteristics

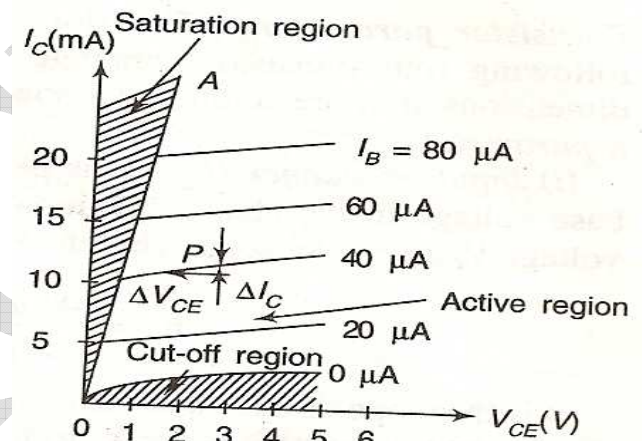


Fig. 4.12 CE Output Characteristics

## C.C.CONFIGURATION:

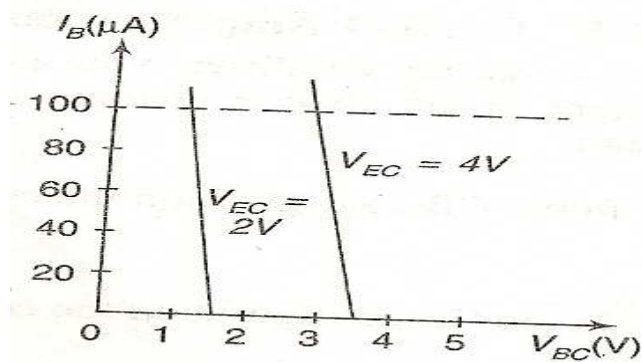


Fig. 4.14 CC Input Characteristics

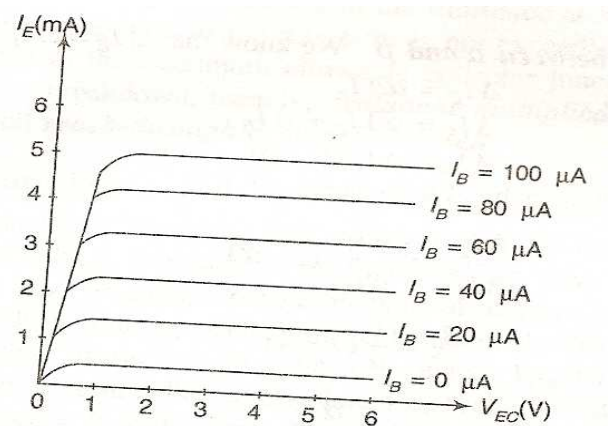


Fig. 4.15 CC Output Characteristics

## DEPARTMENT OF ECE



**EARLY EFFECT OR BASE WIDTH MODULATION.**  
**(IN CB CONFIGURATION)**

As  $V_{CC}$  made to increase the reverse bias, the space charge width between collector and base tends to increase. This results in decrease of effective width of the base. This dependence of base width on collector voltage is known as 'Early Effect'. This decrease of effective base width has three consequences.


- (i) There is less chance of recombination in base region and  $I_c$  increases causing  $\alpha$  to increase with increase in  $V_{CB}$ .
- (ii) The charge gradient is increased with in the base and current of minority carries injected across emitter junction increases.
- (iii) For extremely large  $V_{cs}$ , the effective base width becomes zero causing voltage breaks down in the transistor. This phenomenon is called the "Punch through".

**JFET CONSTRUCTION:**

- a) N Channel JFET
- b) P Channel JFET

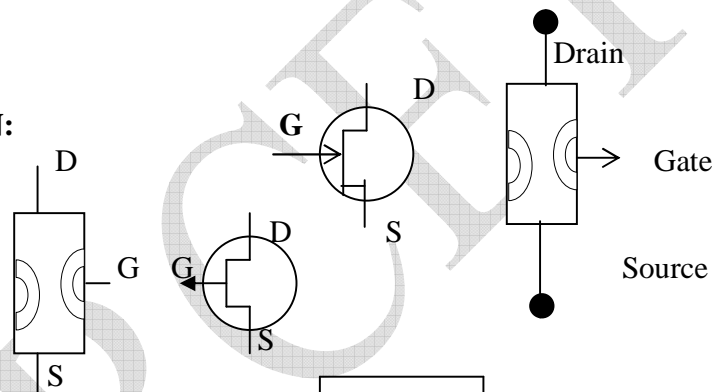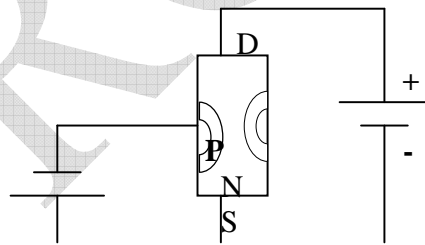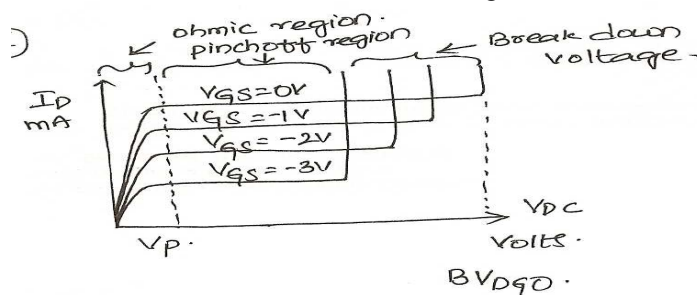**BIASING OF JFET****DRAIN CHARACTERISTICS: -**

**OHMIC REGION:-** Drain current increases With drain voltage



## DEPARTMENT OF ECE

**PINCH OFF VOLTAGE( $V_P$ ):**

$V_{DS}$  for which maximum drain current is there.

Further increase in  $V_{DS}$  will not increase  $I_D$ .

**PINCH OFF REGION: -**

Where drain current is saturated.

**BREAK DOWN VOLTAGE: -**

$V_{DS}$  where JFET breaks down

$V_{GS}$  cut off – Where  $I_B$  becomes zero, irrespective of  $V_{DS}$ .

$$V_P = |V_{GS} \text{ cut off}|$$

**CHARACTERISTICS OF JFET****MUTUAL CONDUCTANCE OR TRANS CONDUCTANCE OF FET ( $g_m$ )**

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \text{ when } V_{DC} \text{ kept constant.}$$

It is the ratio of small change in the drain current to the corresponding small change in gate voltage when drain voltage is kept constant.

b) Drain resistance  $(r_d) = \frac{\Delta V_{DS}}{\Delta I_D}$ ,  $V_{GS}$  kept constant

c) Amplification factor  $\mu = \frac{\Delta V_{DC}}{\Delta V_{GS}}$ ,  $I_D$  kept constant.

Q.1) In common base connection  $I_E = 1\text{mA}$ ,  $I_C = 0.95\text{mA}$  calculate value of  $I_B$ .

(JNTU – 2000)

$$I_B = I_E - I_C = 1 - 0.95 = 0.05\text{mA.}$$

Q2) In a CB configuration current amplification factor is 0.90 and emitter current is 1mA. Determine base current.

$$\alpha = 0.9, \quad I_E = 1\text{mA}$$

$$\alpha = \frac{I_C}{I_E}; \quad I_C = \alpha \cdot I_E = 0.9 \times 1 = 0.9\text{mA}$$

$$I_B = I_E - I_C = 1 - 0.9 = 0.1\text{mA.}$$

Q3) A BJT has  $I_B = 10\text{ }\mu\text{A}$ ,  $\alpha = .99$  and  $I_{CBO} = 1\text{ }\mu\text{A}$  what is collector current.

Solution:

$$I_C = \beta I_B + (1+\beta) I_{CBO}$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = \frac{0.99}{0.01} = 99$$

$$I_C = 99 \times 10 + (1 + 99)1$$

$$= 990 + 100 = 1090\text{ }\mu\text{A} = 1.09\text{mA.}$$

## DEPARTMENT OF ECE

- Q4) A transistor operating in CB configuration has  $I_C = 2.98\text{mA}$ ,  $I_E = 3.0\text{mA}$  and  $I_{CO} = 0.01\text{mA}$ . What current will flow in collector circuit of that transistor when connected in  $C_E$  configuration and base current is  $30\mu\text{A}$ . (May, 2006)

Given :

$$\text{CB} = I_C = 2.98\text{mA}, \quad I_E = 3.0\text{mA} \quad \therefore \alpha = \frac{2.98}{3.0} = 0.99$$

$$I_{CO} = 0.01\text{mA}.$$

$$\text{CE} = I_B = 30\mu\text{A} \quad I_C = ? \quad I_C = \beta I_B$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = \frac{.99}{0.01} = 99$$

$$I_C = \beta I_B + (\beta + 1) I_{CO}$$

$$= 99 \times 30 \times 10^{-6} + (100) 0.01 \times 10^{-3}$$

$$= 2.97 \times 10^{-3} + 1 \times 10^{-3} = 3.97\text{mA}$$


- Q 5) Given an NPN transistor for which  $\alpha = 0.98$ ,  $I_{CO} = 2\mu\text{A}$ ,  $I_{EO} = 1.6\mu\text{A}$ .  $A_{CE}$  configuration is used and  $V_{CC} = 12\text{V}$  and  $R_C = 4.0\text{K}$ . What is the min. base current required in order that transistor enter in to saturation region.

Given  $\alpha = 0.98$ ,  $I_{CO} = I_{CB} = 2\mu\text{A}$ ,

$I_{EO} = I_{CEO} = 1.6\mu\text{A}$ .

$V_{CC} = 12\text{V}$ ,  $V_{CE} = V_{CC} = 12\text{V}$ ,

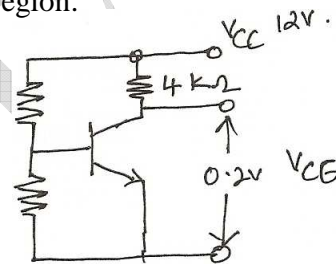$R_L = 4.0\text{K}$ ,  $I_B = ?$  (In saturation)



**Solution:-**

Where Transistor is in saturation  $V_{CE} = 0.2$  (Assumed)

$$\therefore V_{RL} = 12 - 0.2 = 11.8 \text{ Volts.}$$

$$I_c = \frac{V_{RL}}{R_L} = \frac{11.8}{4 \times 10^3} = 2.95 \times 10^{-3} = 2.95\text{mA}$$

We know

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = \frac{.98}{0.02} = 49$$

$$2.95 \times 10^{-3} = 49 I_B + (49 + 1) 2 \times 10^{-6}$$


$$2950\mu\text{A} = 49 I_B + 100\mu\text{A}$$

$$49 I_B = (2950 - 100)\mu\text{A} = 2850\mu\text{A}$$

$$I_B = \frac{2850}{49} = 58.16\mu\text{A}$$

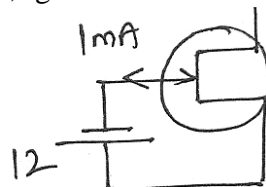- Q 6) When a reverse gate voltage is  $12\text{V}$ , gate current is  $1\text{mA}$ . Determine the resistance between gate & source. (JNTU 2000)

$$R = \frac{V}{I} = \frac{12}{1 \times 10^{-3}} = 12\text{k}\Omega$$




## DEPARTMENT OF ECE

Q 7) When reverse Gate voltage changes from 4.0 to 3.9V, the drain current changes from 1.3 to 1.6 mA. Find the Trans conductance.

Solution:

Given  $\Delta V_{GS} = 4.0 - 3.9 = 0.1 \text{ V}$   
 $\Delta I_D = 1.6 - 1.3 = 0.3 \text{ mA}$   
 $g_m = ? \quad g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{0.3 \times 10^{-3}}{0.1} = 3 \times 10^{-3} \text{ mho}$

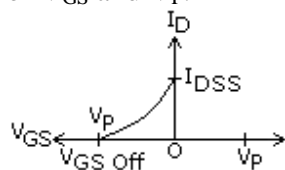Q 8) A FET has a drain current of 4mA. If  $I_{DSS} = 8\text{mA}$  and  $V_{GS \text{ off}} = -6\text{V}$ . Find values of  $V_{GS}$  and  $V_P$ . **(Nov. 2001)**



Given  $I_{DS} = 4 \text{ mA}$   
 $I_{DSS} = 8 \text{ mA}$   
 $V_{GS \text{ off}} = -6 \text{ V}$

**Solution: -**

(i)  $V_P = |V_{GS \text{ off}}| = |-6\text{V}| = 6\text{V}$ .

(ii)  $I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$$4 \times 10^{-3} = 8 \times 10^{-3} \left(1 - \frac{V_{GS}}{6}\right)^2$$


$$\frac{1}{2} = \left(1 - \frac{V_{GS}}{6}\right)^2 \quad \text{or} \quad \frac{1}{\sqrt{2}} = 1 - \frac{V_{GS}}{6}$$

$$(\text{or}) 0.707 = 1 - \frac{V_{GS}}{6};$$

or  $(\text{or}) \frac{V_{GS}}{6} = 1 - 0.707 = 0.293$

$$V_{GS} = 6 \times 0.293 = 1.758 \text{ Volts.}$$
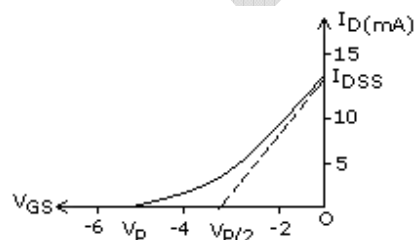
### SATURATION DRAIN CURRENT ( $I_{DSS}$ )



$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad g_m = \frac{2\sqrt{I_{DS} I_{DSS}}}{V_P}$$

$g_{mo}$  is  $g_m$  when  $V_{GS} = 0$


$$g_{mo} = \frac{-2I_{DSS}}{V_P} \quad \text{and} \quad g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right)$$



## DEPARTMENT OF ECE

**COMPARISON OF BJT AND FET**


- 1) FET is uni polar device – current  $I_D$  is due to majority (Where as BJT is Bipolar) charge carries only.
- 2) FET is less noisy as there are no junctions(in conduction channel) FET
- 3) FET Input impedance is very high ( $100\text{ m}\Omega$ ) (due to reverse bias)
- 4) FET is voltage controlled device, BJT is current controlled device
- 5) FETs are easy to fabricate
- 6) FET performance does not change much with temperature. FET has  $-Ve$  temp. Coefficient, BJT has  $+Ve$  temp. coefficient.
- 7) FET has higher switching speeds
- 8) FET is useful for small signal operation only
- 9) BJT is cheaper than FET.

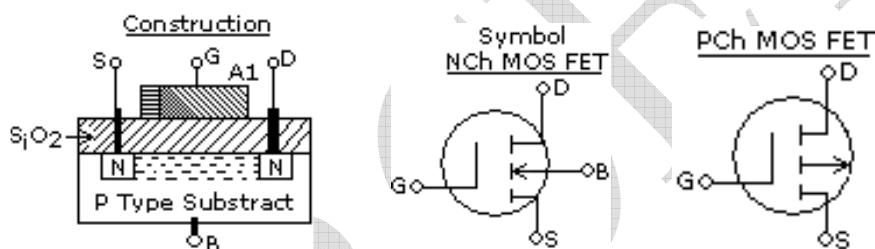**MOS FET (Metal Oxide Semiconductor Field Effect Transistor)**

N regions are highly doped  
P regions are lightly doped.

Both N regions (D & S) are repeated by 1 mil. ( $10^{-3}$  inch) or So.

A thin insulating layer is over the surface. This is  $SiO_2$  (a metal oxide) layer that covers entire channel region given and a gate of metal (AP) is formed over the  $SiO_2$  layer.


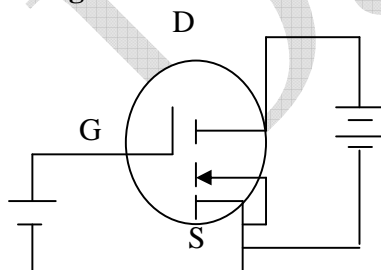
**Biasing: -**

Gate is kept positive w.r.t source. And attracts electrons (or induces negative Charge in the channel opposite to gate) This region acts like a capacitor with  $SiO_2$  layer acts as insulator between two plates of the capacitor.

Due to this induced negative region a temporarily N Channel is created from Drain to source or N channel is enhanced. Therefore it is called as Enhancement MOSFET.


Gate leakage current is in the order of  $10^{-12}$  Amps. Hence input impedance is very ( $10^{10}$  to  $10^{15}$  ohms).

## DEPARTMENT OF ECE

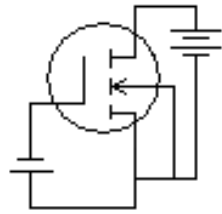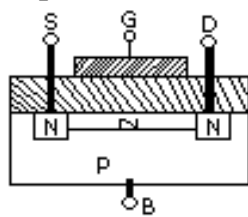**Depletion Mode.**

N channel exists.


Gate is kept negative wrt source.

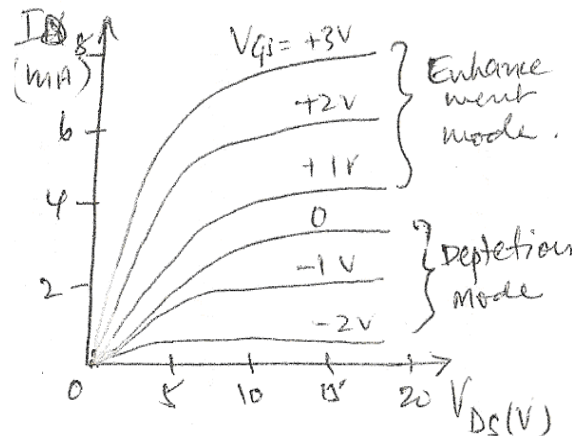**Volt Ampere characteristics of MOSFET (or) Output characteristics of MOS FET****Precautions of Handling MOS FET**

- MOS FET may be damaged due to high voltage or static charge. Thin  $\text{SiO}_2$  layer get damaged which is between Gate and Channel.
- Static voltage up to 300V may develop across a man if he uses high resistance soled shoes.
- MOS FET are protected by shorting ring that is rapped around all the four terminals.
- Technician handling the MOS FET are required to use shorting strap to discharge static charge.

Q) Explain the working principle of UJT with its characteristics (May 06, 07).

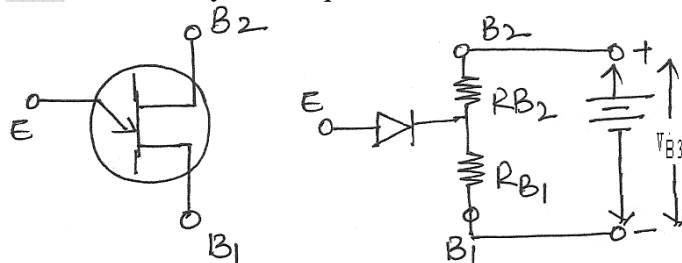Unit Junction Transistor Symbol Equivalent Circuit




It has only one PN junction. Therefore it is called as Unit Junction Transistor.

- Arrow indicates direction of convectional circuit
- Inter Base resistance ( $R_{BB}$ ) =  $R_{B1} + R_{B2}$ .

## DEPARTMENT OF ECE


- Intrinsic stand off ratio  $\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$  and ranges from 0.56 to .75.
- Voltage drop across  $R_{B1} = \eta V_{BB}$  which reverse biases PN junction.

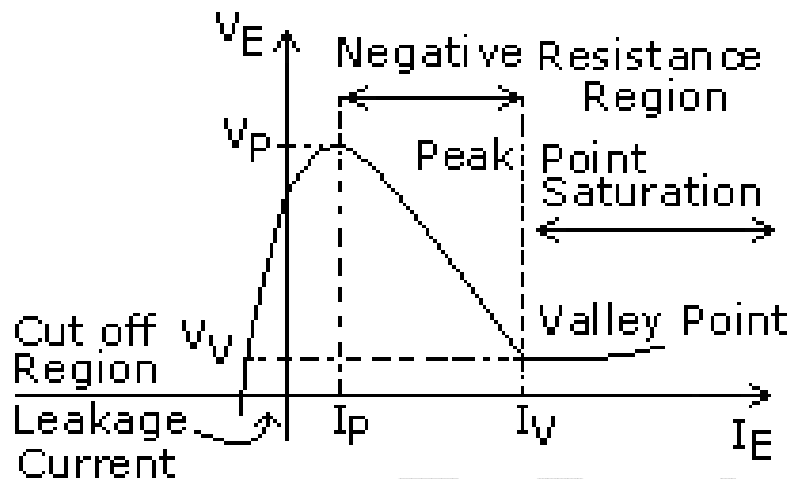**Working Principle**

- UJT remains cut off till emitter voltage is greater than  $\eta V_{BB}$ .
- 
- When  $V_E > \eta V_{BB}$ , large number of holes are injected into the N region.
- 
- These holes are repelled by terminal  $B_2$  (being +Ve biased) and collected by  $B_1$ .
- 
- Accumulation of holes in E to  $B_1$  region reduced the resistance in this section leading to increase in current  $I_E$ .
- 
- UJT has a stable firing voltage  $V_P = \eta V_{BB} + V_d = \text{voltage across } R_{B1} + V_d$ .
- $(R_{B1}) / (R_{B1} + R_{B2}) \cdot V_{BB}$ .

## DEPARTMENT OF ECE

## UJT RELAXATION OSCILLATOR.

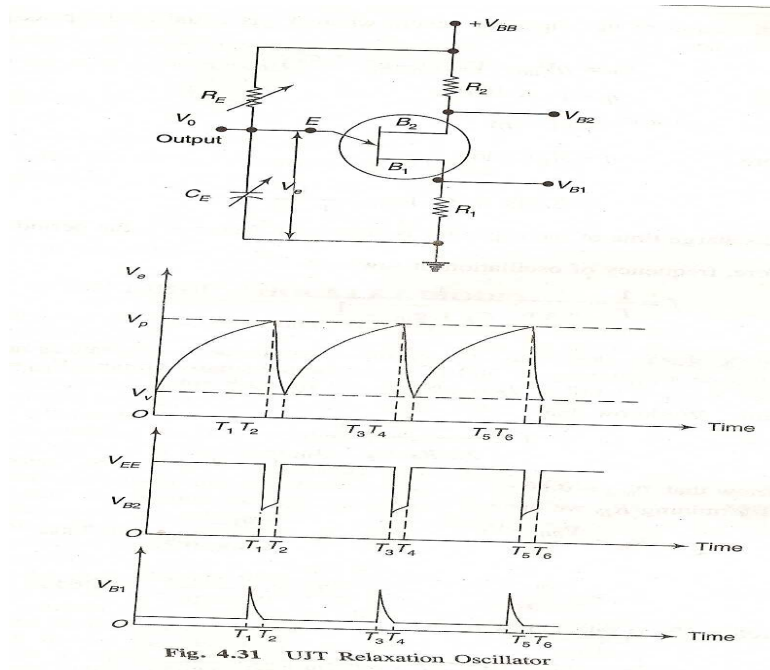


- UJT is used to generate saw tooth waveform
- $R_1$  and  $R_2$  are external resistors (not  $R_{B1}$  &  $R_{B2}$ )
- By changing  $C_E$  and  $R_E$  we can change the frequency of oscillation.

$$V_C = V_{BB} \left( 1 - e^{\frac{-t}{R_E C_E}} \right)$$

$$V_P = \eta V_{BB} = V_{BB} \left( 1 - e^{\frac{t}{R_E C_E}} \right)$$

$$\text{or } n = \left( 1 - e^{\frac{-t}{R_E C_E}} \right), \text{ taking log e both sides } t = R_E C_E \log_e (1/1-n)$$

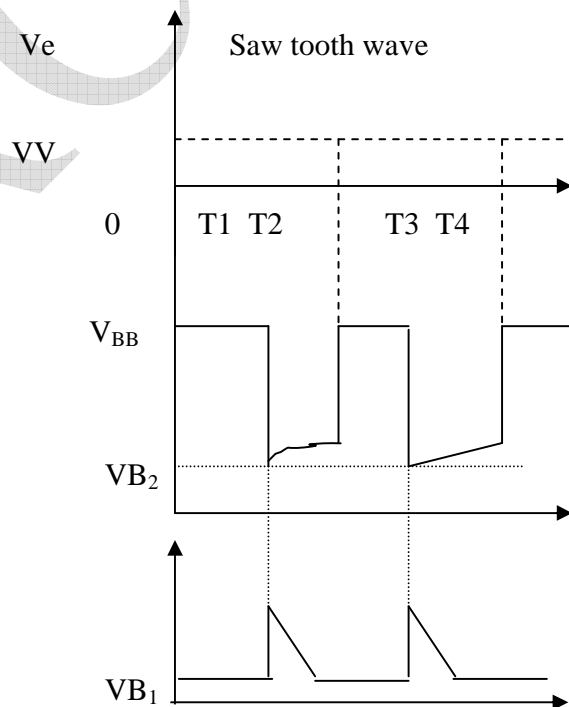
$$\text{or } t = 2.303 R_E C_E \log_{10} (1/1-n)$$



## DEPARTMENT OF ECE

- Frequency of Oscillation  $f = \frac{1}{t} = \frac{1}{2.3R_E C_E \log_{10} \frac{1}{1-n}}$

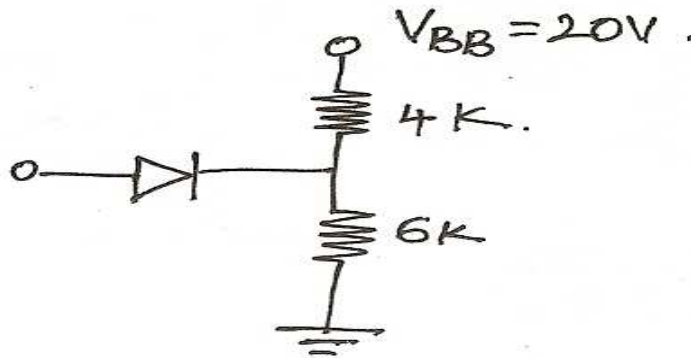- Q1) A silicon UJT has an inter base resistance  $R_{BB} = 10k\Omega$  and  $R_{B1} = 6k\Omega$  with  $I_E = 0$ . If  $V_{BB} = 20V$  and  $V_E < V_P$  find UJT current (c) and  $V_P$  (Dec.2003)



$$R_{BB} = 10K\Omega; \quad I \text{ current (c)} = \frac{V_{BB}}{R_{BB}} = \frac{20}{10K} = 2mA$$

$$V_P = V_{RB1} + V_d = 6K \times 2mA + 0.7V = 12.7V \text{Volts}$$

- Q2) If  $\eta = 0.8$  and  $V_{BB} = 15V$  and  $V_d = 0.7V$ , find the value of  $V_P$ . (June 2005)

**Solution:**

$$V_P = \eta V_{BB} + V_d = 0.8 \times 15 + 0.7 = 12.7 \text{ Volts}$$

- Q 3) A UJT has a firing potential of 20V. It is connected across the capacitor of a series RC circuit with  $R = 100K$  and  $C = 1000 \text{ Pf}$  supplied by a source 40V DC. Calculate the time period of saw tooth wave form generated.

**Solution: -**

$$V_C = V_{BB} \left( 1 - e^{-t/R_C} \right)$$

$$V_C = 20V, V_{BB} = 40V, R = 100K, C = 1000Pf.$$

$$20 = 40 \left( 1 - e^{-\frac{t}{10^5 \times 1000 \times 10^{-12}}} \right) \text{ or } \frac{1}{2} = 1 - e^{-\frac{t}{10^4}}$$

$$\text{Or } \frac{1}{2} = 1 - e^{-10^4 t} \quad \text{or} \quad e^{-10^4 t} = 1 - 1/2 = 1/2$$

$$-10^4 t \log_e = \log_e 1/2 \text{ or } -10^4 t = -0.693$$

$$t = \frac{0.693}{10^4} = \frac{.693 \times 10^6}{10^4} \mu \text{sec} = 69.3 \mu \text{sec}.$$

## DEPARTMENT OF ECE

**SILICON CONTROLLED RECTIFIER:**

- 1) It is a four layer three Terminal device
- 2) Leakage current in silicon is very small compared Germanium

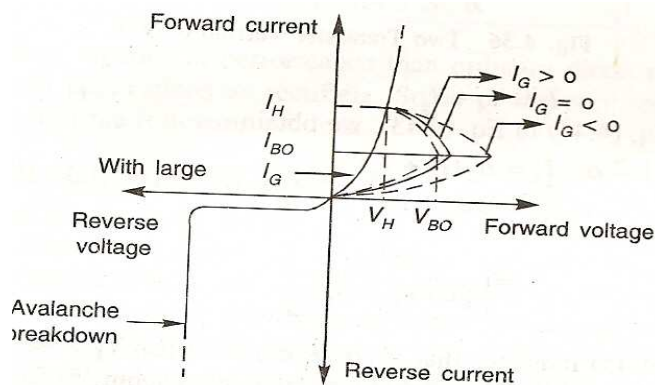
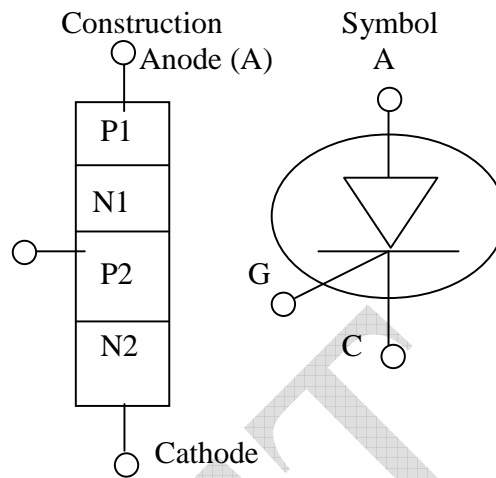
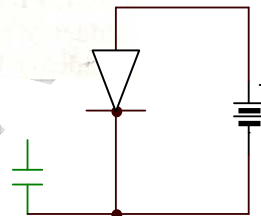


Fig. 4.35 Characteristics of SCR

- a) cut off region
- b) negative Resistance region

Biasing of SCR.

**CHARACTERISTICS OF SCR.**

- 3) SCR acts as a switch when it is forward biased.
- 4) When gate is open i.e.,  $I_G = 0$ , and anode voltage is applied junctions  $P_1 - N_1$  and  $P_2 - N_2$  are forward biased where  $N_1 - P_2$  is reverse biased. Only small reverse current flows.
- 5) If we increase anode voltage further, at one stage anode current increases suddenly and voltage across the SCR falls to holding voltage  $V_H$ .
- 6) Once SCR fires (conducts), it will remain in conduction till the current through the device is reduced less than  $I_H$ , adding current by reducing applied voltage (to less than holding voltage) close to zero.

## DEPARTMENT OF ECE

- 7) The firing angle can be varied by varying the Gate voltage. With very large positive (gate current break over may occur at very low voltage and SCR works as if it is a normal PN diode.

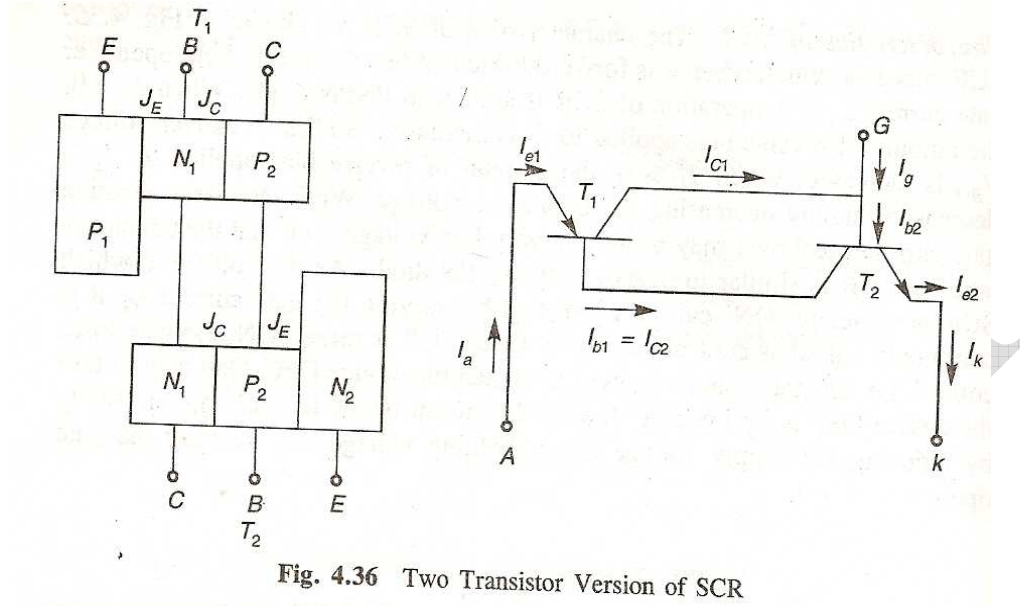
**TWO TRANSISTOR VERSION OF SCR.**

Fig. 4.36 Two Transistor Version of SCR

-  $T_1$  is PNP and  $T_2$  is NPN.

$$I_{b1} = I_A - I_{e1} = I_A - \alpha_1 I_A = I_A(1 - \alpha_1) \quad - \quad (1)$$

$$I_{b1} = I_{c2} \text{ and } I_{c2} = \alpha_2 I_K \quad - \quad (2)$$

$$I_{b1} = I_A(1 - \alpha_1) = \alpha_2 I_K \quad - \quad (3)$$

$$\text{We know } I_K = I_A + I_g. \quad (I_A = I_{c1} + I_{b1}) \quad - \quad (4)$$

Putting the value of  $I_K$  from eqn. (4) in eqn. (3)

$$I_A(1 - \alpha_1) - \alpha_2(I_A + I_g)$$

$$I_A(1 - \alpha_1) = \alpha_2(I_A + I_g)$$

$$I_A(1 - \alpha_1 - \alpha_2) = \alpha_2 I_g. \text{ Or } I_A = \left( \frac{\alpha_2 I_g}{1 - (\alpha_1 + \alpha_2)} \right) \quad - (5)$$

Equation 5 indicates that if  $(\alpha_1 + \alpha_2) = 1$ ,  $I_A = \infty$

- SCR is also called as Thyrister
- Latching current ( $I_L$ ) the min. current required to fire the device
- Holding current ( $I_H$ ) – min. current to keep the SCR conductivity
- Voltage safety factor  $V_f = \frac{PIV}{\sqrt{2} \text{ RMS of operating voltage.}}$

Value of  $V_f$  is 2 to 2.7.

## DEPARTMENT OF ECE

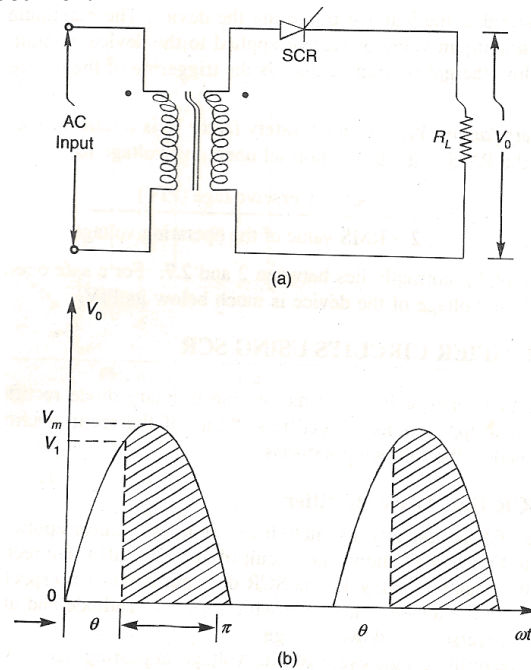
**SCR Half wave Rectifier.**

Fig. 4.37 SCR Half Wave Rectifier

SCR does not conduct during negative half cycle (like normal PN diode)

- Firing angle  $\theta$  depends on gate voltage
- Conduction angle is  $(\pi - \theta)$

**Average DC output**

$$\begin{aligned}
 V_{av} &= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \cdot d\omega t \\
 &= \frac{1}{2\pi} [-V_m \cos \omega t]_0^{\pi} \\
 &= \frac{1}{2\pi} [-V_m \cos \pi - \cos \theta] \\
 &= \frac{1}{2\pi} [-V_m (-1 - \cos \theta)] \\
 &= \frac{V_m}{2\pi} (1 + \cos \theta)
 \end{aligned}$$

**RMS VOLTAGE:**  $V_{RMS}$  is given by  $V_{RMS} = \frac{V_m}{2} \left[ \frac{1}{\pi} (\pi - \theta + \sin 2\theta) \right]^{1/2}$



## DEPARTMENT OF ECE

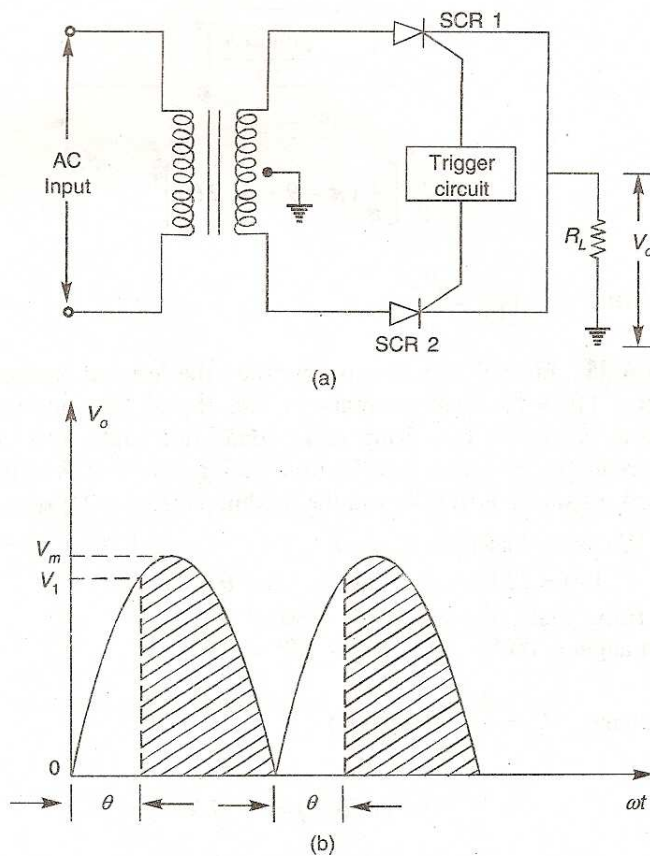
**SCR FULL WAVE RECTIFIER**

Fig. 4.38 SCR Full Wave Rectifier

$$V_{DC} = \frac{V_m}{\pi} (1 + \cos \theta)$$

- Q) An SCR FWR is connected to 250V, 50 Hz mains to supply ac voltage to resistive load of  $10 \Omega$  for firing angle of  $90^\circ$ . Find DC output voltage and load current.  
(May, 2000)

**Solution: -**

Given  $V_{RMS} = 230V$ ,  $R_L = 10\Omega$ ,  $\theta = 90^\circ$   
 $V_{DC} = ?$   $I_L = ?$

$$V_{RMS} = \frac{V_{max}}{\sqrt{2}}$$

$$V_{DC} = \frac{V_m}{\pi} (1 + \cos \theta)$$

## DEPARTMENT OF ECE

Or  $V_{\max} = V_{\text{RMS}} \sqrt{2} = 250\sqrt{2} = 353.6 \text{ volts}$

$$\frac{353.6}{\pi} (1 + \cos 90) = 112.6 \text{ volts}$$

$$I_L = \frac{V_{\text{DC}}}{R_L} = \frac{112.6}{10} = 11.26 \text{ Amps}$$

Q 2) A sinusoidal voltage  $V = 200 \sin 314 t$  is applied to an SCR whose forward break down voltage is 150V. Determine the time during which SCR remain off.

Solution: -

Given  $V_1 = 150\text{V}$ ,  $V_m = 200\text{V}$   
 $\omega = 314$   $\theta = ?$   $t = ?$

$$V_1 = V_m \sin \theta \quad \text{or} \quad \sin \theta = \frac{V_1}{V_m} = \frac{150}{200} = \frac{3}{4}$$


$$\theta = \sin^{-1} 3/4 = 48.6^\circ$$

$$T = 1/f \quad f = ? \quad \omega = 2\pi f = 314$$

$$T = 1/50 = 0.02 \text{ sec} = 20 \text{ m. sec.}$$

$$t = T \times \frac{\theta}{360} = 20 \times \frac{48.6}{360} = 2.7 \text{ m sec}$$
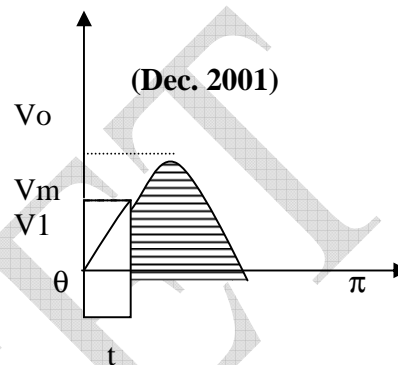
$$\text{or} \quad f = 314/2\pi = 50 \text{ Hz.}$$



Q 3) A half wave rectifier employing SCR is adjusted to have a gate current of 1mA and its forward breakdown voltage is 150V. If a sinusoidal voltage of 400V peak is applied, determine.

- i) Firing angle
  - ii) Average output voltage
  - iii) Average current for a load resistance of  $200\Omega$
  - iv) Power output.
- (Nov. 2002)

Given

$$V_1 = 150\text{V}, V_m = 400\text{V}, \theta = ? V_{\text{DC}} = ? I_{\text{DC}} = ? P_{\text{DC}} = ? R_L = 200\Omega$$

Solution: -

$$V_1 = V_m \sin \theta, \text{ or } \sin \theta = V_1 / V_m = 150/400 = 3/8 = 0.375.$$

$$\theta = \sin^{-1} 0.375 = 22^\circ.$$

$$V_{\text{DC}} = \frac{V_m}{2\pi} (1 + \cos \theta) = \frac{400}{2\pi} (1 + \cos 22^\circ) = \frac{400}{2\pi} (1.927) = 122.6 \text{ volts}$$


$$I_{\text{DC}} = \frac{V_{\text{DC}}}{R_L} = \frac{122.6}{200} = 0.613 \text{ Amps.}$$

$$P_{\text{DC}} = V_{\text{DC}} \cdot I_{\text{DC}} = 122.6 \times 0.613 = 75.15 \text{ Watts.}$$

## DEPARTMENT OF ECE

Color	Construction	Typical FWD Voltage (V)
Amber	Al In Ga P	2.1
Blue	Ga N	5.0
Green	Ga P	2.2
Orange	Ga As P	2.0
Red	Ga As P	1.8
White	Ga N	4.1
Yellow	Al In Ga P	2.1

- Reverse break down voltage of LED is very less – 3 to 5 volts
- LEDs are used for displays, including seven-segment display.

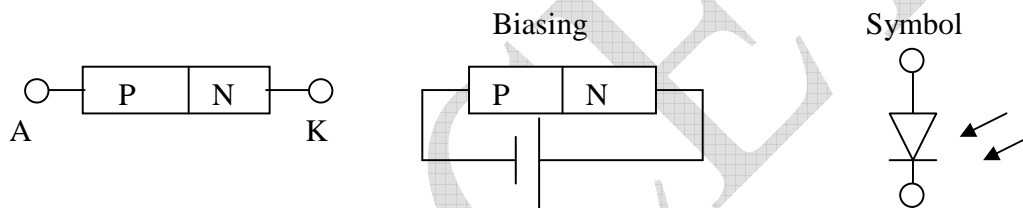**PHOTO DIODES:**


- Photo diode is always reverse biased
- When light falls on reverse biased junction, electrons are liberated and an EMF is available at the terminals, which leads to current through external load.

$$W = hf \text{ Joules}$$

$$1 \text{ Lumen} = 1.496 \times 10^{-10} \text{ watts}$$

- Current will be zero only for a positive voltage  $V_T$ .
- Current  $\propto$  luminous flux

application – signal detector, alarm systems.

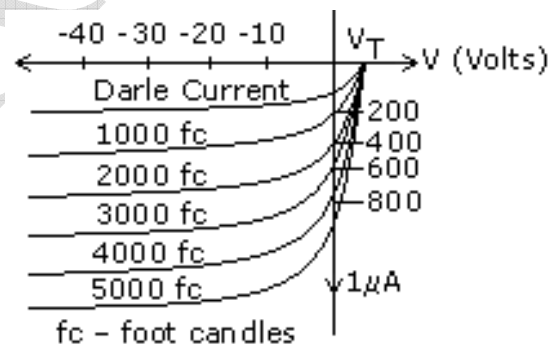**COMPARISON OF CB, CE, CC CONFIGURATIONS:**

Q) Summarize salient features of characteristics of BJT operating in CE, CB, CC configurations. (August 07)

(Auth: EDC by Salivahanam : P-112)

S. No.	Property	CB	CE	CC
1	Input Resistance	Low ( $\approx 100\Omega$ )	Moderate ( $\approx 750\Omega$ )	High ( $\approx 750k\Omega$ )
2	Output resistance	High ( $\approx 450k$ )	Moderate ( $\approx 45k$ )	Low ( $\approx 75\Omega$ )
3	Current gain	1	High	High
4	Voltage gain	$\approx 150$	$\approx 500$	$< 1$

## DEPARTMENT OF ECE

5	Phase shift between input and output voltages	0 or 360°	180°	0 or 360°
6	Applications	High frequency circuits	AF circuits	Impedance matching.

Q 1b) Calculate the values of  $I_E$ ,  $\beta_{dc}$  and  $\alpha_{dc}$  for a transistor with  $I_C = 13\mu A$ ,  $I_B = 200\mu A$ ,  $I_{CBO} = 6\mu A$ . Also determine the new level of  $I_C$  which will result in reducing  $I_B = 100\mu A$ .  
(August 07)

Solution: -

Given  $I_C = 13\mu A$  find  $I_C$ , when  $I_B = 100\mu A$   
 $I_B = 200\mu A$  PART - I  
 $I_{CBO} = 6\mu A$   $I_E = ?$   $\beta_{dc} = ?$   $\alpha_{dc} = ?$

**PART - I**

When  $I_B = 200\mu A$   $I_C$  cannot be  $13\mu A$ .

as  $I_C = \beta \times I_B$ .

Assume  $I_C = 13$  Amperes

$$\text{Then } \beta_{dc} = \frac{I_C}{I_B} = 13/200 \times 10^3 = 65$$

$$I_E = I_C + I_B \text{ or } I_E = 13 + 0.2 \text{ Amperes} = 13.2 \text{ Amperes}$$

$$\text{We can also use the formulae } I_E = \frac{1}{1-\alpha} I_{CBO} + \frac{1}{1-\alpha} I_B,$$

Which will also result  $I_C \approx 13.2$  Amperes.

$$\alpha_{dc} = \frac{I_C}{I_E} = \frac{13}{13.2} = 0.985$$

**PART - II**

$$I_C = \beta_{dc} \cdot I_B = 65 \times 200 \times 10^{-3} = 6.5 \text{ Amperes}$$

5. a) A transistor operating in CB configuration has  $I_C = 2.98 \text{ mA}$  in  $I_E = 3.00 \text{ mA}$  and  $I_{CO} = 0.01 \text{ mA}$ . What current will flow in the collector circuit of the transistor when connected in CE configuration with base current of  $30\mu A$  (May 2006)

**Solution:**

To find

Given  $I_C = 2.98 \text{ mA}$

If  $I_B = 30\mu A$ ,  $I_C = ?$

$I_E = 3 \text{ mA}$

$I_{CO} = 0.01 \text{ mA}$

$$I_C = \beta I_B + (\beta+1) I_{CO} \text{ and } \beta = \frac{\alpha}{1-\alpha}, \alpha = \frac{I_C}{I_E}$$

$$\alpha = \frac{2.98}{3.0} = 0.99 \quad \beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$$

$$I_C = 99 \times 30 \times 10^{-6} + (99+1) \times 0.01 \times 10^{-3} = 3970\mu A = 3.97 \text{ mA}.$$

## DEPARTMENT OF ECE

- 5(b) The reverse saturation current in a transistor is  $8\mu\text{A}$ . If the transistor common base current gain is 0.979, calculate the collector and emitter current for  $40\mu\text{A}$  base current.

(May 2006)

**Solution:**

Given  $I_{CO} = I_{CBO} = 8\mu\text{A}$   
 $\alpha = 0.979$

To find

 $I_C$  &  $I_E$  for  $I_B = 40\mu\text{A}$ 

$$I_E = \frac{1}{1-\alpha} I_{CBO} + \frac{1}{1-\alpha} I_B; \quad \frac{1}{1-\alpha} = \frac{1}{1-0.979} = 47.62$$

$$I_E = 47.62 \times 8 \times 10^{-6} + 47.62 \times 40 \times 10^{-6} = 2285 \times 10^{-6} = 2285\mu\text{A}$$

$$I_C = I_E - I_B = 2285 - 40 = 2245\mu\text{A}.$$

- Q 6b) Given an NPN transistor for which  $\alpha = 0.98$ ,  $I_{CO} = 2\mu\text{A}$  and  $I_{EO} = 1.6\mu\text{A}$ . A common emitter connection is used and  $V_{CC} = 12\text{V}$  and  $R_L = 4.0\text{K}$ . what is the minimum base current required in order that transistor enter into saturation region.

(Nov. 05)

**Solution:**Given  $\alpha = 0.98$  $I_{CO} = 2\mu\text{A}$  $I_{EO} = 1.6\mu\text{A}$  $V_{CC} = 12\text{V}$  $R_L = 4.0\text{K}$ .

To Find

 $I_B$  for  $I_{csat}$ 

When the transistor is in saturation  $I_C = I_{csat}$  and  $V_{CE}$  of ideal transistor = 0 volts.

$$I_{csat} = \frac{V_{cc}}{R_L} = \frac{12}{4000} = 3\text{mA}$$

$$I_B = \frac{I_C}{\beta} \text{ and } \beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = 49$$

$$I_B = \frac{3 \times 10^{-3}}{49} = 0.061\text{mA} \quad \text{Or} \quad 61\mu\text{A}.$$

- Q 9b) The current gain of a transistor in CE circuit is 49. Calculate CE gain and find base current where the emitter current in  $3\text{mA}$ .

**Solution**Given  $\beta = 49$ 

To find

 $\alpha = ?$  $I_B$  for  $I_E = 3\text{mA}$ .

## DEPARTMENT OF ECE


$$d = \frac{\beta}{1+\beta} = \frac{49}{1+49} = 0.98$$

$$I_E = (\beta+1) I_B \quad \text{or} \quad I_B = \frac{I_E}{1+\beta} = \frac{3 \times 10^{-3}}{1+49} = 60 \mu A$$

Q 1b) In the circuit shown if  $I_C = 2\text{mA}$  and  $V_{CE} = 3\text{V}$ . Calculate  $R_1$  and  $R_3$ .

May 07, Aug. 06, 07)

Solution: -

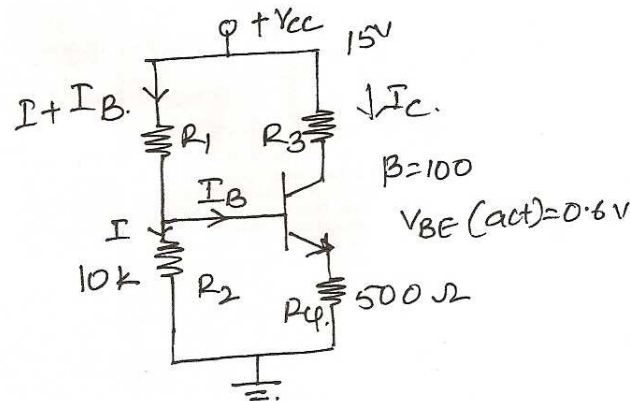

$$I_C = 2\text{mA} \text{ and } \beta = 100$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{100} = 200 \mu A$$

$$I_E = I_C + I_B = 2\text{mA} + 200 \mu A$$

$$= 2020 \mu A$$

$$V_E = I_E \cdot R_4 = 2020 \times 10^{-6} \times 500$$

$$V_E = 1.01 \text{ volts}$$

$$V_B = V_E + V_{BE} = 1.01 + 0.6 = 1.61 \text{ volts}$$

$$V_B = V_{R2} = 1.61 \text{ volts}$$

$$I = \frac{V_B}{R_2} = \frac{1.61}{10 \times 10^{-3}} = 0.161\text{mA} = 161 \mu A$$

$$V_{R1} = V_{CC} - V_{R2} = 15 - 1.61 = 13.39 \text{ volts}$$

$$R_1 = \frac{V_{R1}}{I + I_B} = \frac{13.39}{(161 + 20) \times 10^{-6}} = \frac{13.39}{181 \times 10^{-6}} = 73.97 \text{ k}\Omega$$

$$R_1 = 73.97 \text{ k}\Omega$$

$$V_{R3} = V_{CC} - V_{CE} - V_E = 15 - 3 - 1.01 = 10.99 \text{ volts}$$

$$R_3 = \frac{V_{R3}}{I_C} = \frac{10.99}{2 \times 10^{-3}} = 5.49 \text{ k}\Omega$$

$$R_3 = 5.49 \text{ k}\Omega.$$

## DEPARTMENT OF ECE

Q 3) For the JFET shown in the circuit with the voltage divider bias as shown below, calculate  $V_G$ ,  $V_S$ ,  $V_D$  and  $V_{DS}$  if  $V_{GS} = -2V$  (Sep. 2006)

Solution:

$$V_G = \frac{V_{DD} \cdot R_2}{R_1 + R_2} = \frac{15 \times 4K}{(12 + 4)k} = \frac{15}{4} = 3.75V$$

Since gate current is negligible voltage drop

Across  $R_G = 0$

$$V_{GS} = V_G - I_{DRL} \cdot R_S$$

$$-2V = 3.75 - I_{DRL} \cdot 1K$$

$$I_{DRL} = \frac{3.75 + 2}{1K} = 5.75mA$$

$$I_D = I_{DRL} = 5.75mA$$

$$V_{DS} = V_{DD} - I_{DRL} \cdot (R_D + R_S) = 15 - 5.75 \times 10^{-3} \times 1500 = 6.375V$$

$$V_D = V_{DD} - I_{DRL} \cdot R_D = 15 - 5.75 \times 10^{-3} \times 500 = 12.125V$$

$$V_{DS} = V_{DD} - I_{DRL} \cdot R_D - I_{DRL} \cdot R_S = 15 - 2.875 - 5.75 = 6.375V$$

$$V_D = V_{DD} - I_{DRL} \cdot R_D = 15 - 2.875 = 12.125V$$

## COMPARISON OF MOS FET WITH JFET

- 1) In JFET, the transverse electric field across the reverse biased P N junction controls the conductivity of the channel. In FET Transverse electric field is induced across the insulating layer.
- 2) Input impedance of MOS FET is much higher ( $10^{10}$  to  $10^{15} \Omega$ ) compared to that of JFET ( $10^8 \Omega$ ) because gate is insulated from channel.
- 3) The output characteristics of JFET are flatter than that of MOS FET because drain resistance of JFET is much higher than MOS FET.
- 4) JFET is operated in depletion mode only where as MOSFET can be operated in depletion and enhancement mode.
- 5) MOSFET are easier to fabricate than JFET
- 6) MOSFETs are easily get damaged due to static charge
- 7) In MOSFET source and drain can be interchanged
- 8) CMOSFETs dissipates very low power
- 9) MOS FETs are widely used in VLSI.

