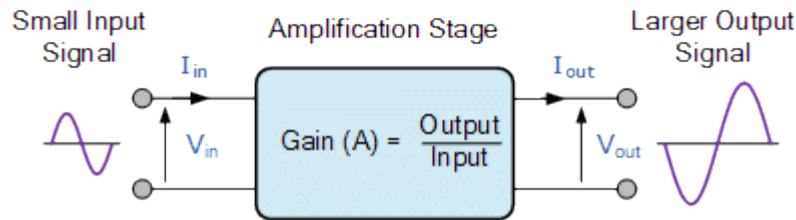


## Introduction to the Amplifier

An amplifier is an electronic device or circuit which is used to increase the magnitude of the signal applied to its input



**Amplifier** is the generic term used to describe a circuit which produces an increased version of its input signal. Amplifier circuits are different and they are classified according to their circuit configurations and modes of operation.

Generally, amplifiers can be sub-divided into two distinct types depending upon their power or voltage gain. One type is called the **Small Signal Amplifier** which include pre-amplifiers, instrumentation amplifiers etc. Small signal amplifiers are designed to amplify very small signal voltage levels of only a few micro-volts ( $\mu\text{V}$ ) from sensors or audio signals.

The other type are called **Large Signal Amplifiers** such as audio power amplifiers or power switching amplifiers. Large signal amplifiers are designed to amplify large input voltage signals or switch heavy load currents as you would find driving loudspeakers.

In general the classification of an amplifier depends upon the size of the signal, large or small, its physical configuration and how it processes the input signal

The type or classification of an Amplifier is given in the following table.

### Classification of Signal Amplifier

Type of Signal	Type of configuration	Classification	Frequency of operation
Small	Common Emitter	Class A	DC Current
Large	Common Base	Class B	Audio frequency(AF)
	Common collector	Class AB	Radio frequency(RF)
	---do----	Class C	HF,UHF &SHF

### Important Points to remember:

An ideal signal amplifier will have three main properties: Input Resistance or ( $R_{IN}$ ), Output Resistance or ( $R_{OUT}$ ) and of course amplification known commonly as Gain or (A).

### Voltage Amplifier Gain

$$\text{Voltage Gain } (A_v) = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{V_{out}}{V_{in}}$$

### Current Amplifier Gain

$$\text{Current Gain } (A_i) = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_{out}}{I_{in}}$$

### Power Amplifier Gain

$$\text{Power Gain } (A_p) = A_v \times A_i$$

Note that for the Power Gain you can also divide the power obtained at the output with the power obtained at the input. Also when calculating the gain of an amplifier, the subscripts v, i and p are used to denote the type of signal gain being used.

The power gain ( $A_p$ ) or power level of the amplifier can also be expressed in **Decibels, (dB)**. The Bel (B) is a logarithmic unit (base 10) of measurement that has no units. Since the Bel is too large a unit of measure, it is prefixed with *deci* making it **Decibels** instead with one decibel being one tenth (1/10th) of a Bel. To calculate the gain of the amplifier in Decibels or dB, we can use the following expressions.

- Voltage Gain in dB:  $a_v = 20 \cdot \log(A_v)$
- Current Gain in dB:  $a_i = 20 \cdot \log(A_i)$
- Power Gain in dB:  $a_p = 10 \cdot \log(A_p)$

Note that the DC power gain of an amplifier is equal to ten times the common log of the output to input ratio, where as voltage and current gains are 20 times the common log of the ratio. Note however, that 20dB is not twice as much power as 10dB because of the log scale.

### Amplifier Example

Determine the Voltage, Current and Power Gain of an amplifier that has an input signal of 1mA at 10mV and a corresponding output signal of 10mA at 1V. Also, express all three gains in decibels, (dB).

The Various Amplifier Gains:

$$A_v = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{1}{0.01} = 100$$

$$A_i = \frac{\text{Output Current}}{\text{Input Current}} = \frac{10}{1} = 10$$

$$A_p = A_v \times A_i = 100 \times 10 = 1,000$$

Amplifier Gains given in Decibels (dB):

$$a_v = 20 \log A_v = 20 \log 100 = 40 \text{ dB}$$

$$a_i = 20 \log A_i = 20 \log 10 = 20 \text{ dB}$$

$$a_p = 10 \log A_p = 10 \log 1000 = 30 \text{ dB}$$

Then the amplifier has a Voltage Gain, ( $A_v$ ) of 100, a Current Gain, ( $A_i$ ) of 10 and a Power Gain, ( $A_p$ ) of 1,000

### **Ideal Amplifier**

We can now specify the characteristics for an ideal amplifier from our discussion above with regards to its **Gain**, meaning voltage gain:

- The amplifiers gain, ( $A$ ) should remain constant for varying values of input signal.
- Gain is not be affected by frequency. Signals of all frequencies must be amplified by exactly the same amount.
- The amplifiers gain must not add noise to the output signal. It should remove any noise that is already exists in the input signal.
- The amplifiers gain should not be affected by changes in temperature giving good temperature stability.
- The gain of the amplifier must remain stable over long periods of time.

### Definition and distinction or details of class of amplifiers.

- Amplifier classification takes into account the portion of the input signal in which the output transistor conducts as well as determining both the efficiency and the amount of power that the switching transistor both consumes and dissipates in the form of wasted heat.


#### The most commonly used being:

- Class A Amplifier – has low efficiency of less than 40% but good signal reproduction and linearity.
- Class B Amplifier – is twice as efficient as class A amplifiers with a maximum theoretical efficiency of about 70% because the amplifying device only conducts (and uses power) for half of the input signal.
- Class AB Amplifier – has an efficiency rating between that of Class A and Class B but poorer signal reproduction than Class A amplifiers.
- Class C Amplifier – is the most efficient amplifier class but distortion is very high as only a small portion of the input signal is amplified therefore the output signal bears very little resemblance to the input signal. Class C amplifiers have the worst signal reproduction.

### **Class A Amplifier Operation**

**Class A Amplifier** operation is where the entire input signal waveform is faithfully reproduced as the transistor is perfectly biased within its active region. This means that the switching transistor is never driven into its cut-off or saturation regions. The result is that the AC input signal is perfectly “centred” between the amplifiers upper and lower signal limits as shown below.

### Class A Amplifier Output Waveform

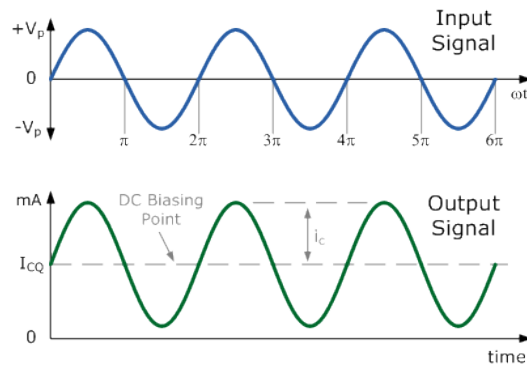

A Class-A amplifier configuration uses the same switching transistor for both halves of the output waveform and due to its central biasing arrangement, the output transistor always has a constant DC biasing current, ( $I_{CQ}$ ) flowing through it, even if there is no input signal present. In other words the output transistors never turns “OFF” and is in a permanent state of idle. hence it requires a heat sink as DC is lost as heat.


### Class B Amplifier Operation

The **Class-B Amplifier** uses two complimentary transistors (either an NPN and a PNP or a NMOS and a PMOS) to amplify each half of the output waveform.

One transistor conducts for only one-half of the signal waveform while the other conducts for the other or opposite half of the signal waveform. This means that each transistor spends half of its time in the active region and half its time in the cut-off region thereby amplifying only 50% of the input signal.

Therefore with zero input signal there is zero output. As only half the input signal is presented at the amplifiers output this improves the amplifier efficiency over the previous Class-A configuration as shown below.

### Class B Amplifier Output Waveform

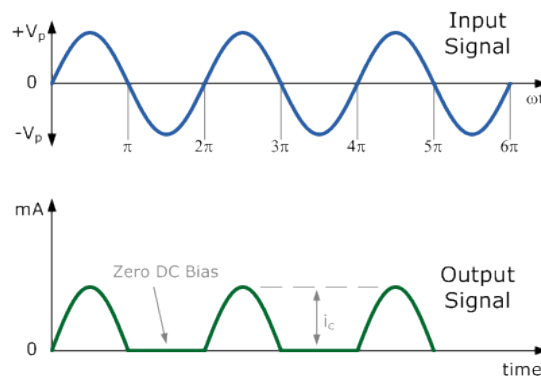


### Class AB Amplifier Operation

The **Class-AB Amplifier** is a compromise between the Class-A and the Class-B configurations above. While Class-AB operation still uses two complementary transistors in its output stage a very small biasing voltage is applied to the Base of each transistor to bias them close to their cut-off region when no input signal is present.

An input signal will cause the transistor to operate as normal within its active region, eliminating any crossover distortion which is always present in the class-B configuration. A small biasing Collector current ( $I_{CQ}$ ) will flow through the transistor when there is no input signal present, but generally it is much less than that for the Class-A amplifier configuration.

Thus each transistor is conducting, "ON" for a little more than half a cycle of the input waveform. The small biasing of the Class-AB amplifier configuration improves both the efficiency and linearity of the amplifier circuit compared to a pure Class-A configuration above.

### Class AB Amplifier Output Waveform

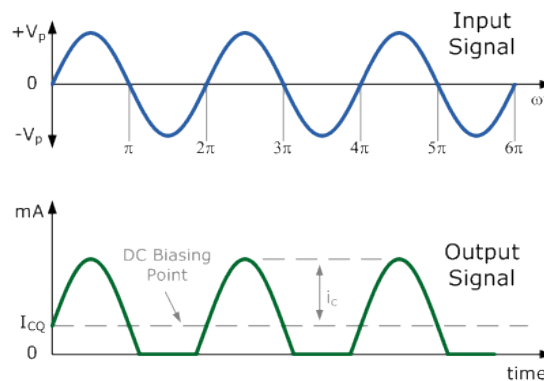

Here we can make a comparison between the most common types of amplifier classifications in the following table.

### Power Amplifier Classes

Class	A	B	C	AB
Conduction Angle	$360^\circ$	$180^\circ$	Less than $90^\circ$	$180$ to $360^\circ$
Position of the Q-point	Centre Point of the Load Line	Exactly on the X-axis	Below the X-axis	In between the X-axis and the Centre Load Line

Overall Efficiency	Poor 25 to 30%	Better 70 to 80%	Higher than 80%	Better than A but less than B 50 to 70%
Signal Distortion	None if Correctly Biased	At the X-axis Crossover Point	Large Amounts	Small Amounts

OPTIONAL(Badly designed amplifiers especially the Class "A" types may also require larger power transistors, more expensive heat sinks, cooling fans, or even an increase in the size of the power supply required to deliver the extra wasted power required by the amplifier. Power converted into heat from transistors, resistors or any other component for that matter, makes any electronic circuit inefficient and will result in the premature failure of the device.

So why use a Class A amplifier if its efficiency is less than 40% compared to a Class B amplifier that has a higher efficiency rating of over 70%. Basically, a Class A amplifier gives a much more linear output meaning that it has, **Linearity** over a larger frequency response even if it does consume large amounts of DC power.)

In this **Introduction to the Amplifier** tutorial, we have seen that there are different types of amplifier circuit each with its own advantages and disadvantages. In the next tutorial about amplifiers, we will look at the most commonly connected type of transistor amplifier circuit, the common emitter amplifier. Most transistor amplifiers are of the Common Emitter or CE type circuit due to their large gains in voltage, current and power as well as their excellent input/output characteristics.

## **UNIT III**

### **BJT AMPLIFIERS**

BJT h-parameter model

Analysis of transistor amplifier using h-parameter model

CB, CE and CC amplifiers

Comparison of CB, CE and CC configurations

Simplified h-parameter model






# BJT AMPLIFIERS
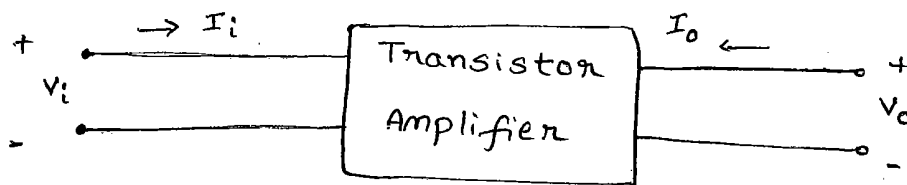
## H-Parameter Representation of a Transistor

A transistor can be treated as a two-port network



Hence  $I_i$  = Input current to the Amplifier

$V_i$  = Input voltage to the Amplifier

$I_o$  = output current of the Amplifier

$V_o$  = output voltage of the Amplifier

Transistor is a current operated device.

Hence input voltage  $V_i$  and output current  $I_o$  are the dependent variables.

Input current  $I_i$  and output voltage  $V_o$  are Independent variables.

$$V_i = f_1(I_i, V_o)$$

$$I_o = f_2(I_i, V_o)$$

This can be written in the equation form as follows

$$V_i = h_{11} I_i + h_{12} V_o$$

$$I_o = h_{21} I_i + h_{22} V_o$$

The above equation can also be written using alphabetic notations

$$V_i = h_i I_i + h_r V_o$$

$$I_o = h_f I_i + h_o V_o$$

### Definitions of h-Parameter:

The parameters in the above equation are defined as follows

$$h_{11} = h_i = \left. \frac{V_i}{I_i} \right|_{V_o=0} = \text{Input resistance with output short circuited.}$$

$$h_{12} = h_r = \left. \frac{V_i}{I_o} \right|_{I_i=0} = \text{Reverse voltage transfer ratio with input open circuited.}$$

$$h_{21} = h_f = \left. \frac{I_o}{I_i} \right|_{V_o=0} = \text{Short circuit } \overset{\text{Forward}}{\text{current gain}} \text{ with output short circuited.}$$

$$h_{22} = h_o = \left. \frac{I_o}{V_o} \right|_{I_i=0} = \text{output Admittance with input open circuited.}$$

### BJT H-parameter Model:


Based on the definition of hybrid parameters the mathematical model for two port networks known as h-parameter model (Hybrid Parameter model) can be developed.

The two equations of a transistor is given by

$$V_i = h_i I_i + h_r V_o$$

$$I_o = h_f I_i + h_o V_o$$

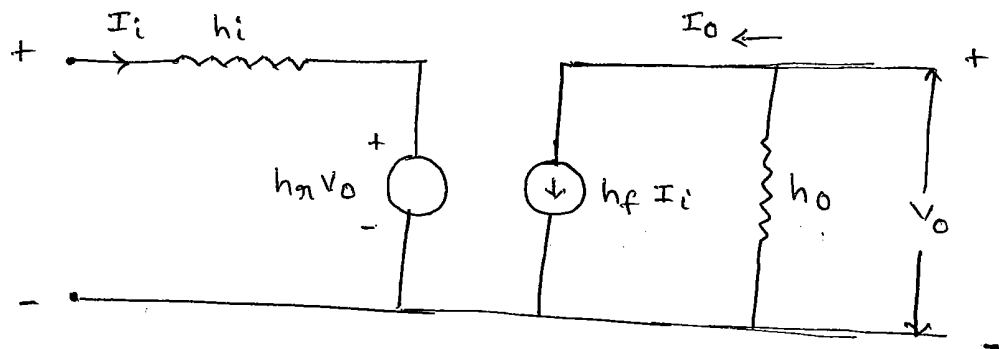Based on above two equations the equivalent circuit on Hybrid Model for transistor can be drawn.



### Advantages (or) Benefits of h-parameters

- 1) Real numbers at audio frequencies
- 2) Easy to measure
- 3) can be obtained from the transistor static characteristic curves.
- 4) convenient to use in circuit analysis and design.
- 5) Easily convertible from one configuration to other
- 6) Most of the transistor manufacturers specify the h-parameters.

### h parameter Model for CE configuration

Let us consider the common emitter configuration shown in figure below. The variables  $I_b$ ,  $I_c$ ,  $V_b$  and  $V_c$  represent total instantaneous currents and voltages.

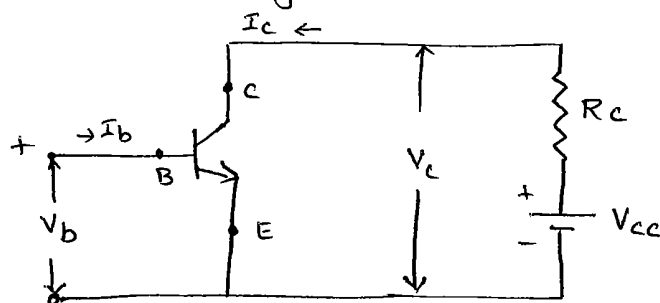


Fig: simple common emitter configuration


Here  $I_b$  - Input current

$V_b$  - Input voltage

$I_c$  - output current

$V_c$  - output voltage

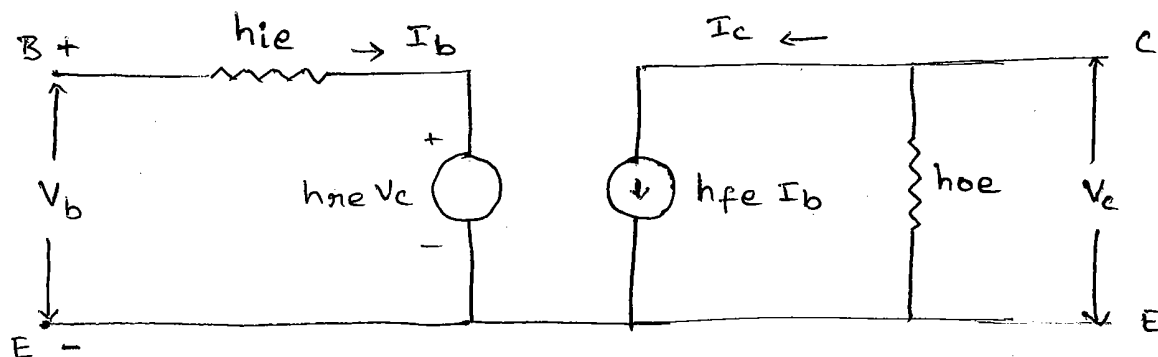h-parameter model for common emitter configuration is shown in figure below.



$$V_b = h_{ie} I_b + h_{ne} V_c$$

$$I_c = h_{fe} I_b + h_{oe} V_c$$


where 
$$h_{ie} = \left. \frac{\Delta V_B}{\Delta I_B} \right|_{V_c = \text{constant}} = \left. \frac{V_b}{I_b} \right|_{V_c = \text{constant}}$$

$$h_{ne} = \left. \frac{\Delta V_B}{\Delta V_c} \right|_{I_B = \text{constant}} = \left. \frac{V_b}{V_c} \right|_{I_b = \text{constant}}$$

$$h_{fe} = \left. \frac{\Delta I_c}{\Delta I_B} \right|_{V_c = \text{constant}} = \left. \frac{i_c}{i_b} \right|_{V_c = \text{constant}}$$



$$h_{oe} = \left. \frac{\Delta I_c}{\Delta V_c} \right|_{I_B = \text{constant}} = \left. \frac{i_c}{V_c} \right|_{I_b = \text{constant}}$$
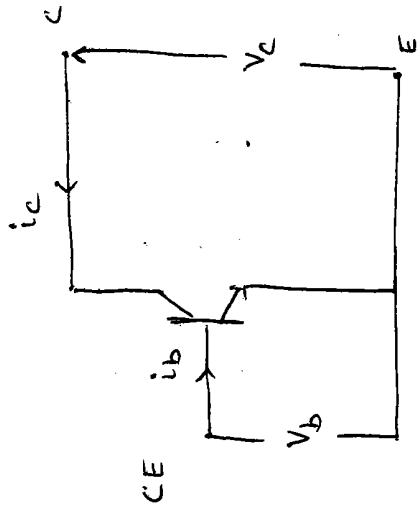
# Hybrid model for the transistor in three different configurations





$$V_b = h_{ie} i_b + h_{re} V_c$$

$$i_c = h_{fe} i_b + h_{oe} V_c$$

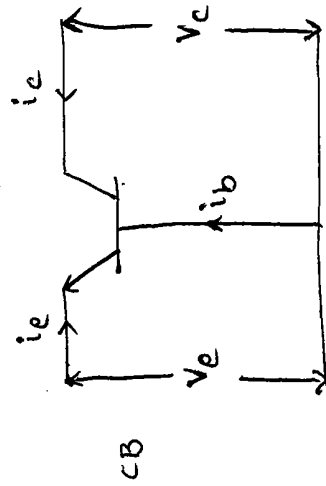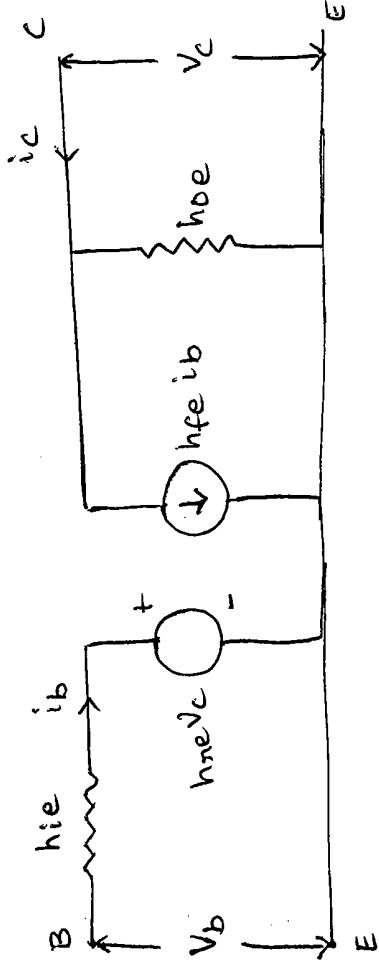


$$V_e = h_{ib} i_e + h_{rb} V_c$$

$$i_c = h_{fb} i_e + h_{ob} V_c$$

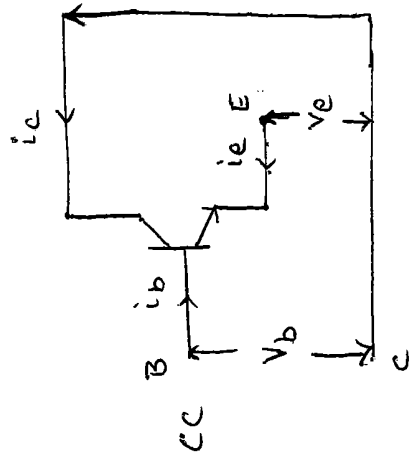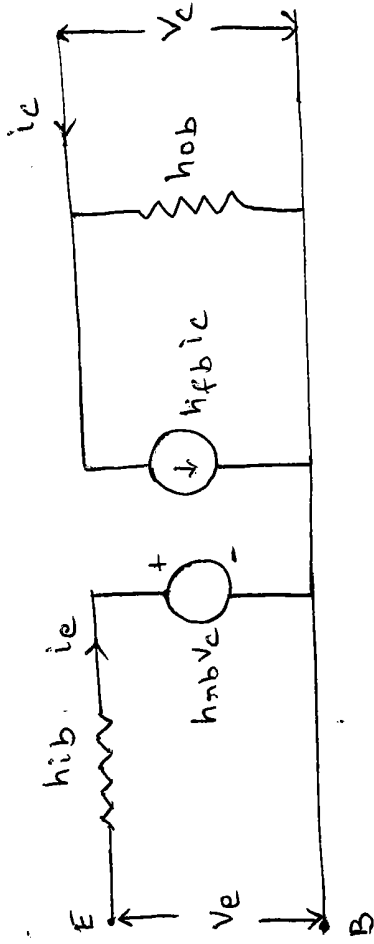

$$V_b = h_{ic} i_b + h_{rc} V_e$$

$$i_e = h_{fc} i_b + h_{oc} V_e$$

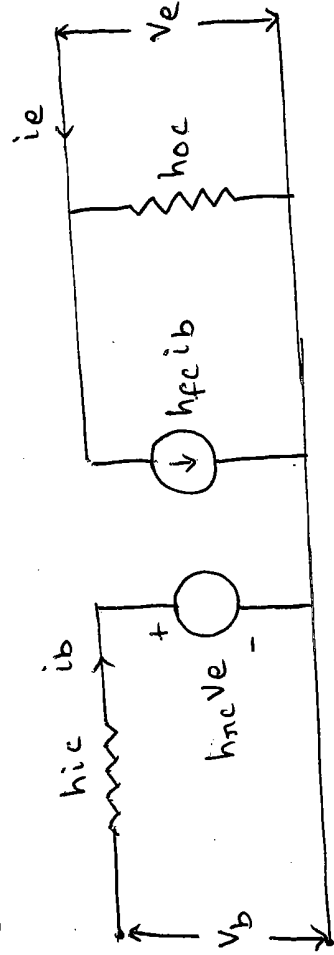


## Typical h-parameter values for a transistor

Parameter	CE	CC	CB
$h_i$	$1100\Omega$	$1100\Omega$	$22\Omega$
$h_r$	$2.5 \times 10^{-4}$	1	$3 \times 10^{-4}$
$h_{fe}$	50	-51	-0.98
$h_o$	$25\mu A/V$	$25\mu A/V$	$0.49\mu A/V$
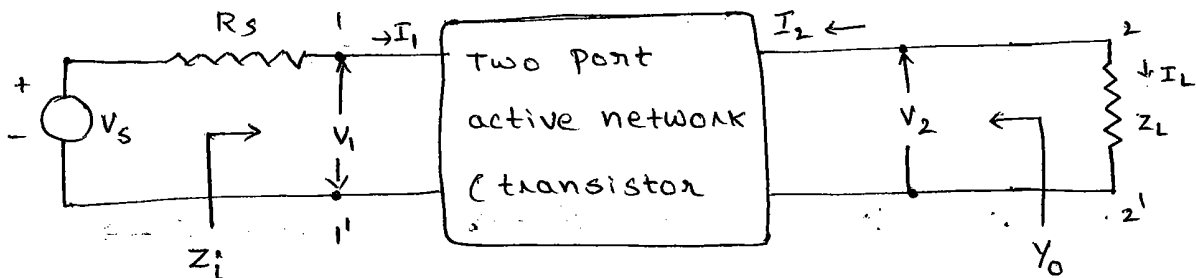
## Analysis of a transistor amplifier circuit using h-parameter model.

A transistor amplifier can be constructed by connecting an external load and signal source as indicated in figure below. and biasing the transistor properly.



The hybrid parameter model for above network is shown in figure below.

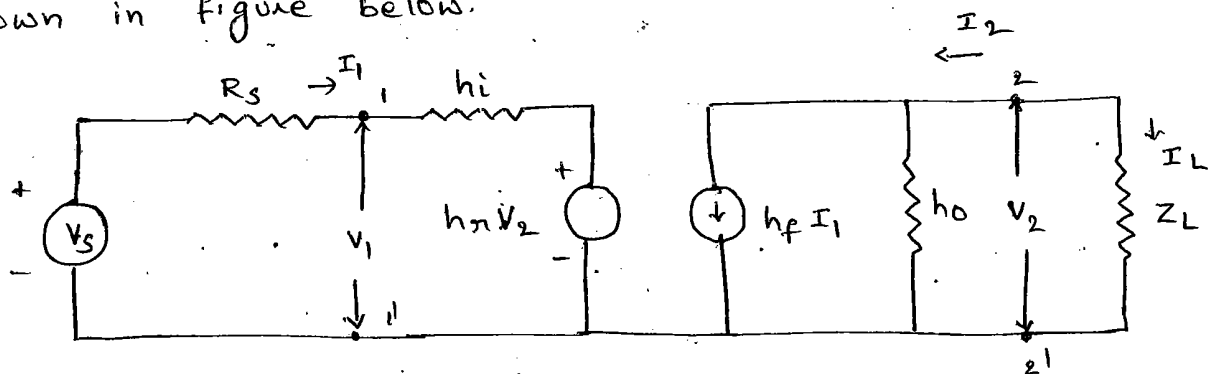


Fig: Transistor hybrid parameter model.

## 1) Current Gain (or) Current Amplification $A_I$ :

For a transistor amplifier the current gain  $A_I$  is defined as the ratio of output current to input current.

$$A_I = \frac{I_L}{I_1} = -\frac{I_2}{I_1}$$

From the circuit  $I_2 = h_f I_1 + h_o V_2 \rightarrow (1)$

$$V_2 = I_L Z_L = -I_2 Z_L \rightarrow (2)$$

Sub (2) in (1)

$$I_2 = h_f I_1 - I_2 Z_L h_o$$

$$I_2 + I_2 Z_L h_o = h_f I_1$$

$$I_2 (1 + Z_L h_o) = h_f I_1 \Rightarrow \frac{I_2}{I_1} = \frac{h_f}{1 + Z_L h_o}$$

$$A_I = \frac{-I_2}{I_1} = \frac{-h_f}{1 + Z_L h_o}$$

	<u>CE</u>	<u>CB</u>	<u>CC</u>
$A_I$	$\frac{-h_{fe}}{1 + Z_L h_{oe}}$	$\frac{-h_{fb}}{1 + Z_L h_{ob}}$	$\frac{-h_{fc}}{1 + Z_L h_{oc}}$

## 2) Input Impedance $z_i$

In the circuit  $R_s$  is the signal source resistance. The impedance seen when looking in to the amplifier terminals (1, 1') is the amplifier input impedance  $z_i$ .

$$z_i = \frac{V_1}{I_1}$$

From figure  $V_1 = h_i I_1 + h_{re} V_2$

$$\text{So } Z_i = \frac{h_i I_1 + h_r V_2}{I_1} = h_i + h_r \frac{V_2}{I_1} \rightarrow \textcircled{1}$$

$$V_2 = -I_2 Z_L = A_I I_1 Z_L \quad \left[ \because A_I = \frac{-I_2}{I_1} \right]$$

$$\textcircled{1} \Rightarrow Z_i = h_i + h_r \frac{A_I I_1 Z_L}{I_1}$$

$$Z_i = h_i + h_r A_I Z_L$$

$$Z_i = h_i - h_r Z_L \frac{h_f}{1 + h_o Z_L} \quad \left[ \because A_I = \frac{-h_f}{1 + h_o Z_L} \right]$$

$$Z_i = h_i - \frac{h_f h_r}{\frac{1}{Z_L} + h_o}$$

$$Z_i = h_i - \frac{h_f h_r}{Y_L + h_o} \quad \left[ \because Y_L = \frac{1}{Z_L} \right]$$

	<u>CE</u>	<u>CB</u>	<u>CC</u>
$Z_i$	$h_{ie} - \frac{h_{fe} h_{re}}{Y_L + h_{oe}}$	$h_{ib} - \frac{h_{fb} h_{rb}}{Y_L + h_{ob}}$	$h_{ic} - \frac{h_{fc} h_{rc}}{Y_L + h_{oc}}$

3) voltage gain ( $A_V$ ):

The ratio of output voltage  $V_2$  to input voltage gives the voltage gain of the transistor

$$A_V = \frac{V_2}{V_1}$$

$$\text{Substituting } V_2 = -I_2 Z_L = A_I I_1 Z_L$$

$$\Rightarrow A_V = \frac{A_I I_1 Z_L}{V_1} = \frac{A_I Z_L}{V_1 / I_1} = \frac{A_I Z_L}{Z_i}$$

	<u>CE</u>	<u>CB</u>	<u>CC</u>
$A_V$	$\frac{A_I Z_L}{Z_i}$	$\frac{A_I Z_L}{Z_i}$	$\frac{A_I Z_L}{Z_i}$



4) output Admittance ( $Y_0$ ) :

$$Y_0 = \frac{I_2}{V_2} \quad \text{with } V_s = 0 \quad \text{and } R_L = \infty$$

from the circuit  $I_2 = h_f I_1 + h_o V_2$

$$\text{Dividing by } V_2, \quad \frac{I_2}{V_2} = h_f \frac{I_1}{V_2} + h_o \rightarrow \textcircled{1}$$

with  $V_s = 0$ , by KVL in input circuit

$$R_s I_1 + h_i I_1 + h_r V_2 = 0$$

$$I_1 (R_s + h_i) + h_r V_2 = 0$$

$$\text{Hence } \frac{I_1}{V_2} = - \frac{h_r}{R_s + h_i}$$

$$\text{now Eq } \textcircled{1} \Rightarrow \frac{I_2}{V_2} = - \frac{h_f h_r}{R_s + h_i} + h_o$$

$$\Rightarrow Y_0 = h_o - \frac{h_f h_r}{R_s + h_i}$$

CE

CB

CC


$$Y_0 \quad h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}}$$

$$h_{ob} - \frac{h_{fb} h_{rb}}{R_s + h_{ib}}$$

$$h_{oc} - \frac{h_{fc} h_{rc}}{R_s + h_{ic}}$$

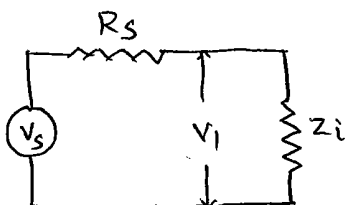5) Voltage gain ( $A_{V_s}$ ) (Including source) :

$$A_{V_s} = \frac{V_2}{V_s} = \frac{V_2}{V_1} \frac{V_1}{V_s} \Rightarrow A_{V_s} = A_V \frac{V_1}{V_s}$$



$$V_1 = \frac{V_s Z_i}{R_s + Z_i} \Rightarrow \frac{V_1}{V_s} = \frac{Z_i}{R_s + Z_i}$$

$$\text{now } A_{V_s} = \frac{A_V Z_i}{R_s + Z_i}$$

$$A_{VS} = \frac{A_I R_L}{Z_i} \times \frac{Z_i}{R_S + Z_i} = \frac{A_I R_L}{R_S + Z_i}$$


if  $R_S = 0$  then  $A_{VS} = \frac{A_I R_L}{Z_i} = A_V$

## 6) Current Amplification ( $A_{IS}$ )

$$A_{IS} = \frac{-I_2}{I_S} = \frac{-I_2}{I_1} \cdot \frac{I_1}{I_S} = A_I \frac{I_1}{I_S}$$

The modified input circuit using Norton's equivalent circuit for the source for the calculation of  $A_{IS}$

$$A_{IS} = A_I \frac{R_S}{R_S + Z_i}$$

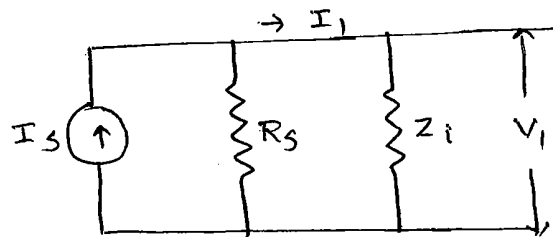

$$A_{VS} = \frac{A_{IS} Z_L}{R_S}$$

## ⇒ In CE configuration

Current Gain  $A_I = \frac{-h_{fe}}{1 + h_{oe} Z_L} \quad [Z_L = R_L]$

Input Impedance  $Z_i = h_{ie} - \frac{h_{fe} h_{ne}}{Y_L + h_{oe}} \quad [Y_L = \frac{1}{Z_L} = \frac{1}{R_L}]$

Voltage Gain  $A_V = A_I \frac{Z_L}{Z_i}$

Output Admittance  $Y_o = h_{oe} - \frac{h_{fe} h_{ne}}{h_{ie} + R_S}$

## ⇒ In CB configuration

Current Gain  $A_I = \frac{-h_{fb}}{1 + h_{ob} Z_L}$

Input Impedance  $Z_i = h_{ib} - \frac{h_{fb} h_{nb}}{Y_L + h_{ob}}$

Voltage Gain  $A_V = A_I \frac{Z_L}{Z_i}$

Output Admittance  $Y_o = h_{ob} - \frac{h_{fb} h_{nb}}{h_{ib} + R_S}$

⇒ In CC configuration

$$\text{Current gain } A_I = \frac{-h_{fe}}{1 + h_{oc} Z_L}$$

$$\text{Input Impedance } Z_i = h_{ie} - \frac{h_{fe} h_{rc}}{Y_L + h_{oc}}$$

$$\text{Voltage gain } A_v = \frac{A_I Z_L}{Z_i}$$

$$\text{Output Admittance } Y_o = h_{oc} - \frac{h_{fe} h_{rc}}{h_{ie} + R_s}$$

Conversion formulae for hybrid parameters

CB

CC

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}}$$

$$h_{ic} = h_{ie}$$

$$h_{rb} = \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{rc}$$

$$h_{rc} = 1$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$h_{fc} = -(1 + h_{fe})$$

$$h_{ob} = \frac{h_{oe}}{1 + h_{fe}}$$

$$h_{oc} = h_{oe}$$

1) characteristics of common emitter Amplifier

1) Current gain  $A_I$  is high for  $R_L < 10k\Omega$

2) The voltage gain is high for normal values of Load resistance  $R_L$

3) The input resistance  $R_i$  is medium

4) The output resistance  $R_o$  is moderately high

### Applications of common emitter amplifier :

1. of the three configurations CE amplifier alone is capable of providing both voltage gain and current gain.
2. The output resistance  $R_o$  and input resistance  $R_i$  are moderately high
3. CE amplifier is widely used for Amplification purpose

### 2) characteristics of common Base Amplifier :

1. current gain is less than unity and its magnitude decreases with the increase of load resistance  $R_L$
2. voltage gain  $A_v$  is high for normal values of  $R_L$
3. The input resistance  $R_i$  is the lowest of all the three configurations.
4. The output resistance  $R_o$  is the highest of all the three configurations.

### Applications of common base Amplifier

The CB Amplifier is not commonly used for Amplification purpose. It is used for

- 1) Matching a very low impedance source.
- 2) As a non inverting amplifier with voltage gain exceeding unity
- 3) For driving a high impedance load
- 4) As a constant current source.

### 3) characteristics of common collector Amplifier

1. For low value of  $R_L$  ( $< 10k\Omega$ ) the current gain  $A_i$  is high and almost equal to that of a CE amplifier

2. The voltage gain  $A_v$  is less than unity.
3. The input resistance is the highest of all the three configurations.
4. The output resistance is the lowest of all the three configurations.

### Applications of common collector Amplifier:

1. The CC Amplifier is widely used as a buffer stage between a high impedance source and low impedance load. (CC Amplifier is called emitter follower)

### Comparison of Transistor Amplifier Configurations.

The characteristics of three configurations are summarized in table below. Here the quantities  $A_I$ ,  $A_v$ ,  $R_i$ ,  $R_o$  and  $A_p$  (Power gain) are calculated for  $R_L = R_s = 3\text{ k}\Omega$

Quantity	CB	CC	CE
$A_I$	0.98	47.5	-46.5
$A_v$	131	0.989	-131
$A_p$	128.38	46.98	6091.5
$R_i$	22.6 $\Omega$	144 $\text{k}\Omega$	1065 $\Omega$
$R_o$	1.72 $\text{M}\Omega$	80.5 $\Omega$	45.5 $\text{k}\Omega$

## Simplified CE Hybrid Model (or) Approximate CE

### Hybrid model (Approximate Analysis):

As the  $h$  parameters themselves vary widely for the same type of transistor, it is justified to make approximations and simplify the expressions for  $A_I$ ,  $A_v$ ,  $A_p$ ,  $R_i$  and  $R_o$ .

The behaviour of the transistor circuit can be obtained by using the simplified hybrid model. The  $h$ -parameter equivalent circuit of the transistor in the CE configuration is shown in figure below.

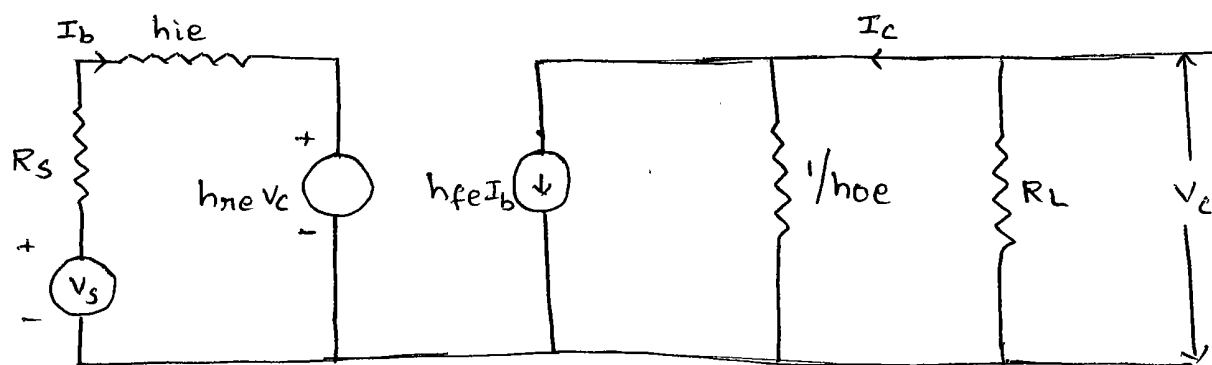


Fig: Exact CE Hybrid Model.

Here  $\frac{1}{h_{oe}}$  is in parallel with  $R_L$

The parallel combination of two unequal impedances is approximately equal to the lower value i.e.  $R_L$ . Hence if  $\frac{1}{h_{oe}} \gg R_L$ , then the term  $h_{oe}$  may be neglected

provided that  $h_{oe} R_L \ll 1$

If  $h_{oe}$  is omitted, the collector current  $I_c$  is given by

$$I_c = h_{fe} I_b$$

under this condition the magnitude of voltage generated in the emitter circuit is

$$h_{ne} |V_c| = h_{ne} I_c R_L = h_{ne} h_{fe} I_b R_L$$

since  $h_{ne} h_{fe} \approx 0.01$ , this voltage may be neglected in comparison with the voltage drop across  $h_{ie}$ . ie  $h_{ie} I_b$  provided that  $R_L$  is not too large. ie if the load resistance  $R_L$  is small it is possible to neglect the parameter  $h_{ne}$  and:  $h_{oe}$  and the approximate equivalent circuit is obtained as shown in figure below.

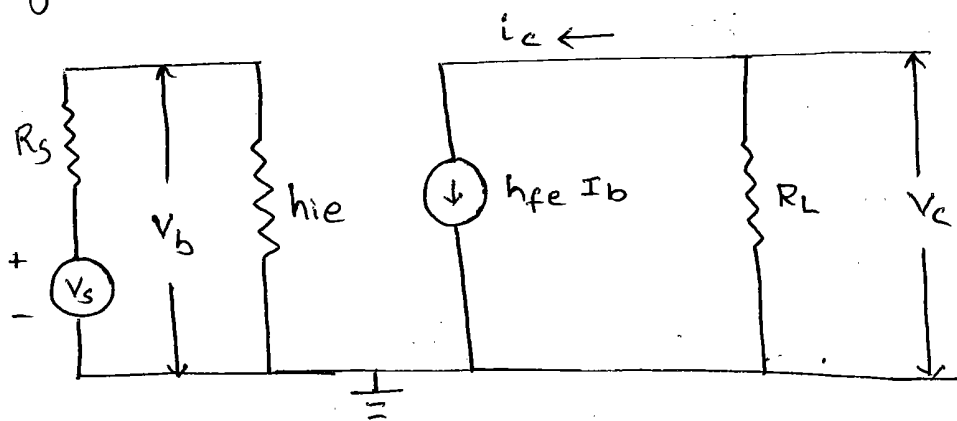


Fig: Approximate CE Hybrid model.

1) Current Gain ( $A_I$ ):

The current gain for CE configuration is

$$A_I = \frac{-h_{fe}}{1 + h_{oe} R_L}, \quad \text{if } h_{oe} R_L < 0.1$$

$$A_I = -h_{fe}$$

2) Input Impedance ( $Z_i$ ):

By exact analysis  $Z_i = R_i = \frac{V_i}{I_i}$

$$V_1 = h_{ie} I_1 + h_{re} V_2$$

$$Z_i = \frac{h_{ie} I_1 + h_{re} V_2}{I_1} = h_{ie} + h_{re} \frac{V_2}{I_1}$$

$$V_2 = -I_2 Z_L = -I_2 R_L = A_I I_1 R_L \quad \left[ \because A_I = \frac{-I_2}{I_1} \right]$$

$$\Rightarrow Z_i = h_{ie} + \frac{h_{re} A_I I_1 R_L}{I_1} \quad \left[ \because V_2 = A_I I_1 R_L \right]$$

$$R_i = \left[ h_{ie} + h_{re} A_I R_L \right]$$

$$R_i = h_{ie} \left[ 1 + \frac{h_{re} A_I R_L}{h_{ie}} \right]$$

$$R_i = h_{ie} \left[ 1 + \frac{h_{re} A_I R_L}{h_{ie}} \times \frac{h_{fe} h_{oe}}{h_{fe} h_{oe}} \right]$$

using the typical values for the h-parameters

$$\frac{h_{re} h_{fe}}{h_{ie} h_{oe}} \approx 0.5$$

$$\Rightarrow R_i = h_{ie} \left[ 1 + \frac{0.5 A_I R_L h_{oe}}{h_{fe}} \right]$$

we know that  $A_I = \frac{-h_{fe}}{1 + h_{oe} R_L}$  if  $h_{oe} R_L < 0.1$

then  $A_I = -h_{fe}$

$$\Rightarrow R_i = h_{ie} \left[ 1 - \frac{0.5 h_{fe} R_L h_{oe}}{h_{fe}} \right]$$

$$\Rightarrow R_i = h_{ie} \left[ 1 - 0.5 h_{oe} R_L \right]$$

if  $h_{oe} R_L < 0.1$

then  $R_i = h_{ie}$   $\left[ R_i = Z_i \right]$



voltage gain:  $A_v = A_i \frac{R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie}}$

Output Impedance:

It is the ratio of  $V_c$  to  $I_c$  with  $V_s = 0$  and  $R_L$  excluded. The simplified circuit has infinite output impedance because with  $V_s = 0$  and external voltage source applied at output, it is found that  $I_b = 0$  and hence  $I_c = 0$

$$R_o = \frac{V_c}{I_c} = \infty \quad [\because I_c = 0]$$

Approximate analysis of CE Amplifier

current gain  $A_i = -h_{fe}$

Input resistance  $R_i = h_{ie}$

Voltage gain  $A_v = \frac{-h_{fe} R_L}{h_{ie}}$

output resistance  $R_o = \infty$

Analysis of CC Amplifier using the approximate Model:

Figure shows the equivalent circuit of CC Amplifier using the approximate model with the collector grounded, input signal applied between base and ground and load connected between emitter and ground.

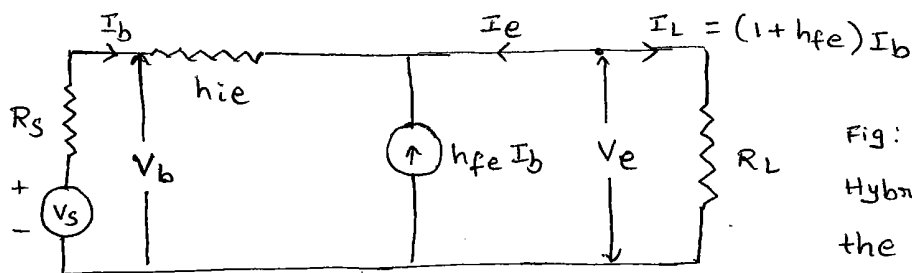


Fig: Simplified Hybrid model for the CC circuit

1) current gain :-

$$A_I = \frac{I_L}{I_b} = \frac{(1+h_{fe}) I_b}{I_b} = (1+h_{fe})$$

2) Input resistance

$$V_b = I_b h_{ie} + (1+h_{fe}) I_b R_L$$

$$R_i = \frac{V_b}{I_b} = h_{ie} + (1+h_{fe}) R_L$$

3) voltage gain

$$A_v = \frac{V_e}{V_b} = \frac{(1+h_{fe}) I_b R_L}{[h_{ie} I_b + (1+h_{fe}) I_b R_L]}$$

$$A_v = \frac{(1+h_{fe}) R_L}{h_{ie} + (1+h_{fe}) R_L} = \frac{h_{ie} + (1+h_{fe}) R_L - h_{ie}}{h_{ie} + (1+h_{fe}) R_L}$$

$$A_v = 1 - \frac{h_{ie}}{h_{ie} + (1+h_{fe}) R_L}$$

$$A_v = 1 - \frac{h_{ie}}{R_i} \quad \left[ \because R_i = h_{ie} + (1+h_{fe}) R_L \right]$$

4) Output Impedance :-

$$\text{output admittance } (Y_o) = \frac{\text{short circuit current in o/p terminals}}{\text{open circuit voltage b/n o/p terminals}}$$

short circuit current  
in output terminals

$$= (1+h_{fe}) I_b = (1+h_{fe}) \frac{V_s}{R_s + h_{ie}}$$

open circuit voltage  
b/n output terminals

$$= V_s$$

$$\therefore Y_o = \frac{1+h_{fe}}{R_s + h_{ie}} \Rightarrow R_o = \frac{h_{ie} + R_s}{1+h_{fe}}$$

output impedance including  $R_L$  ie  $R_o' = R_o \parallel R_L$

## Analysis of CB Amplifier using the approximate model

Figure shows the equivalent circuit of CB amplifier using the approximate model, with the base grounded, input signal is applied between emitter and base and load connected between collector and base

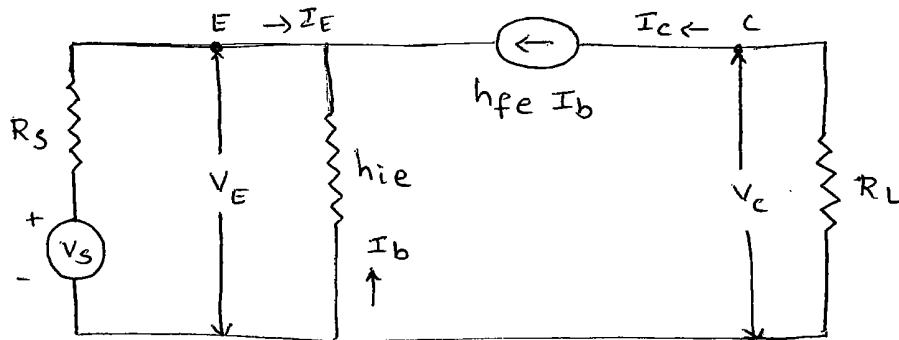


Fig: Simplified Hybrid model for the CB circuit

### 1) current gain :

$$\text{From the figure above } A_I = \frac{-I_c}{I_e} = \frac{-h_{fe} I_b}{I_e}$$

$$I_e = -(I_b + I_c)$$

$$I_e = -(I_b + h_{fe} I_b) = -(1 + h_{fe}) I_b$$

$$\therefore A_I = \frac{-h_{fe} I_b}{-(1 + h_{fe}) I_b} = \frac{h_{fe}}{1 + h_{fe}} = -h_{fb}$$

### 2) Input Resistance :

$$\text{Input Resistance } R_i = \frac{V_e}{I_e}$$

$$\text{From figure } V_e = -I_b h_{ie}, \quad I_e = -(1 + h_{fe}) I_b$$

$$R_i = \frac{h_{ie}}{1 + h_{fe}} = h_{ib}$$

### 3) voltage gain :

$$A_v = \frac{V_c}{V_e}$$

$$V_c = -I_c R_L = -h_{fe} I_b R_L$$

$$V_e = -I_b h_{ie}$$

$$A_v = \frac{h_{fe} R_L}{h_{ie}}$$

### output Impedance

$$R_o = \frac{V_c}{I_c} \text{ with } V_s = 0, R_L = \infty$$

With  $V_s = 0$ ,  $I_e = 0$  and  $I_b = 0$  hence  $I_c = 0$

$$\therefore R_o = \frac{V_c}{0} = \infty$$

### Approximate Analysis of CB Amplifier

- 1) current gain  $A_I = \frac{h_{fe}}{1 + h_{fe}} = -h_{fb}$
- 2) Input Resistance  $R_i = \frac{h_{ie}}{1 + h_{fe}} = h_{ib}$
- 3) voltage gain  $A_v = \frac{h_{fe} R_L}{h_{ie}}$
- 4) output Resistance  $R_o = \infty$

### Approximate Analysis of CC Amplifier

- 1) current gain  $A_I = (1 + h_{fe})$
- 2) Input resistance  $R_i = h_{ie} + (1 + h_{fe}) R_L$
- 3) voltage gain  $A_v = 1 - \frac{h_{ie}}{R_i}$
- 4) output Resistance  $R_o = \frac{h_{ie} + R_s}{1 + h_{fe}}$

Problem: A CE Amplifier is driven by a voltage source of internal resistance  $R_s = 800\Omega$  and the load impedance is a resistance  $R_L = 1000\Omega$ . The h parameters are  $h_{ie} = 1k\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25\mu A/V$ , compute the current gain  $A_I$ , input resistance  $R_i$ , voltage gain  $A_v$ , and output resistance  $R_o$  using exact analysis and approximate analysis.

Solution: Given data

$R_s = 800\Omega$ ,  $R_L = 1000\Omega$ ,  $h_{ie} = 1k\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$ , and  $h_{oe} = 25\mu A/V$

Exact Analysis:-

$$\text{Current Gain } A_I = \frac{-h_{fe}}{1 + h_{oe} R_L} = -48.78$$

$$\text{Input Resistance } R_i = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + \frac{1}{R_L}} = 990.24\Omega$$

$$\text{Voltage gain } A_v = A_I \frac{R_L}{R_i} = -49.26$$

output Resistance

$$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s} = 194 \times 10^{-5} \text{ mho}$$

$$R_o = \frac{1}{Y_o} = 51.42 k\Omega$$

Approximate Analysis:

$$A_I = -h_{fe} = -50$$

$$R_i = h_{ie} = 1k\Omega$$

$$A_v = \frac{-h_{fe} R_L}{h_{ie}} = \frac{-50 \times 1000}{1000} = -50$$

$$R_o = \infty$$

Problem: A voltage source of Internal resistance  $R_s = 900\Omega$  drives a cc amplifier using load resistance  $R_L = 2000\Omega$ . The ce h-parameters are  $h_{ie} = 1200\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 60$  and  $h_{oe} = 25\mu A/V$ . Compute the current gain  $A_I$ , input Resistance  $R_i$ , voltage gain  $A_v$ , and output resistance  $R_o$  using exact analysis and approximate analysis.

Sol conversion formulae:

$$h_{ic} = h_{ie} = 1200\Omega$$

$$h_{fc} = -(1 + h_{fe}) = -(1 + 60) = -61$$

$$h_{rc} = 1$$

$$h_{oc} = h_{oe} = 25\mu A/V$$

Exact Analysis:

$$A_I = \frac{-h_{fc}}{1 + h_{oc} R_L} = 58.095$$

$$R_i = h_{ic} - \frac{h_{fc} h_{rc}}{Y_L + h_{oc}} = 117.39 K\Omega$$

$$A_v = \frac{A_I R_L}{R_i} = 0.9897$$

output Admittance

$$Y_o = h_{oc} - \frac{h_{fc} h_{nc}}{h_{ic} + R_s}$$

$$\Rightarrow R_o = \frac{1}{Y_o} = 34.396 \Omega$$

### Approximate Analysis

$$A_I = 1 + h_{fe} = 1 + 60 = 61$$

$$R_i = h_{ie} + (1 + h_{fe}) R_L = 123.2 \text{ k}\Omega$$

$$A_v = 1 - \frac{h_{ie}}{R_i} = 0.99$$

$$R_o = \frac{h_{ie} + R_s}{1 + h_{fe}} = 34.43 \Omega$$

### Problem:

For a CB transistor Amplifier driven by a voltage source of internal resistance  $R_s = 1200 \Omega$ , the load impedance is a resistor  $R_L = 1000 \Omega$ . The h-parameters are  $h_{ib} = 22 \Omega$ ,  $h_{nb} = 3 \times 10^{-4}$ ,  $h_{fb} = -0.98$ ,  $h_{ob} = 0.5 \mu\text{A/V}$ . Compute the current gain  $A_I$ , Input impedance  $R_i$ , voltage gain  $A_v$ , overall voltage gain  $A_{vs}$ , overall current gain  $A_{is}$ , output impedance  $R_o$  and power gain  $A_p$  using exact and approximate analysis.

### Solution:

$$\text{Current gain } A_I = \frac{-h_{fb}}{1 + h_{ob} R_L} = 0.98$$

$$\text{Input Impedance } R_i = h_{ib} - \frac{h_{fb} h_{nb}}{Y_L + h_{ob}} = 22.3 \Omega$$

$$\text{voltage gain } A_V = \frac{A_I R_L}{R_i} = \frac{0.98 \times 1000}{22.3} = 43.94$$

$$\text{overall voltage gain } A_{VS} = \frac{A_V R_i}{R_i + R_S} = 0.802$$

$$\text{overall current gain } A_{IS} = \frac{A_I R_S}{R_i + R_S} = 0.962$$

$$\text{output Admittance } Y_o = h_{ob} - \frac{h_{fb} h_{nb}}{h_{ib} + R_S} = 0.74 \times 10^{-6} \text{ mho}$$

$$R_o = \frac{1}{Y_o} = 1.35 \text{ M}\Omega$$

$$\text{Power gain } A_P = A_V A_I = 43.06$$

### Approximate Analysis:

$$1) A_I = -h_{fb} = 0.98$$

$$2) R_i = h_{ib} = 22 \Omega$$

$$3) A_V = \frac{h_{fe} R_L}{h_{ie}}$$

$$\Rightarrow A_V = \frac{49 \times 1000}{1100}$$

$$A_V = 44.54$$

$$4) R_o = \infty$$

$A_{VS}$ ,  $A_{IS}$ ,  $A_P$  are same as that of Exact analysis.

$$\left\{ \begin{array}{l} \therefore \text{conversion formulae} \\ h_{fb} = \frac{-h_{fe}}{1 + h_{fe}} \end{array} \right.$$

$$\Rightarrow h_{fe} = \frac{-h_{fb}}{1 + h_{fb}} = 49$$

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}}$$

$$\Rightarrow h_{ie} = h_{ib} (1 + h_{fe})$$

$$h_{ie} = 22 (1 + 49) = 1100 \Omega$$