

UNIT - IIntroduction

- * Ideal Amplifier gives stable op of the given I/p signal.
- * But gain and stability of practical amplifier is not good, because of ambient temp, device parameter and non-linearity of the devices.

They are avoided by Feedback Amplifier.

Feedback

A portion of the o/p signal is feedback to the I/p and combined with the I/p signal to produce the desired o/p is called feedback.

Types:-

(1) Negative F.B (Degenerative):

The portion of o/p signal is subtracted from the I/p signal to produce desired o/p.

(2) Positive F.B (Regenerative):

The portion of the o/p signal is added to the I/p signal to produce desired o/p.


Adv. of -ve F.B

- (1) Higher I/p & lower o/p Impedance.
- (2) Improved gain sensitivity.
- (3) Reduced noise
- (4) Increased BW
- (5) Reduced Distortion.

Dis:-

- (1) Reduced ckt overall gain
- (2) Reduced stability at high freq.

Block Diagram of F.B ckt :-

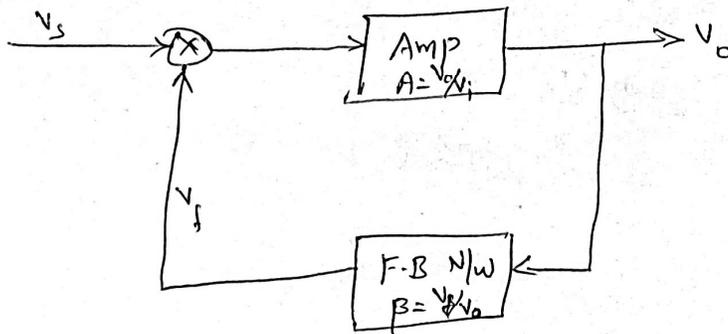

where, V_s - I/p signal

V_o - o/p signal ($V_o = AV_i$)

V_f - F.B signal
($V_f = \beta V_o$)

* Gain of the amplifier without F.B

$$A = \frac{V_o}{V_i}$$

* I/p signal applied to the amplifier is,

$$V_i = V_s \pm V_f$$

(or)

$$V_i = V_s \pm \beta V_o$$

(or)

$$V_s = V_i \pm A\beta V_o$$

$$[\because V_o = AV_i]$$

$$V_s = V_i (1 \pm A\beta)$$

where, $A\beta$ - loop gain of the amplifier.

* The Gain of the amplifier with F.B is,

$$A_f = \frac{V_o}{V_s} = \frac{AV_i}{V_i(1 \pm A\beta)} = \frac{A}{1 \pm A\beta}$$

Note

* -ve sign for +ve F.B, i.e; $A_f = \frac{A}{1 - A\beta}$

* +ve sign for -ve F.B, i.e; $A_f = \frac{A}{1 + A\beta}$

* $1 \pm A\beta$ - desensitivity factor.

* Desensitivity Factor: The Reciprocal of sensitivity is called desensitivity.

* Sensitivity :- It is the ratio of fractional change in amplifier with F.B to the fractional changes in amplifier without F.B ($\because s = \frac{1}{1 \pm A\beta}$)

Positive F.B

* Wt gain of a F.B is greater than the open loop gain.

* If AB approaches unity then the closed loop gain becomes infinity.

* Ckt should give an op without any I/p.

* Dis: Increased distortion and instability and noise.

Negative F.B

* Op signal out of phase with I/p, i.e; I/p signal is decreased, It is called -ve F.B.

* If $(1+AB) > 1$ then the closed loop gain reduces from the open loop gain A . So they called degenerative

F.B.

* If $(1+AB) \gg 1$,

$$A_{vf} = \frac{A}{1+AB} \approx \frac{A}{AB} \approx \frac{1}{B}$$

* F.B gain depends on B , i.e; A_{vf} inversely proportional to F.B factor B .

Properties of Negative Feedback:-

Performance Measurement of Negative Feedback Amplifiers

Adv

- (1) Improved stability
- (2) Reduction in gain
- (3) Reduction in distortion
- (4) Reduction in noise
- (5) Increase the B/P Imped.
- (6) Decrease the O/P Imped.
- (6) Increase in BW.

Proof

(1) Improved stability:-

The gain of the amplifier negative F.B is given by,

$$A_f = \frac{A}{1 + A\beta}$$

If $1 + A\beta \approx A\beta$ then $A_f = \frac{A}{A\beta} = \frac{1}{\beta}$

$\therefore A_f$ depends on β

i.e; A_f (F.B amplifier gain) does not affected by changes in temp, transistor parameters and frequency.
So A_f (gain) of the amplifier is extremely stable.

(2) Reduction in forward Gain:-

The Forward gain of the -ve F.B can be calculated as follows.

$$\text{Let, } V_i = V_s - V_f$$

$$V_f = \beta V_o \text{ and } V_o = AV_i$$

$$\therefore V_o = AV_i = A(V_s - V_f)$$

$$= A(V_s - \beta V_o) = AV_s - A\beta V_o$$

$$V_o(1 + A\beta) = AV_s$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

[\because closed loop gain is less than open loop gain A]

i.e., A_f is depends on sensitivity factor of $(1 + A\beta)$

(3) Reduction in Distortion

D = Distortion in amplifier without F.B

D' = Distortion in amplifier with F.B

Assume, $D' = \alpha D$ ————— (1)

* Therefore the fraction of o/p distortion which is fed back to I/P is,

$$\beta D' = \beta \alpha D$$

* After amplification the distortion becomes $\beta \alpha DA$, it is antiphase with original distortion D .

* hence the new distortion $D' = D - \beta \alpha DA$ ————— (2)

1) Compare now the Equ. (1) & (2),

$$\alpha D = D - \beta \alpha D A$$

(iii)

$$\alpha D + \beta \alpha D A = D$$

(iv)

$$\alpha = \frac{D}{D(1+\beta A)} = \frac{1}{1+\beta A}$$

Thus, $D' = \alpha D = \frac{D}{1+\beta A}$

However the improvement in the distortion is possible only if the distortion produced by the amplifier itself, not when it is already present in the i/p signal.

(1) Reduction in Noise :-

* considered F.B. ckt with two amplifier (A_1 & A_2)

* N is noise introduced after stage -1. Therefore o/p

volt. can be expressed as,

$$V_o = A_1 A_2 V_s - A_2 N - A_1 A_2 \beta V_o$$


$A_2 = \frac{V_o}{N}$ $\beta = \frac{V_f}{V_o}$

$$V_o [1 + A_1 A_2 \beta] = A_1 A_2 V_s - A_2 N$$

$$= A_1 A_2 \left[V_s - \frac{N}{A_1} \right]$$

$$V_o = \frac{A_1 A_2}{1 + A_1 A_2 \beta} \left[V_s - \frac{N}{A_1} \right] = \frac{A_1 A_2 V_s}{1 + A_1 A_2 \beta} - \frac{N A_2}{1 + A_1 A_2 \beta}$$

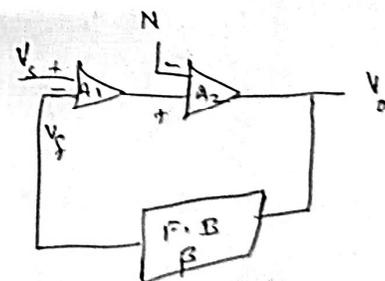\therefore The overall noise of the two stage amplifier is reduced by the factor of $(1 + A_1 A_2 \beta)$



(5) Increased I/p resistance :-

$$R_i = \frac{V_i}{I_i} \quad \left[\text{I/p impe. of Amplifier without F.B} \right]$$

$$R_{if} = \frac{V_s}{I_i} \quad \left[\text{I/p impe of Amplifier with F.B} \right]$$


From figs,

$$V_s = V_i + V_f = V_i + \beta A V_i$$

but, $V_i = I_i R_i$

$$V_s = I_i R_i [1 + \beta A]$$
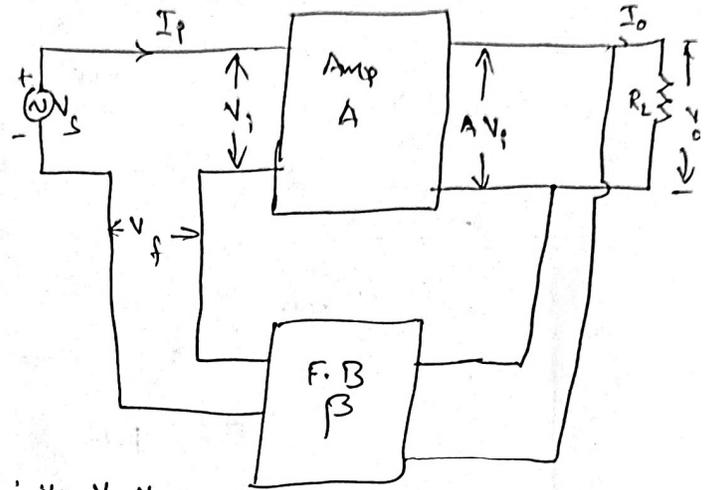
$$R_{if} = \frac{V_s}{I_i} = R_i (1 + \beta A)$$



$$\begin{aligned} \therefore V_f &= V_s - V_i \\ V_s &= V_i + V_f \end{aligned}$$

$R_{if} = R_i$ multiplied by the desensitization factor $(1 + \beta A)$, hence it is increased by $(1 + \beta A)$.

(6) O/p Impedance

$R_o =$ o/p Impe. of the amplifier without F.B

$R_{of} =$ " " " with F.B

from figure,

$$V_o = A V_i + I_o R_o$$

$$I_o R_o = V_o - A V_i$$


we know, $V_s = V_i + V_f$

Assume $V_s = 0 \therefore V_i = -V_f$

$$I_o R_o = V_o + A V_f = V_o + A \beta V_o = V_o (1 + A \beta)$$

$$\frac{V_o}{I_o} = \frac{R_o}{1 + A \beta}$$

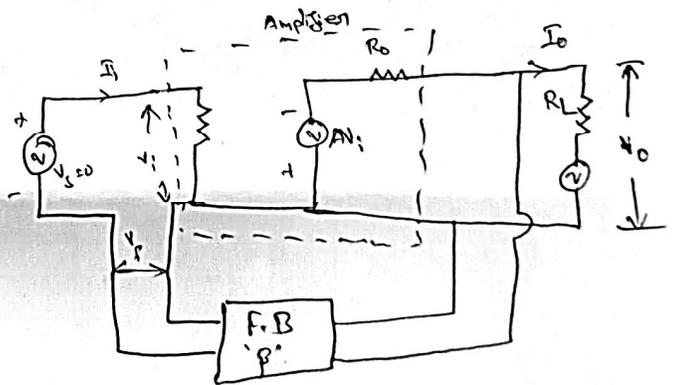
o/p Impe. is decreased by the factor of $(1 + \beta A)$



3
(b) Increased BW:-

* BW is difference BW two cut off freq.

i.e; $BW = f_2 - f_1$

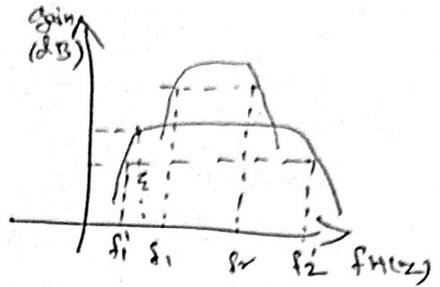

* BW is increased in F.B ckt & gain of the amplifier is decreased.

- Thus the gain BW product is remains the same (~~proof~~)

Proof

(a) Lower cut-off freq. of ^{without} F.B amplifier:

$$\text{gain, } A_L = \frac{A_m}{1 - j(f_1/f)}$$

A_m - Voltage gain in mid freq range
 f_1 = Lower cut-off freq. of amplifier without F.B.

The gain of the amplifier with feedback (at lower cut-off freq.) can be written as,

$$A_{vf} = \frac{A_L}{1 + A_L \beta} = \frac{\frac{A_m}{1 - j(f_1/f)}}{1 + \beta \frac{A_m}{1 - j(f_1/f)}} = \frac{A_m}{1 - j(f_1/f) + \beta A_m}$$

$$= \frac{A_m}{1 + \beta A_m - j(f_1/f)} = \frac{A_m}{1 + \beta A_m} \left[\frac{1}{1 - j \left(\frac{f_1}{f(1 + \beta A_m)} \right)} \right]$$

$$A_{vf} = \frac{A_{mf}}{1 - j \left(\frac{f_1'}{f} \right)} \quad \left[\because f_1' = \frac{f_1}{1 + \beta A_m} \quad \& \quad A_{mf} = \frac{A_m}{1 + \beta A_m} \right]$$

* Equ. shows $f_1' < f_1$

i.e; -ve F.B decreases Lower cut-off freq. by the factor of $(1 + \beta A_m)$

(b) Upper cut-off freq of a F.B amplifier

$$\text{gain, } A_{vf} = \frac{A_m}{1 + j(f/f_2)}$$

$$A_{vf} = \frac{A_{vf}}{1 + A_{vf}\beta} = \frac{\frac{A_m}{1 + j(f/f_2)}}{1 + \left(\frac{A_m}{1 + j(f/f_2)}\right)\beta} = \frac{A_m}{1 + j(f/f_2) + A_m\beta}$$

$$A_{vf} = \frac{A_m}{1 + A_m\beta} \left(\frac{1}{1 + j\left(\frac{f}{f_2(1 + A_m\beta)}\right)} \right) = \frac{A_{mf}}{1 + j(f/f_2')}$$

where, $f_2' = f_2(1 + A_m\beta) =$ upper cut-off freq with F.B.

$$A_{mf} = \frac{A_m}{1 + A_m\beta} = \text{midband gain of the amplifier with F.B.}$$

* Equ. show that $f_2' > f_2$

i.e., upper cut-off freq. is increased in -ve F.B.

\therefore BW is high in -ve F.B.

Basic - Feedback Topologies

In F.B amplifier, sample o/p volt. (or) c.t by means of sampling (or) feedback N/w and applied at the I/p of the Amplifier. Based on the quantity to be amplified the amplifiers are classified into 4 types.


- (1) Volt. Amplifier
- (2) c.t Amplifier
- (3) Trans conductance Amplifier
- (4) Trans resistance Amplifier.

(1) Voltage Amplifier (or) Voltage Controlled Volt Source (VVS)

In this amplifier,


$$V_i = \text{I/P Volt.}$$

$$V_o = \text{O/P Volt.}$$

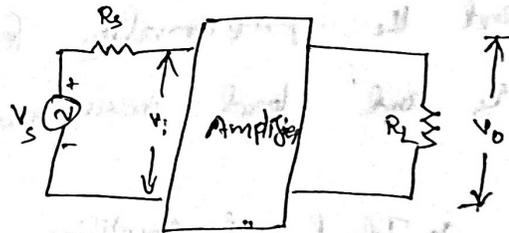

* ideal volt. sources (or) volt. amplifier
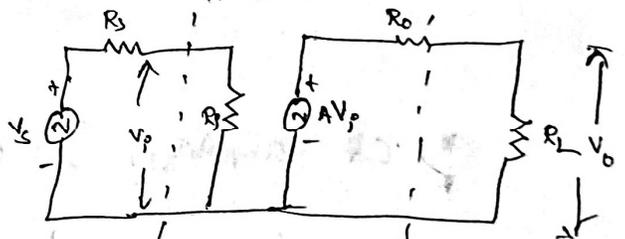
$$R_i \gg R_s \text{ thus } V_i \approx V_s$$



where

* R_i, R_s are I/P S sources resistance

and also if $R_L \gg R_o$, thus

$$V_o = A_v V_i \quad \text{(or)} \quad V_o \approx A_v V_s$$

note: * o/p V_o is directly proportional to I/p Volt. and proportionality factor is independent of the magnitudes of the source and load resistances. It is called 'Voltage Amplifier'


* Ideal volt. amplifier $\rightarrow R_i - \text{Infinite}$
 $R_o - \text{Zero}$

(2) Current Amplifier (or) Voltage Controlled Current Sources (VCCS)

* In this ckt, o/p signal & F.B signals are current,

* $R_i \ll R_s$ & $I_i \approx I_s$ and also $R_o \gg R_L$ then $I_L \approx A_i I_i$

$$\therefore A_i = \frac{I_o}{I_i}$$

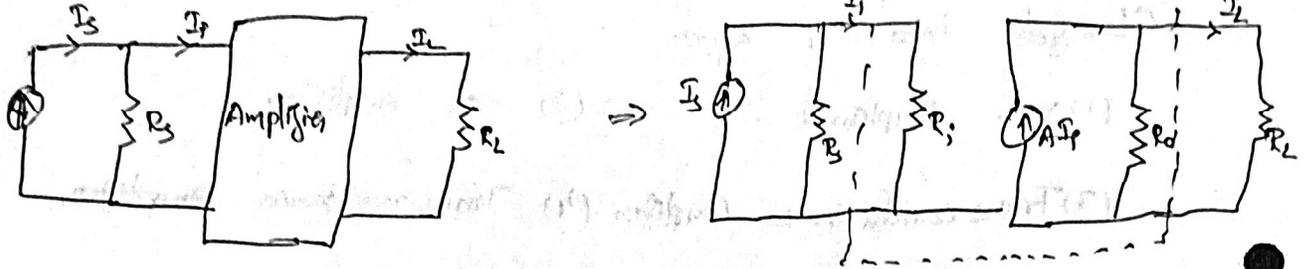

* o/p I_o is directly proportional to the i/p signal current I_i , and the proportionality factor is independent of source resistance R_s and load resistance R_L .

* Ideal C_i Amplifier $\rightarrow R_i = 0$

$R_o = \infty$ (Infinite)

* C_i amplifier is opposite to that of voltage amplifier

* It drives a low resistance load and volt. amplifier driven by a high resistance source.


7
(3) Transconductance Amplifier (or) CC Controlled Volt. Source

* It is the ratio of CC in one loop to V.O.H. in some other loop.

* In this amplifier, Volt is given I/P (V) and CC is taken O/P

* $I_o \propto V_i$

$$G_m = \frac{I_o}{V_i}$$

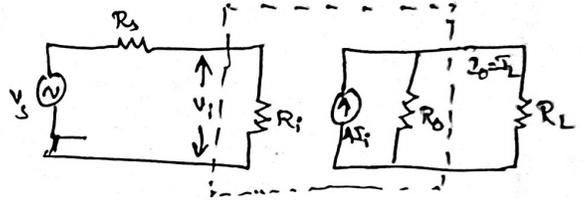

* In this case, $R_i \gg R_s$ then $V_i \approx V_s$ and $\frac{I_o}{R_o} \ll R_L$

then, $I_o = G_m V_i \approx G_m V_s$

Since $R_o \gg R_L$, it drives a low resistive load.

(4) Transresistance Amplifier (or) Current Controlled Current Source (CCS)

* It is the ratio of Volt. in one loop to Current in some other second loop.


* A source act as I/P signal & Volt. is taken as O/P

* I/P is represent as Norton eqn. CKF

O/P is " as Thevenin's "

* $R_s \gg R_i$, then $I_i \approx I_s$

$$I_o R_o \ll R_L$$

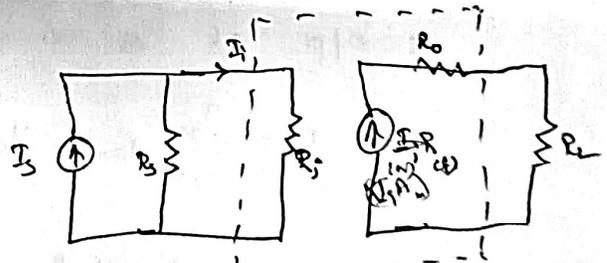

then $V_o = R_m I_i \approx R_m I_s$

$R_m \approx A_m R_o$ $\leftarrow A_m I_i \approx A_m I_s$

$$R_m \approx A_m = \frac{V_o}{I_i}, \text{ with } R_L = \infty$$

$\therefore R_m$ is the open-circuit mutual (or) transfer resistance.

I/p & o/p resistance with F.B

* There are 4 basic ways to connecting F.B signal.

* Both CR (or) Volt. can be F.B to the I/p either in series

(or) parallel.

* It is classified as, (1) Volt. Series F.B Connection

(2) Volt. Shunt F.B Connection

(3) Current Series F.B Connection

(4) Current Shunt F.B Connection.

(1) Volt. Series F.B:-

* o/p Volt. directly proportional to the I/p Volt., thus it is used as Volt. Amplifier.

$$A = \frac{V_o}{V_i} \quad (\text{or}) \quad V_o = AV_i$$

(2) Volt. Shunt F.B

* o/p Volt. \propto I/p CR, is ^{also} called Trans resistance Amplifier.

$$A = \frac{V_o}{I_i} \quad (\text{or}) \quad V_o = AI_i$$

(3) Current Series F.B

* o/p CR is \propto to I/p Volt. (Transconductance)


$$A = \frac{I_o}{V_i} \quad (\text{or}) \quad I_o = AV_i$$

(4) Current Shunt F.B

* o/p CR \propto I/p CR (CR Amplifier)

$$A = \frac{I_o}{I_i} \quad (\text{or}) \quad I_o = AI_i$$

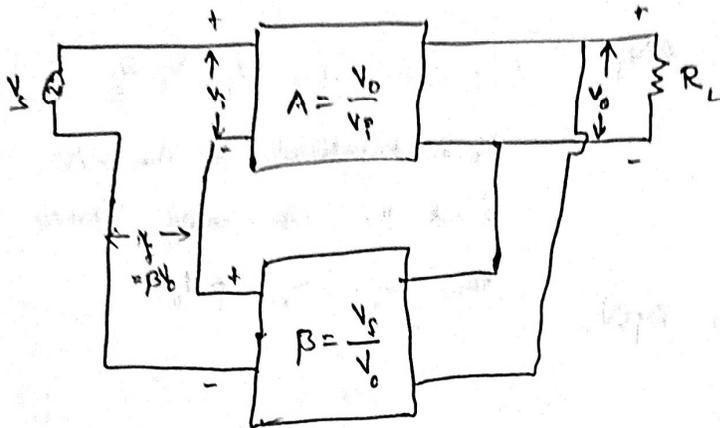Voltage Series Feedback [series-shunt F.B]



Let, $A_v = \frac{V_o}{V_i}$ = gain of the amplifier without F.B (or) $V_o = V_i A$

If F.B is connected then $V_s = V_i + V_f$ (or) $V_i = V_s - V_f$

$$V_s = V_i + \beta V_o = V_i + \beta A V_i = (1 + \beta A) V_i$$

$$A_{v_f} = \frac{V_o}{V_s} = \frac{V_i A}{V_i (1 + \beta A)} = \frac{A}{(1 + \beta A)}$$

I/p Impedance:

$$V_i = V_s - V_f = R_i I_f$$

Assuming R_o to be negligible,

$$V_s = V_i + V_f = R_i I_f + \beta V_o = R_i I_f + \beta A V_i$$

$$V_s = R_i I_f + I_f R_i \beta A = Z_i I_f + I_f \beta A R_i$$

$$V_s = Z_i I_f (1 + \beta A)$$

$$Z_{i_f} = \frac{V_s}{I_f} = Z_i (1 + \beta A)$$

output Impe.

from figure, $V_o = I_o Z_o + A V_i$

$$= I_o Z_o - A V_f$$

$$V_o = 0 \Rightarrow V_i = -V_f$$

$$V_o = I_o Z_o - A \beta V_o$$


$$V_o (1 + A \beta) = I_o Z_o$$

$$Z_{of} = \frac{V_o}{I_o} = \frac{Z_o}{1 + A \beta} = \text{o/p impe of the amplifier with } \beta$$

where, $Z_o = \text{o/p impe. of the amplifier without F.B.}$

Thus the o/p impe. is reduced by a factor of $(1 + A \beta)$

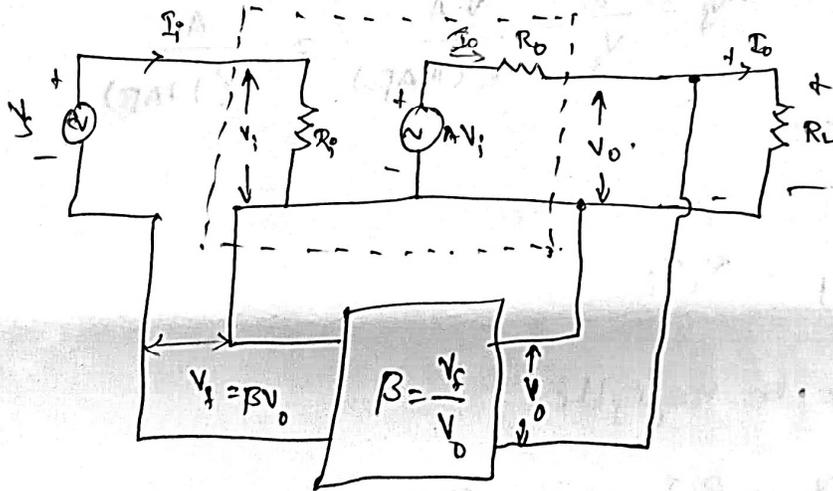from the o/p impe. of the amplifier without F.B



Voltage Shunt Feedback [Shunt - Shunt F.B]

* o/p signal is fed in parallel with the I/p end, then it is called as volt. shunt F.B.

* I/P ct is varied by o/p volt. because of shunt connection.


∴ ratio of V_o/I_p , it is called transistance.

Let, $A = \frac{V_o}{I_p}$ = gain of amplifier without F.B and $\beta = \frac{I_f}{V_o}$

* $I_s = I_p + I_f = I_p + \beta V_o = I_p + \beta A I_p = I_p (1 + \beta A)$

∴ $A_f = \frac{V_o}{I_s} = \frac{V_o}{I_p + \beta A I_p} = \frac{A I_p}{(1 + \beta A) I_p} = \frac{A}{1 + \beta A}$

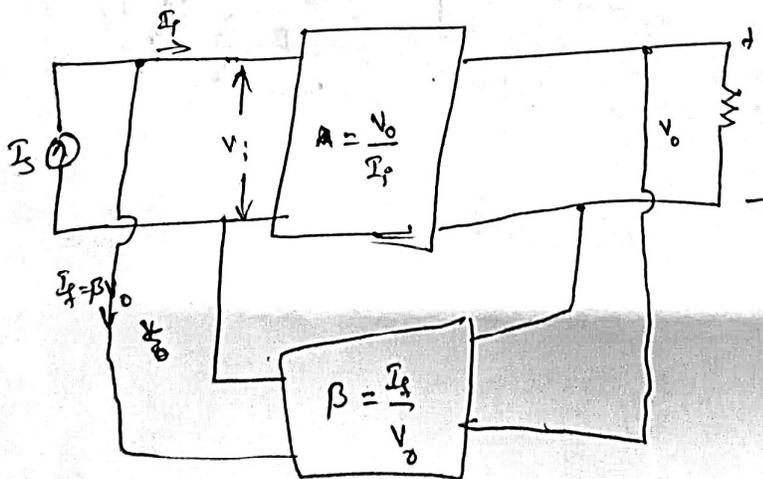Thus, $A_f = \frac{A}{1 + \beta A}$ = gain of the amplifier with F.B



I/p Impedance:-

* A volt. shunt F.B connection with basic amplifier modelled as a dependent volt. source (shown in fig.)

* The I/p impe. with F.B is given by,

$$Z_{if} = \frac{V_i}{I_i} = \frac{V_i}{I_i + I_f} = \frac{V_i}{I_i + \beta V_o} = \frac{V_i}{I_i + \beta A I_i} = \frac{V_i}{I_i (1 + \beta A)}$$

$$Z_{if} = \frac{Z_i}{1 + \beta A}$$

$$\because Z_i = \frac{V_i}{I_i}$$

* I/p Impe. reduced by $(1 + \beta A)$. This is true for both volt. shunt and a shunt F.B connections.

O/p Impe

From fig.

$$V_o = I_o R_o + A I_i = I_o R_o - A I_f$$

we know, $I_f = I_i - I_o$

I_i is transferred to o/p side,

thus $I_i = 0$


then $I_f = -I_o = -\beta V_o$

$$V_o = I_o R_o - \beta A V_o$$

$$V_o (1 + \beta A) = I_o R_o$$

$$R_{of} = \frac{V_o}{I_o} = \frac{R_o}{1 + \beta A}$$

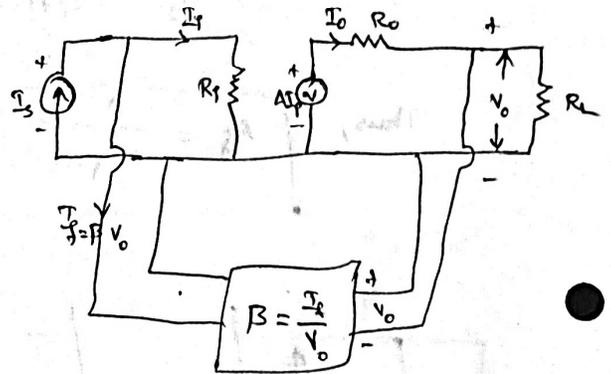* R_{of} reduced by $(1 + \beta A)$, from the amplifier without F.B $Z_o = R_o$.



Method of Identifying Feedback Topology And Basic Amplifier

with loading Effect of Feedback:-

Rules For To Identify the Feedback Topology following rules are followed

- (1) Identify the whether the feedback signal applied is a Volt. (or) ~~Circuit~~ ^{Current} (or) Identify the feedback signal is applied in series (or) shunt with the external excitation.
- (2) Identify the sampled signal is a volt. (or) Ct (or) Identify whether the sampled signal is taken at the op node (or) loop.

To find the Op Sampling Circuits

- (a) If making $V_o = 0$ results in the F.B signal $V_f = 0$ then it is known as Volt. Sampling. (i) (shunt output node)
- (b) If the outer loop $I_o = 0$ if F.B signal becomes zero then it is known as Current Sampling (ii) open the output loop

To find the mixing Circuits

- (i) If the F.B signal is subtracted from the I/P Volt. then it is known as Series mixing.
- (ii) If the F.B signal is subtracted from the I/P Ct then it is known as Shunt mixing.

To find the Z/P Equ. Ckt

(1) for Volt. Sampling set $V_o = 0$


(2) for Ct Sampling set $I_o = 0$

To find the O/P equivalent circuit

(1) for Series mixing set $I_i = 0$

(2) for Shunt mixing set $V_i = 0$

Current Series F.B [series-series F.B]

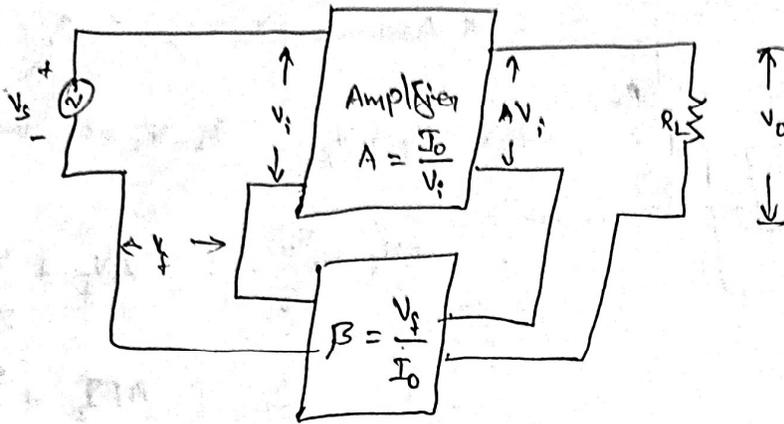

* O/P is F.B to series with I/P ckt
 \therefore I/P Volt. is \propto to I_o .

* The ratio of I_o/V_i is known as transconductance amplifier.

* $R_i \gg R_s$ and $R_o \gg R_L$ thus, $I_o = I_L$

* without F.B, $A = \frac{I_o}{V_o}$

* F.B factor $\beta = \frac{V_f}{I_o}$

* $V_s = V_i + V_f$

$$\therefore A_f = \frac{I_o}{V_s} = \frac{I_o}{V_i + V_f} = \frac{AV_i}{V_i + \beta AV_i} = \frac{A}{1 + A\beta}$$

* gain reduced by $(1 + A\beta)$, when F.B is provided

I/P Impe (from fig)


$$V_s = I_i R_i + V_f = I_i R_i + \beta I_o = I_i R_i + \beta A V_i$$

where, $I_o = A V_i = I_i R_i + A \beta I_i R_i$ [where, $V_i = I_i R_i$]

$$V_s = I_i R_i (1 + A\beta)$$

$$R_{if} = \frac{V_s}{I_i} = R_i (1 + A\beta)$$

O/p Impe.

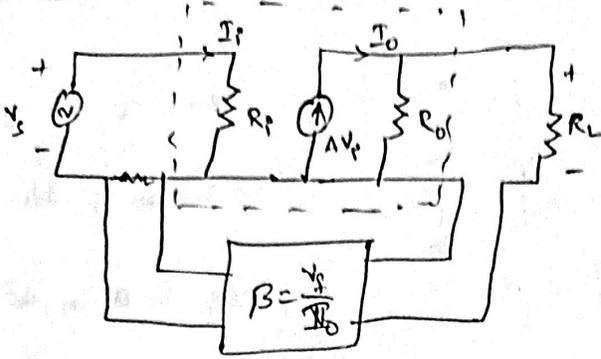

* O/p Impe depends on I/P source volt

* Assume $V_s = 0$, $\therefore I_o = ?$

$$V_s = V_i + V_f \quad \text{If } V_s = 0, \text{ then } V_i = -V_f$$

$$I_o = AV_i + \frac{V_o}{Z_o} = -AV_f + \frac{V_o}{Z_o}$$

$$I_o = -AB I_o + \frac{V_o}{Z_o}$$


$$I_o(1+AB) = \frac{V_o}{Z_o}$$

hence

$$Z_{of} = \frac{V_o}{I_o} = Z_o(1+AB)$$

\therefore O/p Impeel \uparrow by $(1+AB)$.

Current Shunt F.B [shunt-series F.B]

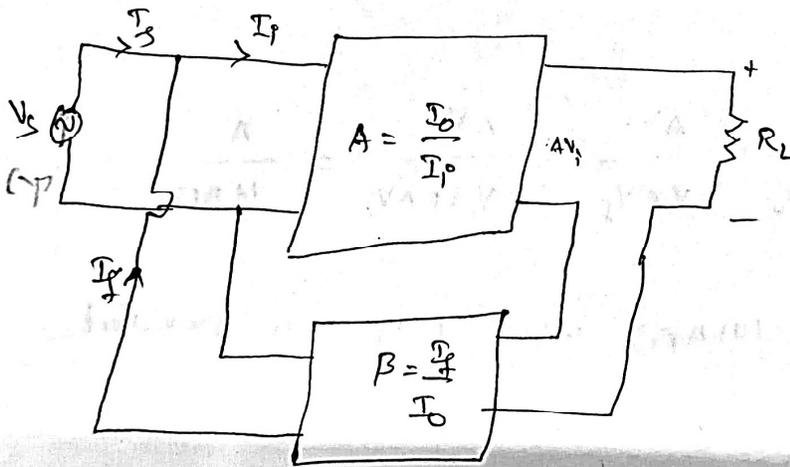

* O/p ~~curr~~ is F.B para
with I/P curr

* \therefore ratio of I_o/I_i becomes
cf gain then, this configuration
behave like a 'cf Amplifier'.


* Let the gain of the amplifier without F.B is $A = \frac{I_o}{I_i}$

F.B factor, $B = \frac{I_i}{I_o}$

$$* A_f = \frac{I_o}{I_s} = \frac{I_i A}{I_i + I_f} = \frac{I_i A}{I_i(1+AB)}$$

\uparrow
 $I_f = I_o B$
 \uparrow
 $AB = \beta A$

" I/p Impe.

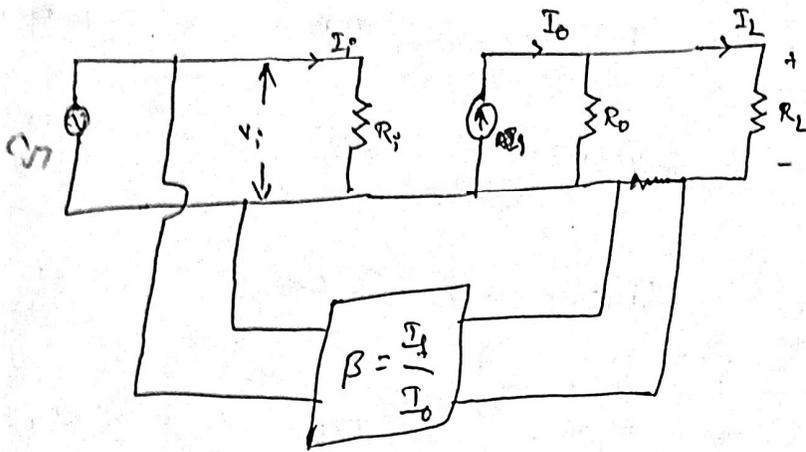

From fig,

$$I_1 = I_i + I_0 = \frac{V_1}{R_i} + \beta I_0 = \frac{V_1}{R_i} + \beta A I_1$$

$I_i = I_1 - \beta I_0$

$$I_i = \frac{V_1}{R_i} + \frac{\beta A V_1}{R_i} = \frac{V_1}{R_i} (1 + \beta A)$$

$$\therefore R_{i\beta} = \frac{V_1}{I_i} = \frac{R_i}{1 + \beta A}$$

O/p Impe

From fig, $I_1 = I_i + I_0$ (or) $I_0 = I_1 - I_i = -I_0 \left[\frac{I_0}{I_1} I_1 = 0 \right]$

$$I_0 = A I_1 + \frac{V_0}{R_0} = \frac{V_0}{R_0} - A I_0 = \frac{V_0}{R_0} - \beta I_0$$

(or)

$$I_0 (1 + \beta) = \frac{V_0}{R_0}$$

(or)




$$R_{o\beta} = \frac{V_0}{I_0} = R_0 (1 + \beta)$$

10-11-17

	Volt. Series F.B	Volt. Shunt F.B	CL Series F.B	CL Shunt F.B
Gain	decreases	decreases	decr.	decre.
stability	Increases	Increases	Incr.	Incr.
Noise	decr.	decr.	decr.	decr.
Distortion	decr.	decr.	decr.	decr.
$(A_{TH}) \frac{V}{I}$ I/p Impe.	Incr.	decr.	Incr.	dec.
O/p Impe.	decr	decr.	Incr.	Incr.

[Faint handwritten notes at the bottom of the page]

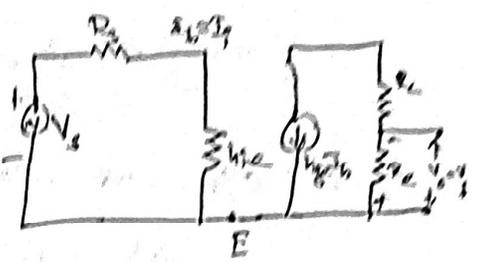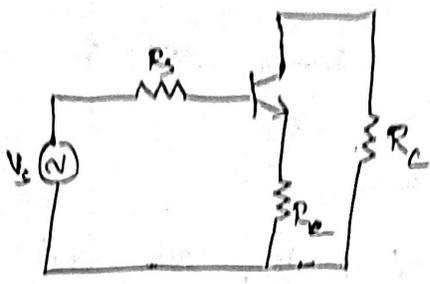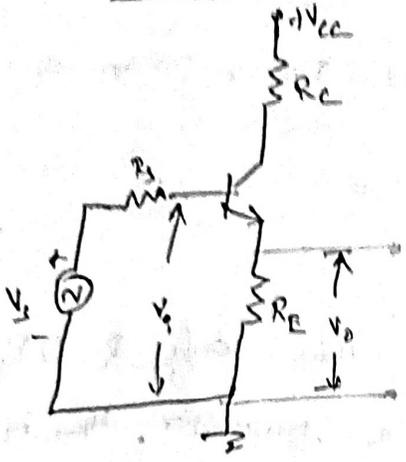13 Voltage Series F.B Amplifier - Emitter Follower



● Step-1 : Method of identify the topology.

(1) * Voltage drop across the resistor R_E is o/p volt. it act as

F.B volt. V_f

\therefore gain F.B CKT $\beta = \frac{V_f}{V_o} = 1$

(2) $\frac{V_f}{V_o} = 1$ F.B volt. $V_f = V_o$ is connected in series with I/p CKT hence it is known as Volt. series F.B amplifier. (also called Emitter follower).

\Rightarrow In this CKT, R_E act as F.B element, which is connected in series with the I/P CKT refer.

Step-2 (Find the I/P & O/P CKT)

(3) In this amplifier, $V_o =$ o/p Volt. & $V_i =$ F.B volt.

without F-B is $A = \frac{V_o}{V_i}$

with F-B is $A_f = \frac{V_o}{V_i}$

The F.B signal $V_f = \beta V_o$ (ov) $\beta = \frac{V_f}{V_o}$

(4) from eqn. CKF, (I/P CKF Analysis)

$V_o = 0$ (or) short CKF, $\therefore R_E = 0$
Assume, $V_o = 0$ (or) short CKF, $\therefore R_E = 0$

hence V_s appear b/w base & emitter, and I/P resistance of transistor h_{ie} is series with R_s .

(5) O/P CKF Analysis:-

- set $I_i = 0$ (I/P loop is open CKF), thus only R_C & R_E is connected in series with βI_b of the transistor, thus in the O/P CKF transistor is replaced by βI_b source which is connected in series with R_C & R_E .

(6) - I/P signal $V_i = V_s - V_o$

- O/P volt. $V_o \gg V_s$, hence -ve F.B, which makes the base emitter junction becomes less ^{forward bias} FB as a result of the gain is decreased.

(7) Ideal CKF, $R_i \uparrow$ & $R_o \downarrow$

Voltage gain

From eqn. CKF
 $V_s = (R_s + h_{ie}) I_i$

$$V_o = \frac{h_{fe} I_b R_e}{\beta}$$

Gain of the amplifier without F.B,

$$A_{vs} = \frac{V_o}{V_s} = \frac{h_{fe} I_b R_e}{(R_s + h_{ie}) I_i} = \frac{h_{fe} R_e}{R_s + h_{ie}}$$

~~The~~ gain

14 The gain of the amplifier with F.B is,

$$A_{VSF} = \frac{A_{VS}}{1 + \beta A_{VS}} = \frac{\frac{h_{fe} R_e}{R_s + h_{ie}}}{1 + \frac{h_{fe} R_e}{R_s + h_{ie}} \beta} = \frac{h_{fe} R_e}{R_s + h_{ie} + \beta h_{fe} R_e} \quad \left[\begin{array}{l} \text{where} \\ \beta = 1 \end{array} \right]$$

If $R_s + h_{ie} \ll h_{fe} R_e$ then $A_{VSF} \approx 1$

Input Impedance

we know the I/P impe of the Volt. Series FB is,

$$R_{if} = R_i (1 + \beta A_{VS}) \quad \text{where } R_i = h_{ie}$$

we know, $A_{VS} = \frac{h_{fe} R_e}{R_s + h_{ie}} \approx \frac{h_{fe} R_e}{h_{ie}} \quad \left[\begin{array}{l} R_s \ll h_{ie} \\ \text{(a)} \\ \neq R_i \end{array} \right]$

$$R_{if} = h_{ie} \left(1 + \frac{h_{fe} R_e}{h_{ie}} \beta \right) = h_{ie} \left(\frac{h_{ie} + h_{fe} R_e \beta}{h_{ie}} \right)$$

$$R_{if} = (h_{ie} + h_{fe} R_e) \quad \left[\beta = 1 \text{ due to unity gain} \right]$$

Output Impe.

* o/p impe. without F.B is, $R_o = \frac{V_o}{I_{sc}} \quad \left[\begin{array}{l} V_o - \text{open ckt volt.} \\ I_{sc} - \text{short ckt ct} \end{array} \right]$

* The o/p impe. of amplifier is given as,

$$R_o = \frac{V}{I} = \lim_{R_e \rightarrow \infty} R_e \text{ (Ideal)}$$

We know the o/p impe. of the voltage series F.B connection is,

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{L_{Re \rightarrow \infty} R_e}{1 + \frac{h_{fe} R_e}{h_{ie} + R_s} \cdot \beta} = L_{Re \rightarrow \infty} \frac{(h_{ie} + R_s) \cdot R_e}{h_{ie} + R_s + h_{fe} R_e \beta}$$

$$= L_{Re \rightarrow \infty} \frac{(h_{ie} + R_s) R_e}{\left(\frac{h_{ie} + R_s}{R_e} + h_{fe} \beta \right) R_e}$$

$$R_{of} = \frac{h_{ie} + R_s}{h_{fe} \beta} \quad \text{if } \beta = 1 \text{ then, then, } R_{of} = \frac{h_{ie} + R_s}{h_{fe}}$$

Current Series F-B Amplifier

* In DC bias: R_e provide stabilization ~~to~~ there is no ac F.B.

* In AC bias: without C_E capacitor, R_E Volt. drop across R_E act as Feedback Volt., Thus R_e is act as F.B element.


* R_E connected b/w I/P & O/P, $(I_b + I_c)$ ct flow through in R_E .

$$- \text{In } R_e \Rightarrow V_f = (I_b + I_c) R_e$$

$$R_e \approx I_c R_e = -I_c R_e$$

* o/p ct I_c given to I/P, i.e. sample ct I_c subtracted from I/P V_i .

Thus it is known as ct series F.B.

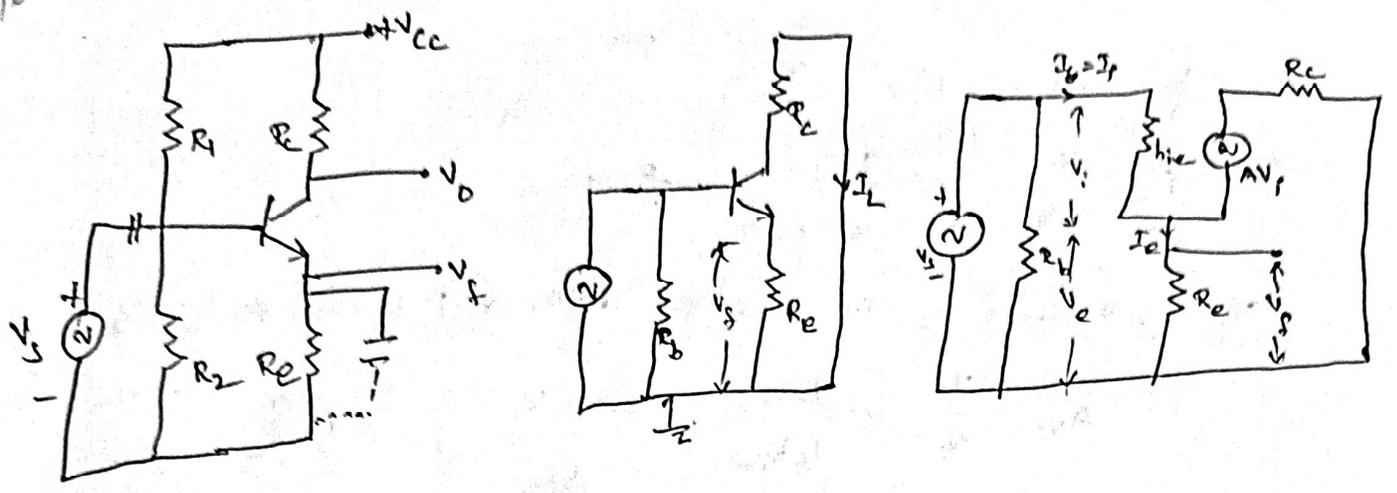

Step 1: Method of Identifying the topology.

- I_f o/p ckt open, $I_L = 0 \Rightarrow$ F.B signal also zero \Rightarrow called CE sample
- F.B signal $\frac{V_o}{A_v}$ is subtracted from the I/p signal $V_s \Rightarrow$ series minus
- \leftarrow Finally, conclusion of this condition is identifies the topology is CE series. F.B.

Step 2 (Find the I/P & O/P ckt)

- $\frac{I_i}{I_f}$ - To find I/P ckt, set $I_L = 0$ for R_E appear in I/P side
- " " O/P " , set $I_i = 0$, then R_E " " O/P side

* I/P Impedance :-

$$R_{if} = \frac{V_s}{I_i} = \frac{V_i + V_e}{I_i} = \frac{V_i}{I_i} + \frac{V_e}{I_i} = R_i + \frac{I_e R_e}{I_i} = R_i + \frac{I_e R_e}{I_e - I_c} = R_i + \frac{R_e}{1 - \frac{I_c}{I_e}}$$

we know, $I_c = I_b h_{fe}$; $I_e = (I_c + I_b) = I_b (1 + h_{fe})$

hence, $\frac{I_e}{I_c} = \frac{1 + h_{fe}}{h_{fe}}$ Thus, $R_{if} = R_i + \frac{R_e}{1 - \frac{h_{fe}}{1 + h_{fe}}} = R_i + R_e (1 + h_{fe})$

$\frac{I_i}{I_f}$ $R_i = h_{ie}$ and biasing resistors are parallel then $R_i' = R_1 || R_2$
 where, $R_b = R_1 || R_2$

Voltage gain we know, $V_o = -I_c R_e \approx -I_e R_e$

$$V_s = (I_b + I_c) R_e \approx I_c R_e$$

$$= \frac{I_c R_e}{I_c R_e} = -\frac{R_o}{R_e} = 1$$

$$\beta = \frac{V_s}{V_o} = -\frac{I_c R_e}{I_c R_e} = -1$$

The volt gain of the amplifier without F.B is given by

$$A_{vs} = \frac{V_o}{V_s} \approx -\frac{I_c R_e}{I_b h_{ie}} = \frac{-h_{fe} R_e}{h_{ie}} \quad \left[\beta = \frac{I_c}{I_b} \right]$$

we know,

$$(A_{vs})_f = \frac{A_{vs}}{1 + A_{vs}\beta} = \frac{-\frac{h_{fe} R_e}{h_{ie}}}{1 + \frac{h_{fe} R_e}{h_{ie}} \left(-\frac{R_e}{R_e}\right)}$$

$$(A_{vs})_f = -\frac{h_{fe} R_e}{h_{ie} + h_{fe} R_e}$$



$$\approx -\frac{h_{fe} R_e}{h_{ie}}$$

o/p Impe


$$R_{of} = R_o (1 + A\beta) = R_o \left(1 + \frac{h_{fe} R_e}{h_{ie}} \left(-\frac{R_e}{R_e}\right) \right)$$

$$R_{of} = R_o \left(1 + \frac{h_{fe} R_e}{h_{ie}} \right)$$

Voltage Shunt F.B Amplifier

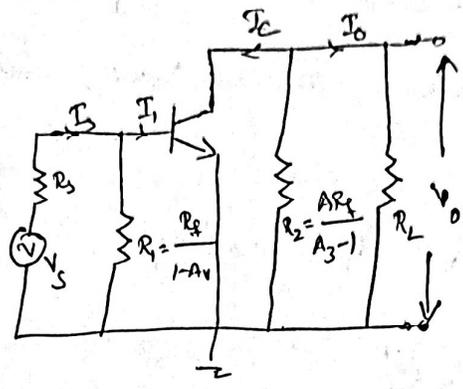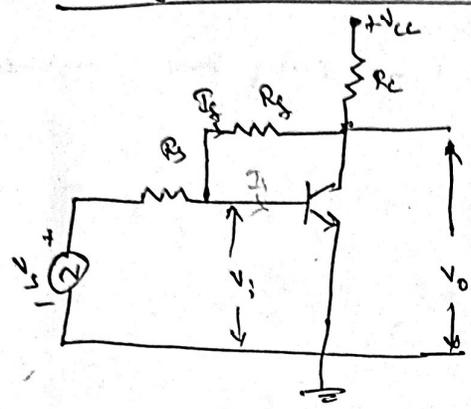

$$A = \frac{V_o}{I_i}$$

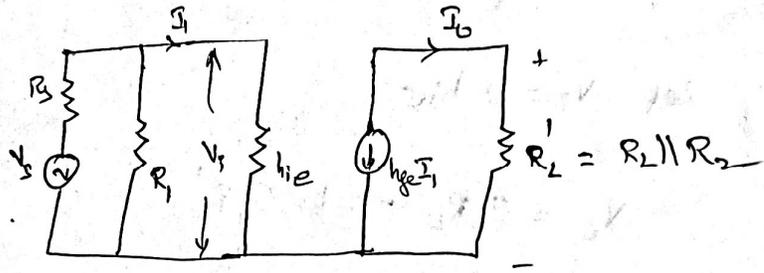

* R_f b/w collector to base, it act as F.B resistance

* V_o is $> V_i$ and 180° out of phase with each other.

Hence,
$$I_f = \frac{V_i - V_o}{R_f} \approx \frac{-V_o}{R_f}$$

where, or
$$\beta = \frac{I_f}{V_o} = \frac{-1}{R_f} = \text{Feedback factor.}$$

* Method of Identifying the topology:-

The o/p volt. $V_o = 0$ then F.B signal reduced to zero thus it is known as volt. Sampling.

- In this case, F.B signal I_f is subtracted from the i/p signal I_s thus it is known as shunt mixing.

hence this topology is known as volt. shunt F.B.

Ans

Step 2 \Rightarrow To find I/P ckt set $V_0 = 0$.

so $R_f = 0$, and it has only source resistance.

\Rightarrow To find o/p ckt: $V_i = 0$, and it has only source resistance R_s .

* I/P Impe.

$$R_{if} = Z_{if} = h_{ie} \parallel R_s \parallel R_f$$

$$* V_0 = -h_{fe} I_b R_L'$$

Let $V_i = I_b h_{ie}$

$$\rightarrow V_0 = I_b R_L' = -h_{fe} I_b R_L'$$

hence, $A_{vs} = \frac{V_0}{V_i} = -\frac{h_{fe} R_L'}{h_{ie}}$

where, $R_L' = R_2 \parallel R_L \approx R_L$


overall voltage gain,

$$A_v = \frac{V_0}{V_i} = \frac{-h_{fe} I_b R_L'}{h_{ie} I_b} = -\frac{h_{fe} R_L'}{h_{ie}}$$

$$A_{vsf} = \frac{A_{vs}}{1 + A_{vs}\beta} = \frac{-\frac{h_{fe} R_L'}{h_{ie}}}{1 + \left(-\frac{h_{fe} R_L'}{h_{ie}}\right) \left(-\frac{1}{R_f}\right)}$$

$$= \frac{-h_{fe} R_L' R_f}{h_{ie} R_f + h_{fe} R_L'}$$

o/p Impe.


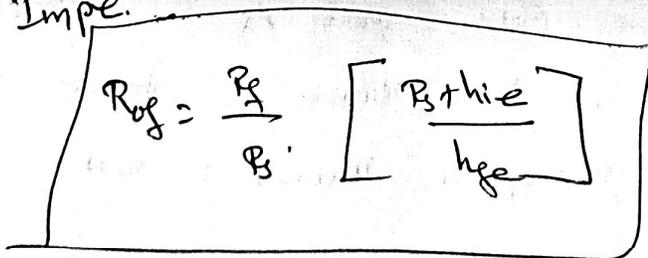


$$R_{of} = \frac{R_o}{1 + A_{vs}} = \frac{R_o}{1 + \left(\frac{h_{fe} R_L'}{h_{ie}}\right) \left(\frac{1}{R_f}\right)} = \frac{R_o \cdot h_{ie} R_f}{h_{ie} R_f + h_{fe} R_L'} = R_f$$

$$R_{of}' = R_{of} \parallel R_L =$$

17 Current Shunt F.B Amplifier

$A = \frac{V_o}{V_i}$

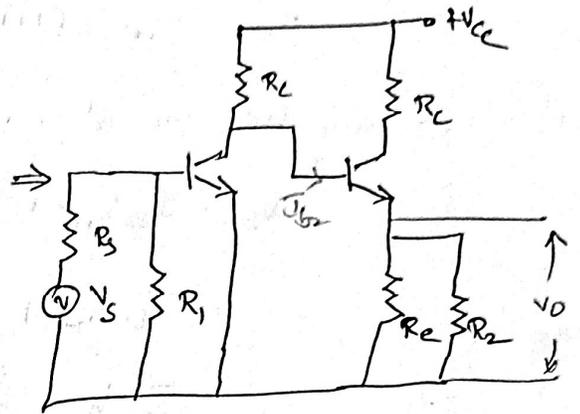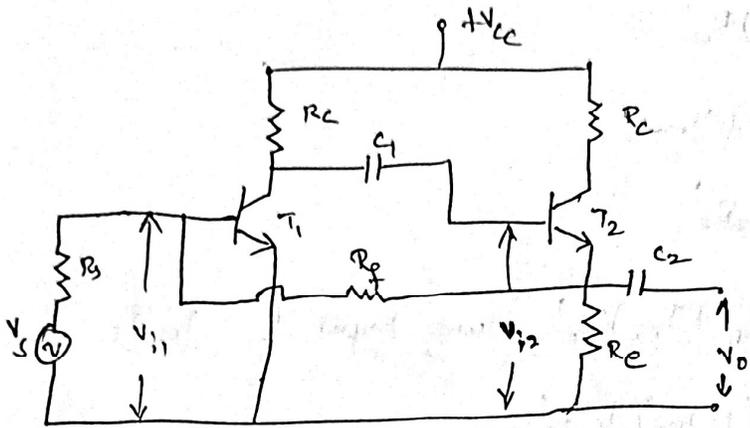

Method of Identifying the topology

- If $V_o = 0$, F.B signal does not become zero, but $I_o = 0$, F.B signal becomes zero. (Ct sampling)
- and F.B signal is connected in shunt with i_p signal ^{Ct} hence it is called 'Ct shunt F-B amplifier'.

* 1st stage connected to 2nd stage amplifier (CE & CC amplifier)

* $V_{i2} > V_{i1}$

* $V_{i2} - 180^\circ$ out of phase with V_{i1}

* $I_f = \frac{V_{i1} - V_o}{R_f} \approx \frac{-V_o}{R_f}$

$V_o = -I_o R_E$

hence, $I_f = \frac{I_o R_E}{R_f}$ (or) $\beta = \frac{I_f}{I_o} = \frac{R_E}{R_f}$

$V_i = I_f R_E$
 $V_o = I_o R_E$
 $\beta = \frac{R_E}{R_f}$

* The I/P imped. of transistor T_2 is given by

$$R_{i2} = h_{ie} + (1+h_{fe})R_e'$$

it can be proved as follows

$$V_{i2} = I_{b2}h_{ie} + I_{e2}R_e'$$

$$= I_{b2}h_{ie} + (I_{b2} + I_{c2})R_e' \quad \text{we know } I_c = h_{fe}I_b$$

$$= I_{b2}h_{ie} + (1+h_{fe})I_{b2}R_e'$$

$$= I_{b2} [h_{ie} + (1+h_{fe})R_e']$$

$$\boxed{\frac{V_{i2}}{I_{b2}} = R_{i2} = h_{ie} + (1+h_{fe})R_e'} \quad \text{[where, } R_e' = R_e \parallel R_2$$

* The Volt. gain of transistor T_1 is, $A_1 = \frac{-h_{fe}R_L'}{h_{ie}}$

$$\text{i.e., } V_o = -h_{fe}I_b R_L' ; V_i = I_b h_{ie} \quad \text{Thus } A_{v1} = \frac{-h_{fe}R_L'}{h_{ie}}$$

* Total Volt. gain

$$A_v = A_{v1} \cdot A_{v2}$$

$$\text{where, } A_{v2} = \frac{-h_{fe}R_L'}{h_{i2}} ; R_1 = \frac{R_f}{1-A} ; R_2 = \frac{R_e A}{1-A}$$

* o/p Impe



$$R_{of} = R_o(1+A\beta) = \infty$$

Total o/p Impe.

$$\begin{aligned} R_{of}' &= R_{of} \parallel R_L \\ &= \infty \parallel R_{c2} \\ &= \infty \parallel R_{c2} \end{aligned}$$

$$\boxed{R_{of}' = R_{c2}}$$

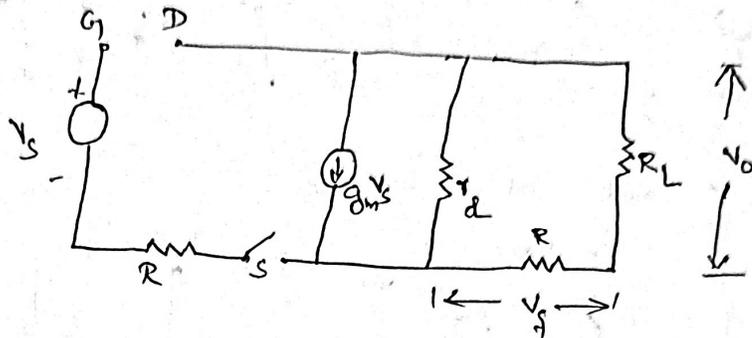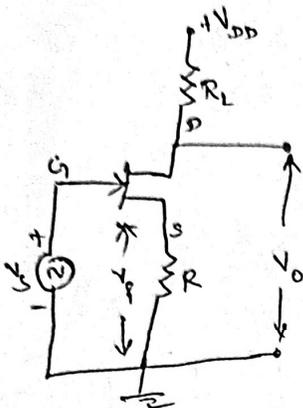19) FET Amplifier using Current Series F.B.



* Volt across 'R' constitute F.B signal,

* Load of I_D is same with the F.B signal hence it is named as Current Series F.B.

$$* V_f = I_D R$$

$$* I/p \text{ of the F.B} = o/p \text{ of } = I_D$$

hence,

$$\beta = \frac{V_f}{I_D} = * \frac{I_D R}{I_D} = * R$$

* without F.B $V_i = V_s$

hence,

$$G_m = A = \frac{I_D}{V_i} = \frac{I_D}{V_s} = \frac{-g_m r_d}{r_d + R_L + R} = \frac{-\mu}{r_d + R_L + R}$$

$$G_{mf} = A_f = \frac{G_m}{1 + G_m \beta} = \frac{-\mu}{r_d + R_L + R + \mu R}$$

* $R_i = \infty$


* similarly, $R_{if} = R_i D = \infty$ where $D = (1 + G_m \beta)$

* $R_o = r_d + R$


* since β is independence of R_L , $1 + \beta G_m = \frac{1 + \beta G_m}{R_L \rightarrow 0} = \frac{r_d + (\mu + 1)R}{r_d + R}$

* $R_{of} = R_o (1 + G_m \beta) = (r_d + R) \frac{r_d + (\mu + 1)R}{r_d + R} \Rightarrow \therefore R_{of \text{ tot}} = R_o \parallel R_{of}$

FET Source Follower As Volt. series F.B

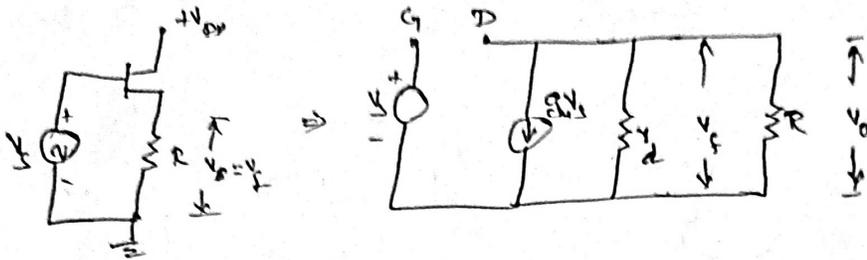

Simplified CM :-

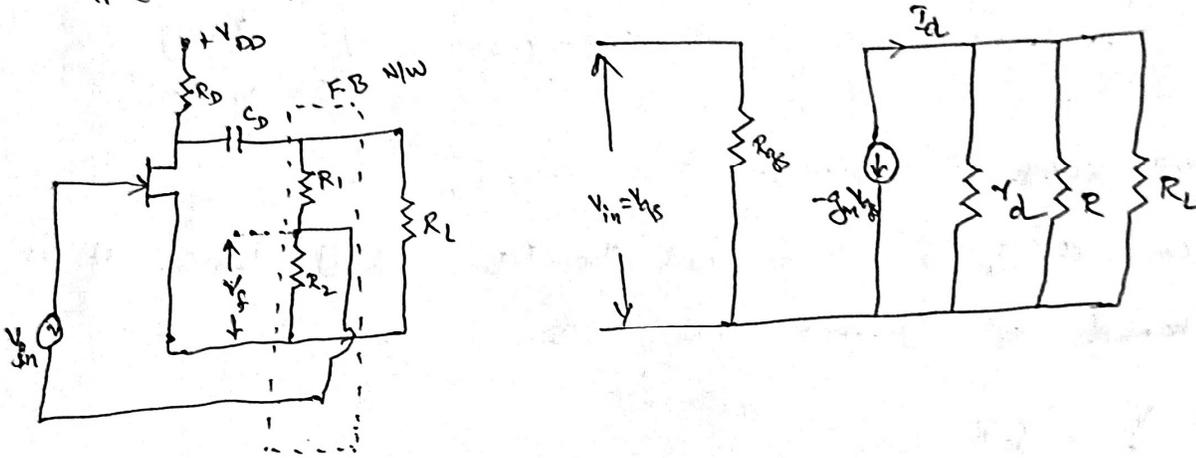

without F.B the amplifier gain is

$$V_o = I_d (y_d || R || R_L) \quad \text{where, } R = R_1 + R_2$$

$$I_d = -g_m V_{gs} = -g_m V_i$$

$$V_o = -g_m V_i (y_d || R || R_L)$$

$$A_v = \frac{V_o}{V_i} = -g_m (y_d || R || R_L)$$

* The F.B N/w provides a F.B factor of

$$\beta = \frac{V_f}{V_o} = \frac{-R_2}{R_1 + R_2} \quad (\text{using potential division rule})$$


$$\therefore \text{gain with } -ve \text{ F.B } A_f = \frac{A}{1 + A\beta}$$

$$A_f = \frac{-g_m (y_d || R || R_L)}{1 + \left(\frac{R_2}{R_1 + R_2}\right) g_m (y_d || R || R_L)}$$

$$* R_i = \infty \quad ; \quad R_o = y_d$$

Nyquist Criterion

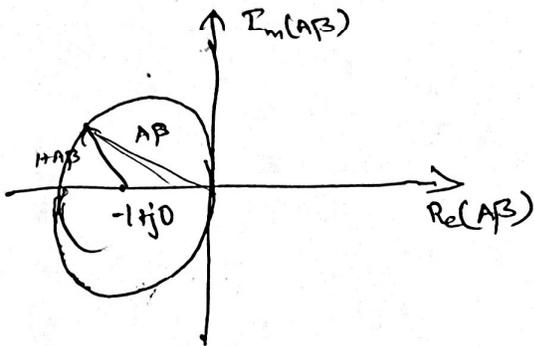- Alternate approach to obtain the condition for stability.
- loop gain (AFB) , being a complex number, may be represented as a point in the complex 'S' plane.





- Further AFB is a function of freq. (values is ω to ∞ points in the complex s-plane)

* Nyquist criterion state that, the amplifier is unstable if this curve encloses the point $-1 + j0$ and the amplifier is stable if the curve does not enclose this point.

✓ * If $|1 + AFB| = 1$ represent a circle of unit radius with its center at the point $-1 + j0$.

* If for any freq AFB extends outside the circle, the FB is negative, since $|1 + AFB| > 1$. on the other hand if AFB is lies entirely within the circle then $|1 + AFB| < 1$ and the FB is ~~negative~~ positive

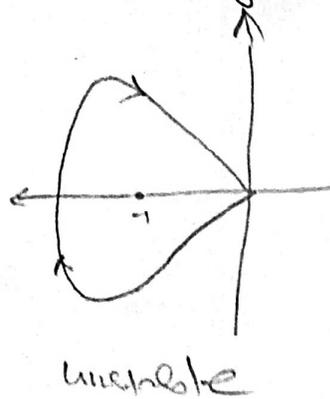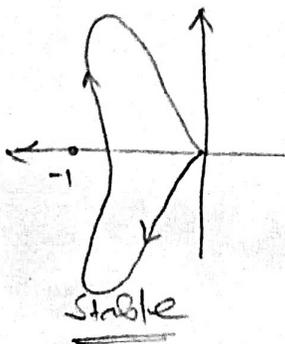

(17-01-21) 101

20 (1) When the -ve F.B is applied to an amplifier of gain 100, the overall gain falls to 50. Calculate (i) the F.B factor β (ii) If the same F.B factor maintained, the value of the amplifier gains required if the overall gain is to be 75.

Sol
 (1) $A_f = \frac{A}{1+A\beta}$ where, $A=100$ & $A_f = 50$

hence, $50 = \frac{100}{1+100\beta}$

(or) $1+100\beta = \frac{100}{50}$

$100\beta = 2 - 1$

$\beta = \frac{1}{100} = 0.01$

(ii)

$A_f = 75$; $\beta = 0.01$ what is $A = ?$

$\left(\frac{1}{A_f}\right) \frac{A\beta}{1+A\beta} = \frac{A}{1+A(0.01)} \Rightarrow A_f = \frac{75}{1-0.75} = 300$

(2) The gain of the amplifier without F.B is 50 whereas with -ve F.B it falls to 25. If due to ageing, the amplifier gain falls to 40. Find the percentage reduction in gain (i) without F.B (ii) with -ve F.B.

Sol

$A_f = \frac{A}{1+A\beta}$; given $A_f = 25$; $A = 50$

$25 = \frac{50}{1+50\beta}$ (or) $\beta = 0.02$ ✓

(i) without F.B % reduction in gain = $\frac{50-40}{50} \times 100 = 20\%$

iii) with -ve F.B;

when the gain without F.B was 50, the gain with F.B was 25, Now the gain without F.B falls to 40.

$$A_f = \frac{40}{1+0.02 \times 40} = 22.2 \checkmark$$

$$\% \text{ reduction in gain} = \frac{25 - 22.2}{25} \times 100 = \underline{\underline{11.2\%}}$$

(3) An amplifier has $A_f = 1000 \pm 100$. Determine the F.B needed to keep the gain with in ± 0.1 percent. Find A_f .

$$\underline{\text{sol}} \quad \frac{dA_f}{A_f} = 0.1\% = \frac{0.1}{100} = 10^{-3}$$

$$\frac{dA}{A} = \frac{100}{1000} = 0.1$$

$$D = 1 + A\beta = \frac{0.1}{10^{-3}} = 100$$

differentiation eq. of gain

$$A_f = \frac{A}{1 + A\beta}$$

diff. wrt.

$$\frac{dA_f}{A_f} = \frac{dA}{A} \left(\frac{1}{1 + A\beta} \right)$$

$$\text{If } A = 1000,$$

$$\beta = \frac{99}{1000} = \frac{1}{10} \text{ approximately}$$

$$A_f = \frac{A}{D} = \frac{1000}{100} = 10.$$

(4) If an amplifier has a gain of 60 db, a F.B of $\beta = 0.005$ is applied. What would be the change in overall gain of the F.B amplifier if the internal amplifier is subjected to a gain reduction of 12%.

$$\underline{\text{sol}}: A = 60 \text{ db} = 20 \log_{10} A = 1000$$

$$\beta = 0.005; \quad \frac{dA}{A} = 12\%$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \left(\frac{1}{1 + A\beta} \right) = \frac{0.12}{1 + 1000(0.005)} = 0.02$$

Therefore, the overall gain of the F.B amplifier will be reduced by 2%

22 (8) Amplifier without F.B has an o/p volt. $V_o = 50V$; with second harmonic distortion of 10% for $V_i = 0.5$ volt. Calculate
 (1) the amount of F.B necessary to reduce distortion to 1%.
 (2) The gain A_f (3) The new I/p Volt. required to restore V_o to 50 Volt. with 1% distortion.

(1) $A = \frac{V_o}{V_i} = \frac{50}{0.5} = 100$ ✓

Distortion $D = 10\%$ of V_o
 $= 0.1 \times 50 = 5$ volt. ✓

Distortion with F.B = $D_f = 0.01 \times 50 = 0.5$ volt. ✓
 reduced to 1%.

(1) The amount of F.B factor 'β' necessary to reduce the D_f to 1%.

$D_f = 2D$

is, $D_f = \frac{D}{1+A\beta} \Rightarrow 0.5 = \frac{5}{1+\beta 100}$

(or) $\beta = 0.09$

$A = \frac{V_o}{V_i} = \frac{50}{0.5}$

(2) $A_f = \frac{A}{1+A\beta} = \frac{100}{1+100 \times 0.09} = 10$

(3) $V_{if} = \frac{V_o}{A_f} = \frac{50}{10} = 5$ Volts.

- Q Two amplifiers each with a gain of 100 are connected in cascade and negative F.B applied to provide an overall gain of 20. determine (1) the required F.B factor
 (2) the percentage increase in the overall gain if the gain of each amplifier increases by 100%.

Sol

(a) $A_0 = A_1 \cdot A_2$ if $A_1 = A_2 = A$ then $A_0 = A^2$

hence gain with F.B $A_f = \frac{A^2}{1 + A^2 \beta}$

$$A_f = \frac{100^2}{1 + \beta 100^2} = 20 \quad -$$


$$\beta = 0.0499 \quad //$$

(b) $A_f = \frac{200^2}{1 + (0.0499) 200^2} = 20.03$

\therefore The increase in the overall gain $= \frac{20.03 - 20}{20} \times 100 \%$

$$= 0.15 \%$$

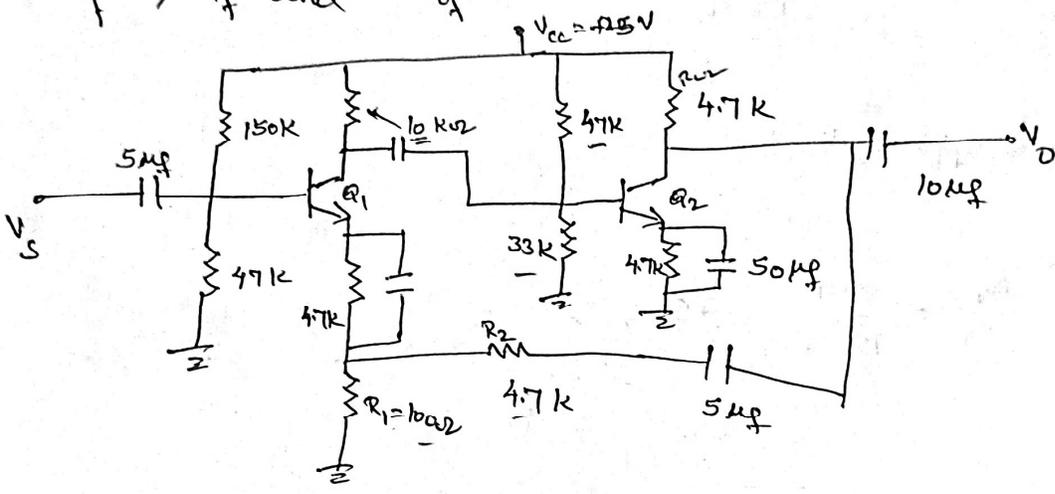21 5 Transistors in the F.B amplifier shown in figure are identical and their parameters are $h_{ie} = 1.1K$, $h_{fe} = 50$, $h_{re} = h_{oe} = 0$. Identify the F.B amplifier and calculate A_{v_f} , R_{i_f} and R_{o_f} .



* overall gain without F.B $A_v = A_{v1} \cdot A_{v2}$

* The effective load resistance R_{L1}' of Q_1 is,

$$R_{L1}' = 10K \parallel 47K \parallel 33K \parallel 1.1K = 942K \text{ (or) } 0.942K$$

* $R_{L2}' \Rightarrow R_{L2} = 4.7K$; $(R_1 + R_2) = 4.8K$

$$R_{L2}' = 4.7K \parallel 4.8K = 2.37K$$

* effective emitter resistance R_e of Q_1 is $R_1 \parallel R_2 = 100\mu \parallel 4.7K = 98\mu$ (or) $0.098K$

* Volt. gain $A_{v1} = \frac{-h_{fe} R_{L1}'}{h_{ie} + (1+h_{fe}) R_e} = \frac{-50 \times 0.942}{1.1 + (50+1) 0.098} = -7.72$

$$A_{v2} = \frac{-h_{fe} R_{L2}'}{h_{ie}} = \frac{-50 \times 2.37 \times 10^3}{1.1 \times 10^{-3}} = -108.$$

$$\therefore \text{overall volt. gain } A_v = A_{v1} \cdot A_{v2} = (-7.72) (-108) = 834$$

$$* \beta = \frac{R_1}{R_1 + R_2} = \frac{100}{4800} = \frac{1}{48}$$

$$\text{loop gain} \rightarrow A_v \beta = \frac{834}{48} = 17.4$$

$$D = 1 + A_v \beta = 18.4$$

$$* A_{vf} = \frac{A_v}{D} = \frac{834}{18.4} = 45.4$$

$$* R_i = h_{ie} + (1 + h_{fe}) R_e$$

$$= 1.1 + (1 + 50) 0.098 \times 10^3 = 6.1 \text{ k}$$

$$R_{if} = R_i D = 6.1 \times 10^3 \times 18.4 = 112.2 \text{ k}\Omega$$

* The output resistance without F.B

$$R_o' = R_{L2} = 2.37 \text{ k}$$

$$R_{of}' = \frac{R_o'}{D} = \frac{2.37 \text{ k}}{18.4} = 129 \Omega$$